

Input resistance of CE amplifier  
is very high  $\rightarrow r_{\pi} \uparrow$

$$R_{in} = r_{\pi} = \frac{\beta}{g_m} \rightarrow g_m \downarrow$$


$$A_v = \frac{V_o}{V_i} = -g_m (R_c \parallel R_L) \left( \frac{r_{\pi}}{r_{\pi} + R_{sig}} \right)$$

$$G_v = \frac{V_o}{V_{sig}}$$


$\swarrow$   $g_m \downarrow \rightarrow A_v \downarrow$

# emitter follower circuit (modified CE)

$\rightarrow$  helps to achieve high

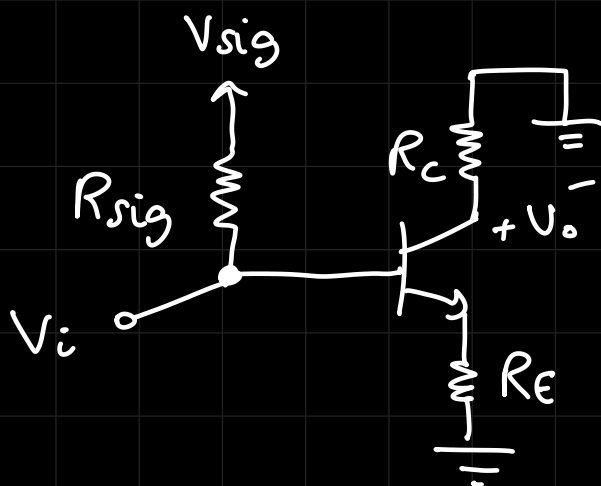

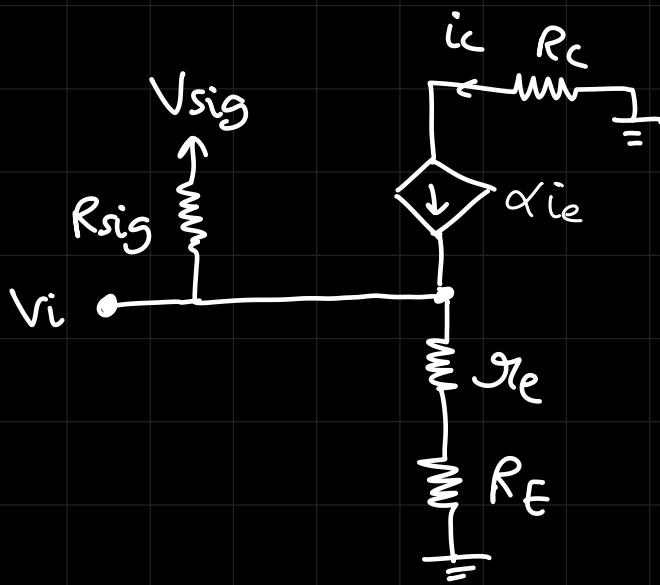T model of this ckt  $\rightarrow$  (AC equivalent)



$$R_{in} = \frac{V_i}{i_b} \quad \rightarrow \quad V_i = i_e (r_e + R_E)$$
$$i_e = (\beta + 1) i_b$$

$$R_{in} = (\beta + 1)(r_e + R_E)$$

$$R_{in} (\text{in CE w/o } R_E) = r_{\pi} = (\beta + 1) r_e$$

$$\frac{R_{in} (\text{CE with } R_E)}{R_{in} (\text{CE w/o } R_E)} = \frac{r_e + R_E}{r_e} = 1 + \frac{R_E}{r_e}$$


$$V_o = -i_c R_c = -\alpha i_e R_c$$

$$V_i = i_e (r_e + R_e)$$

$$A_{V_o} = \frac{V_o}{V_i} = \frac{-\alpha R_c}{r_e + R_e}$$

open ckt volt gain

now with  $R_L = ?$

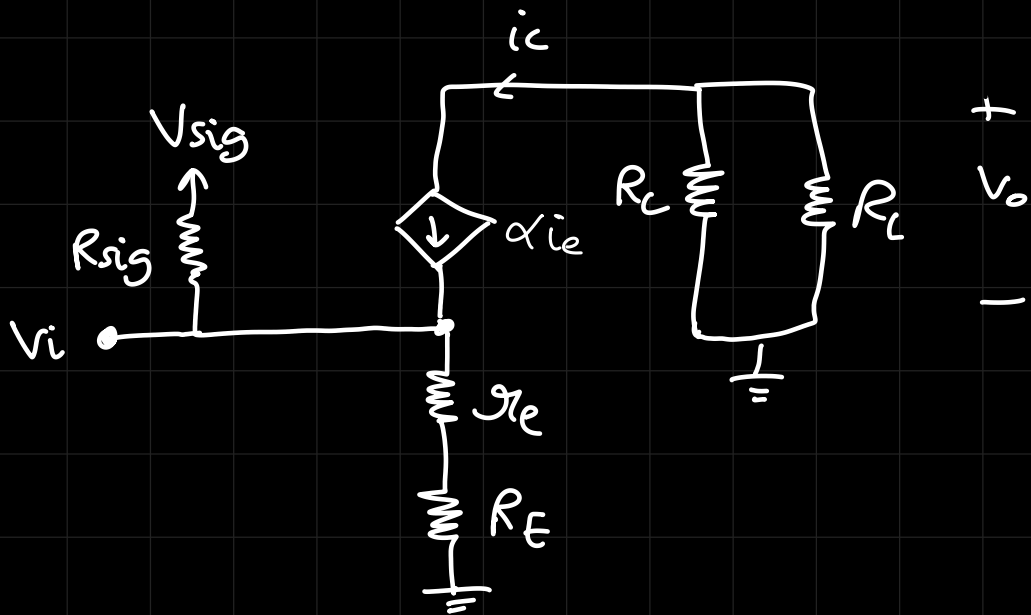

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -i_c (R_c \parallel R_L) = -\alpha i_e (R_c \parallel R_L)$$

$$V_i = i_e (r_e + R_e)$$


$$A_v = \frac{-\alpha (R_c \parallel R_L)}{r_e + R_e}$$

in the AC gain  $\rightarrow A_{v_o} = \frac{-\alpha R_c}{r_e + R_e}$

$$= \frac{-\alpha}{r_e} \left( \frac{R_c}{1 + \frac{R_e}{r_e}} \right) = \frac{-\alpha g_m R_c}{1 + g_m R_e}$$

Input impedance depends on your input signal swing

Condition:  $R_{in} \gg R_{sig}$

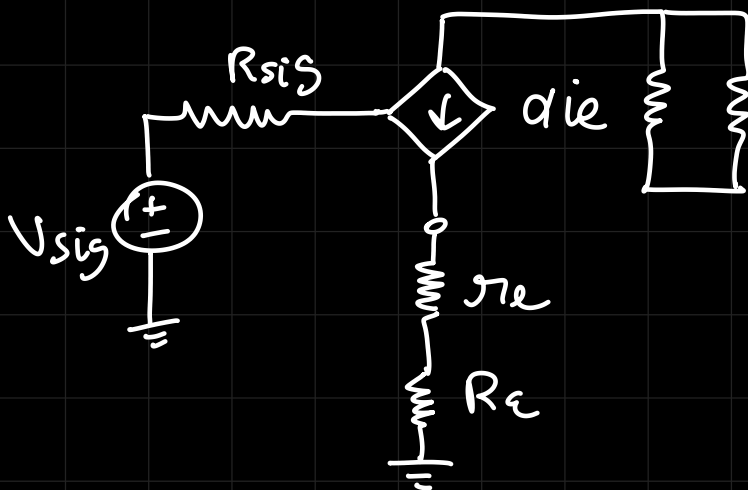

$$G_v = \frac{V_o}{V_{sig}} = \frac{V_o}{V_i} \times \frac{V_i}{V_{sig}}$$

$$G_v = \frac{-\alpha i_e (R_c \parallel R_L)}{i_e (r_e + R_e)} \times \frac{V_i}{V_{sig}} = \frac{-\alpha (R_c \parallel R_L)}{r_e + R_e + R_{sig}}$$

$$V_i = V_{sig} \times \frac{r_e + R_e}{r_e + R_e + R_{sig}}$$

Other way  $\rightarrow V_{sig} = V_i + i_b R_{sig}$

$$\begin{aligned} V_{sig} &= i_e (R_e + r_e) + i_b R_{sig} \\ &= i_b (\beta + 1) (R_e + r_e) + i_b R_{sig} \end{aligned}$$


$$\frac{V_i}{V_{sig}} = \frac{(\beta + 1) (R_e + r_e)}{(\beta + 1) (R_e + r_e)}$$

- ①  $R_{in}$  is much higher than standard CE
- ②  $A_{v_o}$  reduces
- ③  $G_v$  is more tolerant to  $\beta$  variations


> Note: CE amp: phase out of  $180^\circ$  wrt  $V_i$

CB amp: same phase  
i.e. gain  $+ve$

# # Common Base Configuration

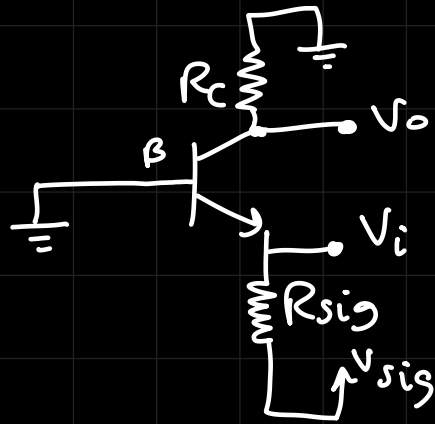

AC equivalent

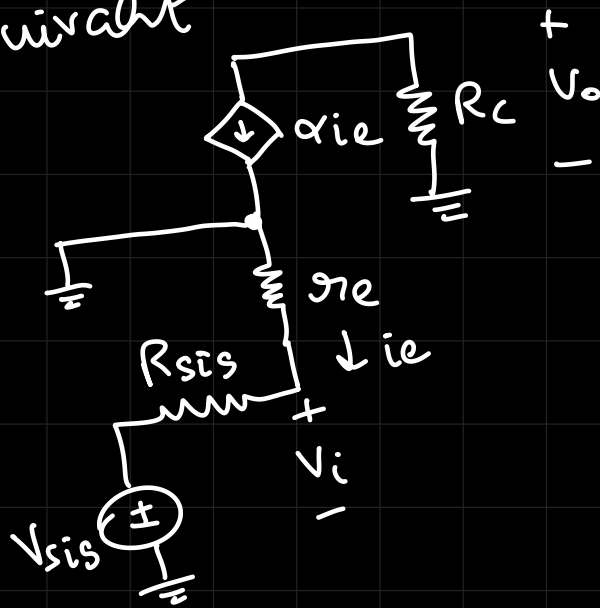

$$\alpha \approx 1 \rightarrow R_{in} = r_e = \frac{1}{g_m}$$


$$A_{v_o} = \frac{V_o}{V_i} = \frac{-\alpha i_e (R_C)}{-i_e r_e} = \frac{\alpha R_C}{r_e} = \underline{g_m R_C}$$

Some phase gain

put Load R

$$A_v = \frac{-\alpha i_e (R_c \parallel R_L)}{-i_e r_e}$$

$$= g_m (R_c \parallel R_L)$$

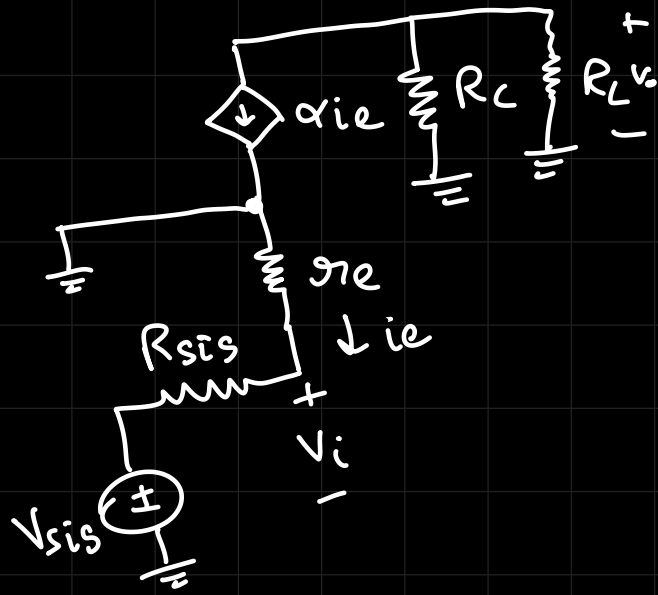

$$G_v = \frac{V_o}{V_{sig}} = \frac{-\alpha i_e (R_c \parallel R_L)}{V_{sig}}$$

$$V_i = V_{sig} \times \frac{r_e}{r_e + R_{sig}}$$

$$G_v = \frac{\alpha (R_c \parallel R_L)}{r_e + R_{sig}} \quad \checkmark$$

TRADEOFF:


+ve  $\rightarrow$  output follows input phase

-ve  $\rightarrow$   $R_{in}$  smaller than CE amp

because  $R_{in} = r_e$  here but  $R_{in} = r_{\pi}$  there and  $r_e < r_{\pi}$

# # Common collector Config

buffer amp ↷

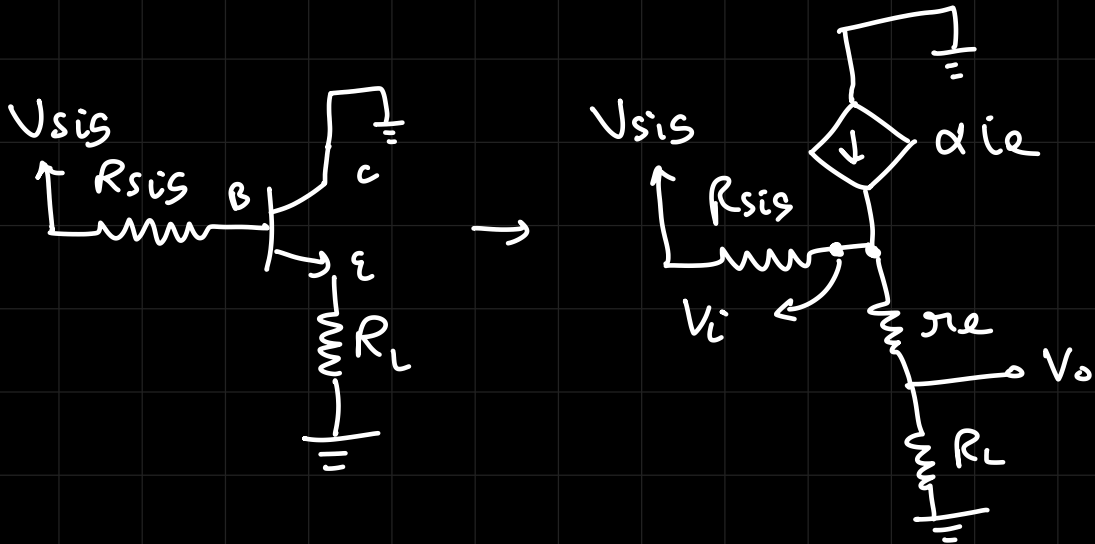

$$R_{in} = \frac{V_i}{i_b} = \frac{V_i(\beta+1)}{i_e} = (\beta+1)(r_{be} + R_L)$$


$$A_v = \frac{V_o}{V_i} = \frac{i_e R_L}{i_e (r_{be} + R_L)} = \frac{R_L}{r_{be} + R_L}$$

$$A_{v0} = \frac{V_o}{V_i} \rightarrow \text{remove } R_L$$

$$= \frac{i_e r_{be}}{i_e r_{be}} = \boxed{1}$$

or mathematically  $\rightarrow R_L = \infty$
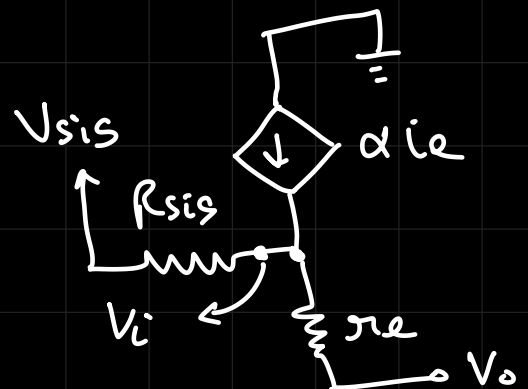
$$A_{v0} = \frac{1}{1 + r_{be}/R_L} \approx \frac{1}{1}$$





$$G_v = \frac{V_o}{V_{sig}} = \frac{V_o}{V_i} \times \frac{V_i}{V_{sig}} = \frac{R_L}{r_e + R_L} \times \frac{i_e(r_e + R_L)}{V_{sig}}$$

$$V_i = \frac{V_{sig} \times (r_e + R_L)(\beta + 1)}{(\beta + 1)(r_e + R_L) + R_{sig}}$$

$$V_{sig} = \frac{i_e(r_e + R_L)}{r_e + R_L} \times \frac{r_e + R_L + R_{sig}}{r_e + R_L}$$

$$G_v = \frac{(\beta + 1) R_L}{(\beta + 1)(R_L + r_e) + R_{sig}} \quad \approx \text{comes down to almost unity } (\sim 0.9 - 1)$$

$(\beta + 1) R_L$  is the main scaling factor and if  $(\beta + 1) R_L$  becomes much much greater than  $R_{sig} \rightarrow G_v \approx 1$

Used when src resistance is very high