

Lecture: TRANSMISSION LINES

$$\frac{\partial I}{\partial z} = -VY$$

↓
admittance

$$\frac{\partial V}{\partial z} = -IZ$$

↑ same as X
↓
impedance

$$\frac{\partial^2 I}{\partial z^2} - \gamma^2 I = 0$$

$$\frac{\partial^2 V}{\partial z^2} - \gamma^2 V = 0$$

$$\gamma = \sqrt{XY}$$

$$X = R + j\omega L$$

$$Y = G + j\omega C$$

$$\frac{1}{R_s}$$

↙

$$I(z) = \overset{\text{forward travelling}}{I_0^+ e^{-\gamma z}} + \overset{\text{backward travelling}}{I_0^- e^{\gamma z}}$$

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$= V_0^+ e^{-i\beta z} e^{-\alpha z} + V_0^- e^{i\beta z} e^{\alpha z}$$

$$v = \frac{1}{\sqrt{LC}} \quad : \text{velocity}$$

Tx line with no reflected wave

$$V(z) = V_0^+ e^{-\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z}$$

$$\frac{V(z)}{I(z)} = Z_0 = \frac{V_0^+}{I_0^+}$$

Characteristic
Impedance
↳ Z_0

$$\frac{\partial V}{\partial z} = \frac{\partial (V_0 e^{-\gamma z})}{\partial z} = -\gamma V = -\gamma V_0 e^{-\gamma z}$$

$$-\gamma V_0^+ e^{-\gamma z} = -\gamma I_0^+ e^{-\gamma z}$$

$$\frac{V_0^+}{I_0^+} = \frac{\gamma}{\gamma} = \frac{\gamma}{\sqrt{\gamma^4}} = \sqrt{\frac{\gamma}{\gamma}}$$

$$\text{So, } Z_0 = \sqrt{\frac{\gamma}{\gamma}} = \frac{\sqrt{R + j\omega L}}{\sqrt{G + j\omega C}}$$


In lossless transmission:

$$Z_0 = \sqrt{\frac{\gamma}{\gamma}} = \sqrt{\frac{0 + j\omega L}{0 + j\omega C}} = \sqrt{\frac{L}{C}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$


for backward travelling wave:
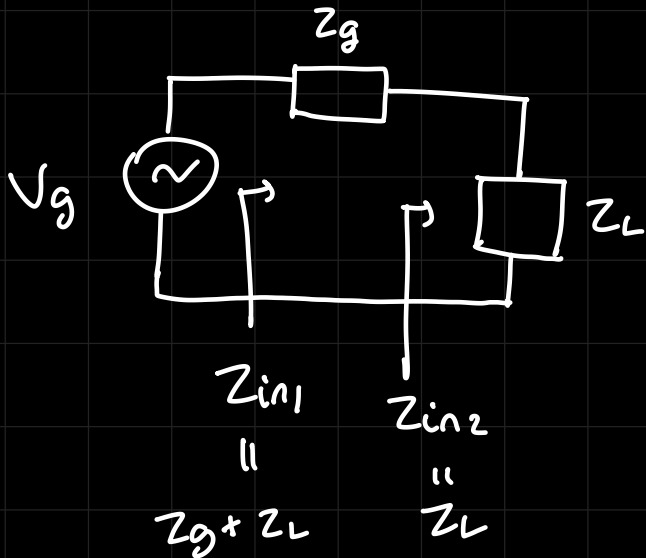
$$\textcircled{1} * \begin{cases} Z_0 \rightarrow -Z_0 \\ V_o^- = -Z_0 I_o^- \\ V_o^+ = Z_0 I_o^+ \end{cases} \quad \frac{V_o^-}{I_o^-} = -Z_0$$



for a small circuit
like this \leftarrow
it ez to determine
input impedances

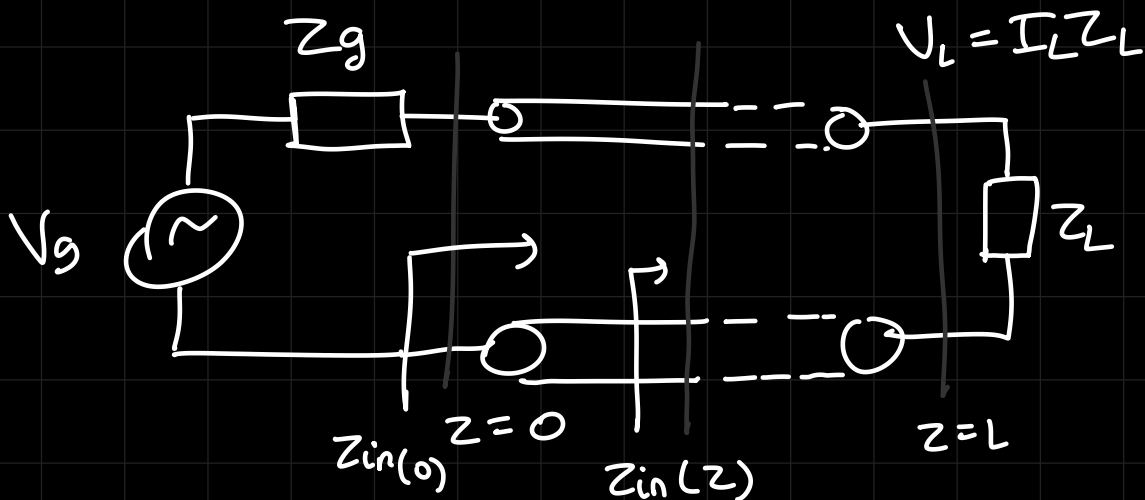for transmission lines we have to
consider the π ckt of R, L, C, R_s as well



g) given L ; what is Z_{in} ?

$$Z_{in}(z) = \frac{V(z)}{I(z)}$$

$$Z_{in} = Z_{in}(0) = \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{I_0^+ + I_0^-}$$

$$\left\{ \text{from ①} \right\} = \frac{V_0^+ + V_0^-}{\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}} = Z_0 \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) \quad \text{②}$$

$$+ \begin{cases} I_L = I_0^+ e^{-\gamma L} + I_0^- e^{\gamma L} \\ V_L = V_0^+ e^{-\gamma L} + V_0^- e^{\gamma L} \\ Z_0 I_L = V_0^+ e^{-\gamma L} - V_0^- e^{\gamma L} \end{cases}$$

↓

$$V_L + Z_0 I_L = 2V_0^+ e^{-\gamma L}$$

$$V_L - Z_0 I_L = 2V_0^- e^{\gamma L}$$

$$V_0^+ = \frac{1}{2} (Z_L + Z_0) I_L e^{\gamma L}$$

$$V_0^- = \frac{1}{2} (Z_L - Z_0) I_L e^{-\gamma L}$$

back to ②

$$Z_{in} = Z_0 \left(\frac{V_o^+ + V_o^-}{V_o^+ - V_o^-} \right)$$

$$= Z_0 \left(\frac{(Z_L + Z_0)e^{\gamma L} + (Z_L - Z_0)e^{-\gamma L}}{(Z_L + Z_0)e^{\gamma L} - (Z_L - Z_0)e^{-\gamma L}} \right)$$

$$= Z_0 \left(\frac{Z_L(e^{\gamma L} + e^{-\gamma L}) + Z_0(e^{\gamma L} - e^{-\gamma L})}{Z_L(e^{\gamma L} - e^{-\gamma L}) + Z_0(e^{\gamma L} + e^{-\gamma L})} \right)$$

$$= Z_0 \left(\frac{Z_L \cdot \cosh(\gamma L) + Z_0 \cdot \sinh(\gamma L)}{Z_L \cdot \sinh(\gamma L) + Z_0 \cdot \cosh(\gamma L)} \right)$$

$$\# \quad Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh(\gamma L)}{Z_L \tanh(\gamma L) + Z_0} \right]$$

for a lossless transmission: $\gamma = j\beta$

$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tanh(\beta L)}{Z_0 + jZ_L \tanh(\beta L)} \right]$$

remember : reflection coefficient

$$\Gamma(z) = \frac{V_0^- e^{\gamma z}}{V_0^+ e^{-\gamma z}} = \frac{V_0^-}{V_0^+} e^{2\gamma z}$$

$$\Gamma_L(z) = \frac{V_0^- e^{\gamma L}}{V_0^+ e^{-\gamma L}}$$

$$\left. \begin{aligned} \frac{1}{2}(V_L + Z_0 I_L) &= V_0^+ e^{-\gamma L} \\ \frac{1}{2}(V_L - Z_0 I_L) &= V_0^- e^{\gamma L} \end{aligned} \right\} \text{from before}$$

$$\Gamma_L(z) = \frac{V_L - Z_0 I_L}{V_L + Z_0 I_L} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\# \quad \Gamma_L(z) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

reflection coeff
right at the
load


We won't have any reflected wave

① when: $\Gamma_L(z) = 0$ i.e. $Z_L = Z_0$

(matched impedance/load)

RFIC

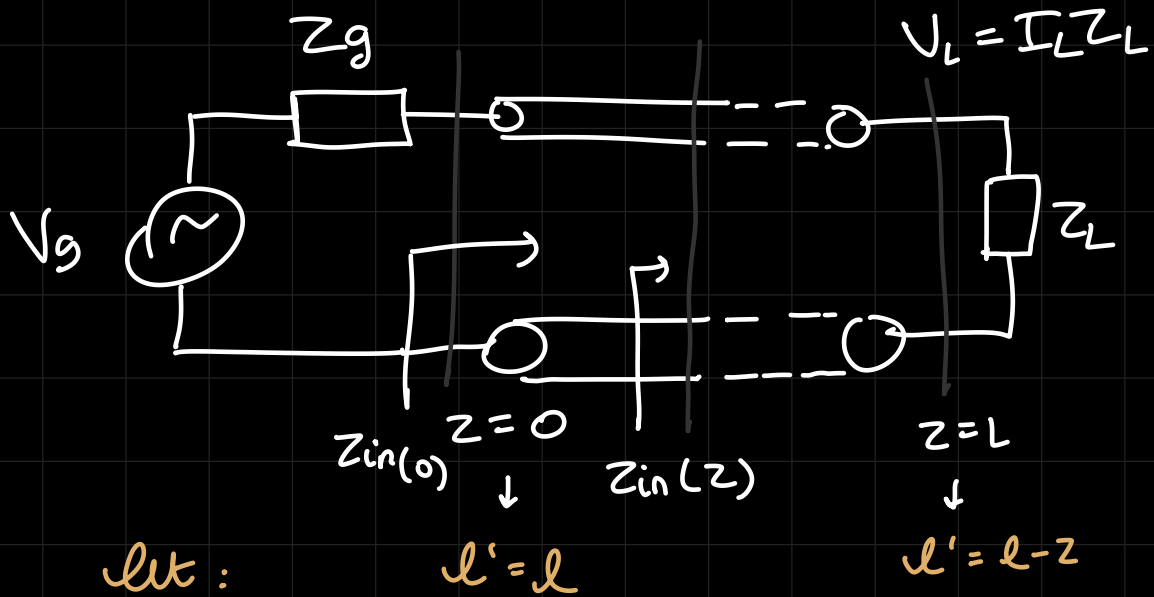② or when the 1st medium is infinitely large
i.e. the interface is at ∞
($L \rightarrow \infty$)



$$\Gamma(z) = \frac{V_0^- e^{\gamma L}}{V_0^+ e^{-\gamma L}} \times \frac{e^{-\gamma L}}{e^{-\gamma z}} \times e^{2\gamma z}$$

$$= \Gamma_L e^{-2\gamma(L-z)} = \Gamma_L e^{-2\gamma l'}$$

$\Gamma(z) = \Gamma_0 e^{-2\gamma l'}$

$$\rightarrow Z_{in}(z) = \frac{V(z)}{I(z)} = \frac{V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}}{I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}}$$

$$= \frac{V_0^+ + V_0^- e^{2\gamma z}}{\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} e^{2\gamma z}} \quad \downarrow \times \frac{e^{\gamma z}}{e^{\gamma z}}$$

$$= \left(\frac{1 + \frac{V_0^-}{V_0^+} e^{2\gamma z}}{1 - \frac{V_0^-}{V_0^+} e^{2\gamma z}} \right) Z_0 \quad \downarrow \div \frac{V_0^+}{V_0^+}$$

$Z_{in} = Z_0 \left(\frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right)$

Reflection coeff (current)

$$\Gamma_{\text{current}_L} = \frac{I_o^- e^{\gamma L}}{I_o^+ e^{-\gamma L}} = -\frac{V_o^- e^{2\gamma L}}{V_o^+} = -\Gamma_{\text{voltage}_L}$$

$$\# \quad \Gamma_{I_L} = -\Gamma_{V_L}$$

Considering lossless transmission

$$\begin{aligned} V(z) &= V_o^+ e^{-i\beta z} + V_o^- e^{i\beta z} \\ &= V_o^+ \cos \beta z - j V_o^+ \sin \beta z + V_o^- \cos \beta z + j V_o^- \sin \beta z \\ &= \cos \beta z (V_o^+ + V_o^-) - j \sin \beta z (V_o^+ - V_o^-) \end{aligned}$$

$$\begin{aligned} \text{amplitude} = |V(z)| &= \sqrt{\cos^2 \beta z (V_o^+ + V_o^-)^2 + \sin^2 \beta z (V_o^+ - V_o^-)^2} \\ &= V_o^{+2} + V_o^{-2} + 2V_o^+ V_o^- \cos(2\beta z) \end{aligned}$$

$$\text{maxima: } \cos(2\beta z) = \cos(2n\pi) = 1$$

↓

$$z = \frac{n\pi}{\beta}$$

$$\boxed{|V(z)|_{\text{max}} = V_o^+ + V_o^-}$$

$$\text{note: } \beta = \omega \sqrt{LC}$$

$$\text{minima: } \cos(2\beta z) = \cos((2n+1)\pi) = -1$$

$$z = \frac{(2n+1)\pi}{\beta}$$

$$\rightarrow \boxed{|V(z)|_{\text{min}} = V_o^+ - V_o^-}$$


$$\beta \rightarrow \frac{2\pi}{\lambda}$$

$$\text{max : at } z = \frac{n\pi}{\beta} = \frac{n\lambda}{2}$$

$$\text{min : at } z = \left(n + \frac{1}{2}\right)\lambda$$

$\beta \equiv$ wave number
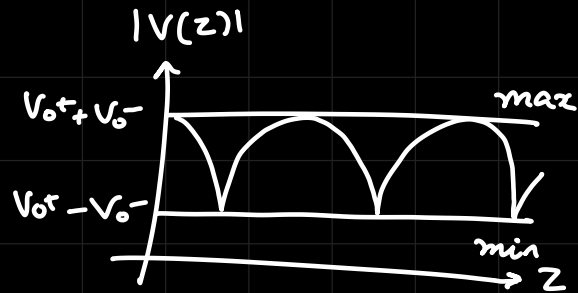
$$\text{and hence } \beta = \frac{2\pi}{\lambda}$$



Standing wave pattern

if $V_0^+ = V_0^- \rightarrow$ pure standing wave

if no reflected back i.e. $V_0^- = 0$,

we get a straight line standing wave pattern

VSWR (voltage standing wave ratio)

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

if $\Gamma_L = 1/-1$ i.e. everything is getting reflected back
 \downarrow

$S = \infty$ (standing wave)

if $|\Gamma_L| = 0 \rightarrow S = 1$

$$1 \leq S \leq \infty$$