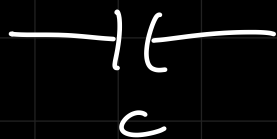


Lecture  $\rightarrow$  Tut



DC  $\rightarrow \omega = 0$

$$X_C = \frac{1}{\omega C} = \infty \quad \text{OC}$$

AC  $\rightarrow \omega \gg \gg$

$$X_C = \frac{1}{\omega C} = 0 \quad \text{SC}$$


all the params bias Base, Collector and emitter current by using DC analysis

Also, the Q point of the transistor calculated by DC Analysis


The input impedance, output impedance and the gain of the BJT calculated by AC analysis

We have 2 imp methods to solve the BJT under AC analysis

(a)  $\pi$  model

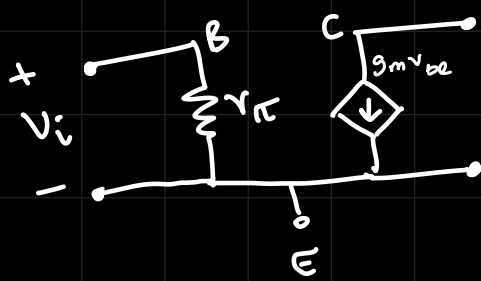

(b) T model

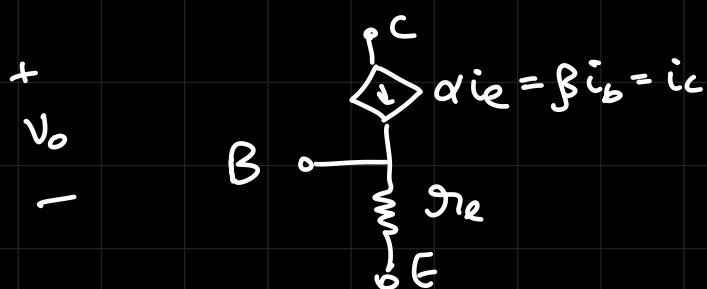


if early effect  
voltage given  
then consider  $r_o$   
in  $\pi$  model

$$r_{\pi} = (\beta + 1) r_e$$
$$r_{\pi} \approx \beta r_e$$

$$r_e = \frac{V_T}{I_E}$$


thermal voltage

$$V_T = 25 / 26 \text{ mV}$$

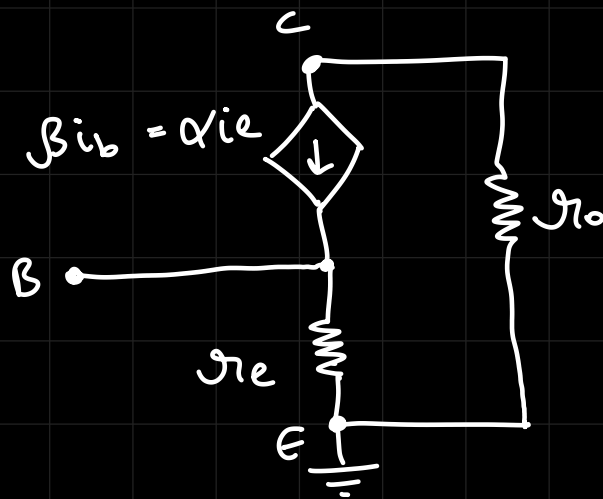

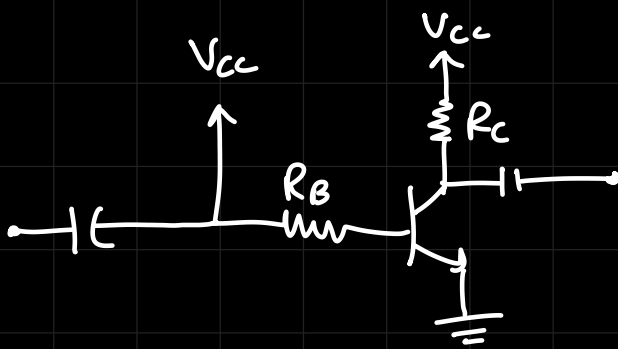g) for a given BJT configuration, determine the  $Z_{in}$ ,  $Z_{out}$ ,  $A_v$

NOTE: we only use  $\pi$  model if there is a capacitor



Fixed Bias


DC analysis

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

↓  
leakage current



no  $R_C$  so, we use  $\pi$  model

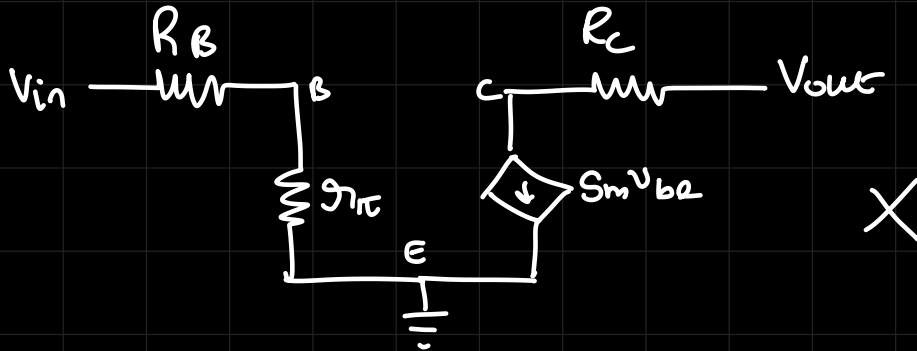


$$V_{out} = -g_m V_{be} R_C$$

$$V_{be} = \frac{r_{\pi}}{r_{\pi} + R_B} V_{in}$$

$$\frac{V_{out}}{V_{in}} = -\frac{I_C}{I_B} \times \frac{V_T / I_B}{V_T / I_B + R_B}$$

} X

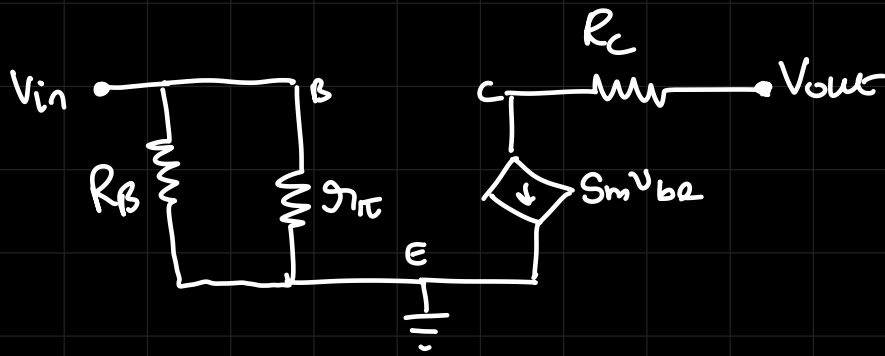

$$V_{out} = -g_m v_{be} \cdot R_C$$

$$v_{be} = \left( \frac{r_{\pi}}{r_{\pi} + R_B} \right) V_{in}$$


$$\frac{V_{out}}{V_{in}} = -g_m R_C \left( \frac{r_{\pi}}{r_{\pi} + R_B} \right)$$

$$Z_{in} = r_{\pi} \parallel R_B$$

$$Z_{out} = R_C$$

$$\text{if } r_o \text{ given} \rightarrow Z_{out} = R_C \parallel r_o$$

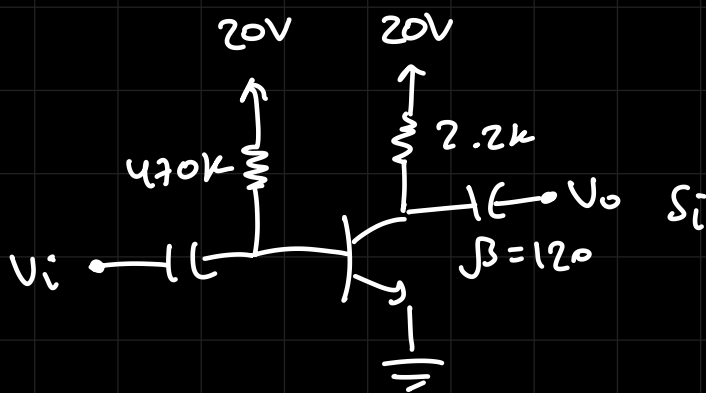Q) calculate  $Z_{in}$ ,  $Z_{out}$ ,  $A_v$ , Q point



$$-20 + 470k(I_B) + 0.7 = 0$$


$$I_B = 19.3 / 470k = 41 \mu A$$

$$I_C = 4.92 \text{ mA}, I_E = 4.96 \text{ mA}$$

$$-20 + 2.2(4.92) + V_{CE} = 0$$

$$V_{CE} = 20 - 10.824 = 9.176 \text{ V}$$
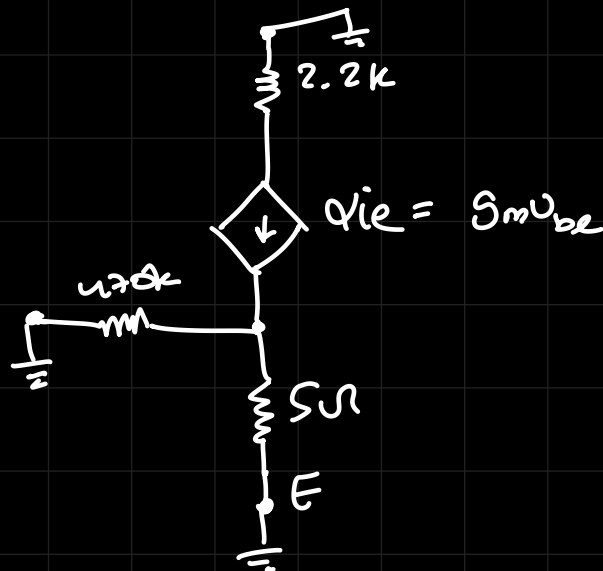
$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{4.96 \text{ mA}} = \sim 5 \Omega$$




$(9.18 \text{ V}, 4.92 \text{ mA})$

$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{1}{R_C} V_{CC}$$


$$y = mx + c$$

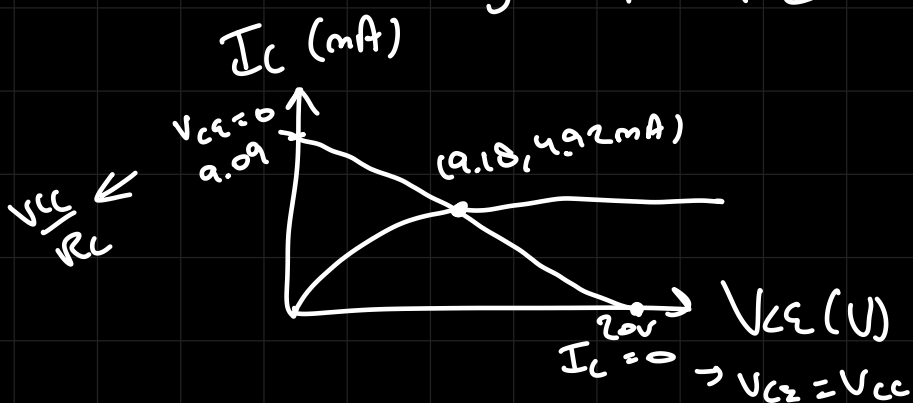

AC analysis  $\rightarrow$  DC remove

$C \rightarrow SC$

$\pi$  model

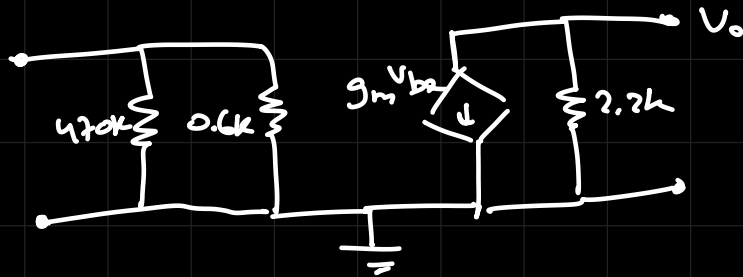

$$r_{\pi} = \frac{V_T}{I_B} = \frac{25}{41} K = 0.6k$$

$$V_o = - \frac{2.2k}{8} V_{be}$$

$$V_{be} = V_{in} (470k \parallel 0.6k)$$


$$\frac{V_o}{V_{in}} =$$

$$V_o = -\beta i_b R_c$$


$$i_b = \frac{V_i}{\beta r_e}$$

$$A_v = -\frac{\beta}{\beta r_e} R_c = -\frac{R_c}{r_e} = -40 V/V$$

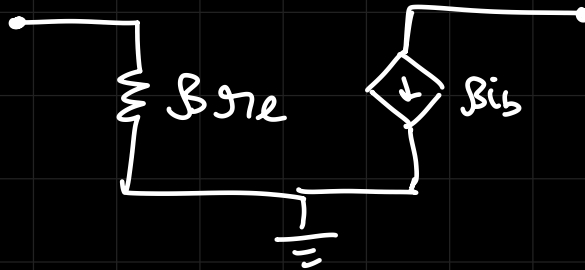repeat all the params in the above numerical considering  $r_o = 50k\Omega$  (early effect impedance)



g) find  $Z_{in}$ ,  $Z_{out}$ ,  $A_v$

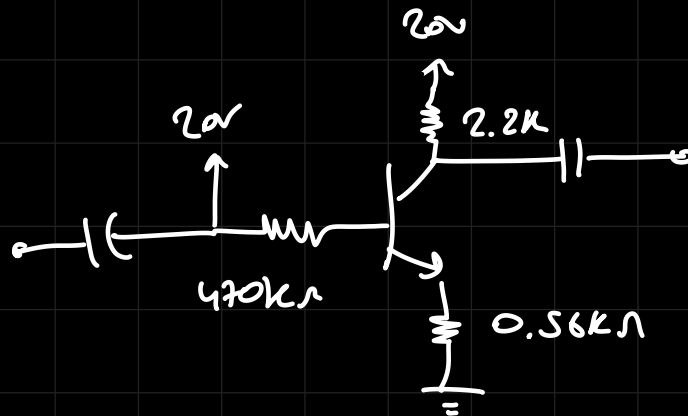

$$-20 + 470k(I_B) + 0.7 + 560I_E = 0$$

If  $R_e$  exists  $\rightarrow T$  model  
else  $\pi$  model

$$-20 + 470k(I_B) + 0.7 + 560I_E = 0$$

$$I_B(470k + 67.76k) = 19.3$$

$$I_B = 35.8 \mu A$$


$$I_E = 4.34 \text{ mA}$$

$$I_C = 4.296 \text{ mA}$$

$$-20 + 9.45 + V_{CE} + 2.43 = 0$$

$$V_{CE} = 8.12 \text{ V}$$
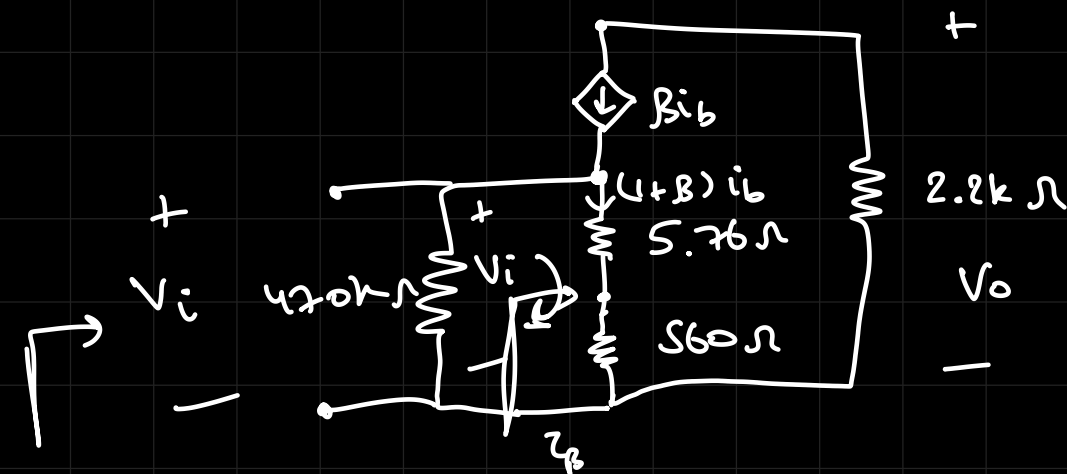
$$r_e = \frac{V_T}{I_E} = \frac{25}{4.34} = 5.76 \Omega$$



$$Z_o = 2.2k\Omega$$

$$Z_{in} = 470k \parallel 565.76\Omega$$

$$= \frac{470 \times 565}{470.565} = 564.32 \Omega$$



$$\text{KVL} \rightarrow -V_i + (1+\beta)i_b(R_e + r_e) = 0$$

$$\Rightarrow V_i = (1+\beta)i_b(R_e + r_e)$$

$$Z_b = \frac{V_i}{i_b} = (1+\beta)(R_e + r_e) \\ = (121)(565.76) = 68.45 \text{ k}\Omega$$

$$Z_{in} = R_B \parallel Z_b = 59.7 \text{ k}\Omega$$

$$V_i = (1+\beta)i_b(R_e + r_e)$$


$$V_o = -i_c R_c \\ = -\beta i_b R_c \\ = -\beta R_c \left( \frac{V_i}{(1+\beta)(R_e + r_e)} \right)$$

$$\text{Assume } \beta \approx \beta + 1$$

$$A_v = \frac{-R_c}{R_e + r_e} = \frac{-2.2 \text{ k}}{565.76} = -3.8 \text{ V/V}$$

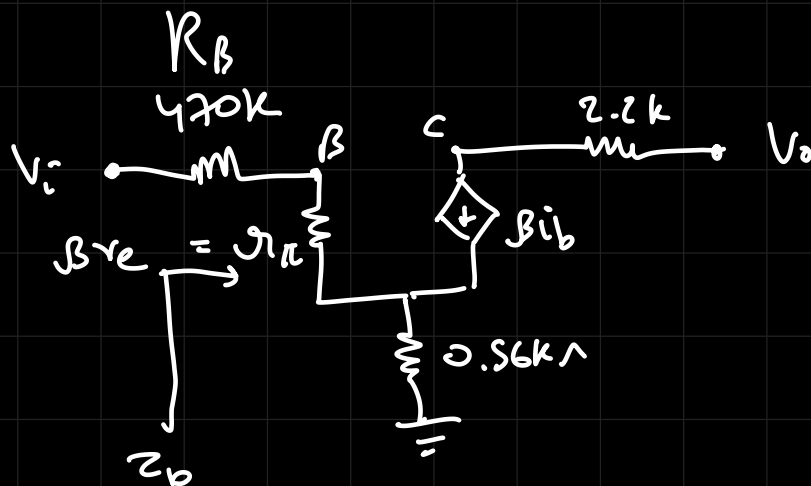g) now do with  $\pi$  model

$$r_{\pi} = \frac{V_T}{I_B} = \frac{25}{35.8 \mu} = 700 \Omega$$



$$V_o = -\beta i_b \cdot R_c$$

$$\times \left\{ i_b = \frac{V_i}{\beta r_e + 0.56k} \right\} \quad V_i = i_b \beta r_e + (1+\beta) R_e$$

$$\times \left\{ \frac{V_o}{V_i} = \frac{-\beta R_c}{\beta r_e + 0.56k} = \frac{-2.2k(120)}{5.76(120) + 560} = \frac{-264}{1.25} = -211.2 \right.$$

$$V_i = i_b (r_e + R_e) \beta \Rightarrow \beta \approx 1+\beta$$

$$\frac{V_o}{V_i} = \frac{-R_c}{r_e + R_e} = -3.8 V/V \quad \text{Same } \checkmark$$

$$Z_b = \frac{V_i}{i_b} = (r_e + R_c) \beta$$
$$= 67.87 \text{ k}\Omega$$

$$Z_{in} = R_B \parallel Z_b = 59.32 \text{ k}\Omega$$

$$Z_o = R_c$$