

Lecture


→ CLASS B Power amplifier

TRANSFORMER COUPLED PUSH PULL Amp

→ It consists of 2 identical transformers and 2 identical transistors Q_1 and Q_2


→ $Q_1 \rightarrow$ NPN , $Q_2 \rightarrow$ PNP

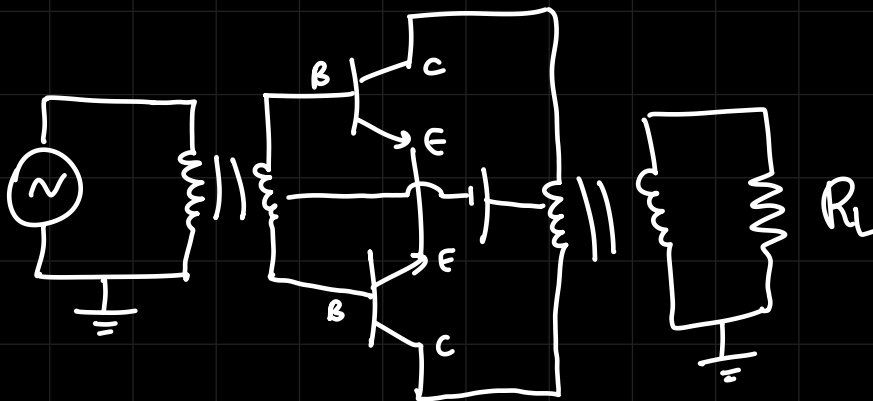→ The secondary winding of the 1st transformer and the primary winding of the 2nd transformer is center tap.




DC $\rightarrow X_L = 0$ for both short circuit

$$V_{BE1} - V_{BE2} = 0$$


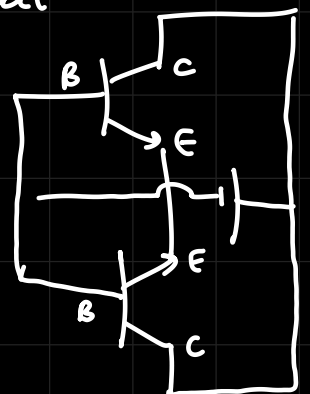


two transistors are used to obtain sinusoidal output. for each transistor, the base terminal are shorted & the emitter wrt DC as shown in the eqⁿ. Therefore, both the transistors remain off / cutoff when no AC input.

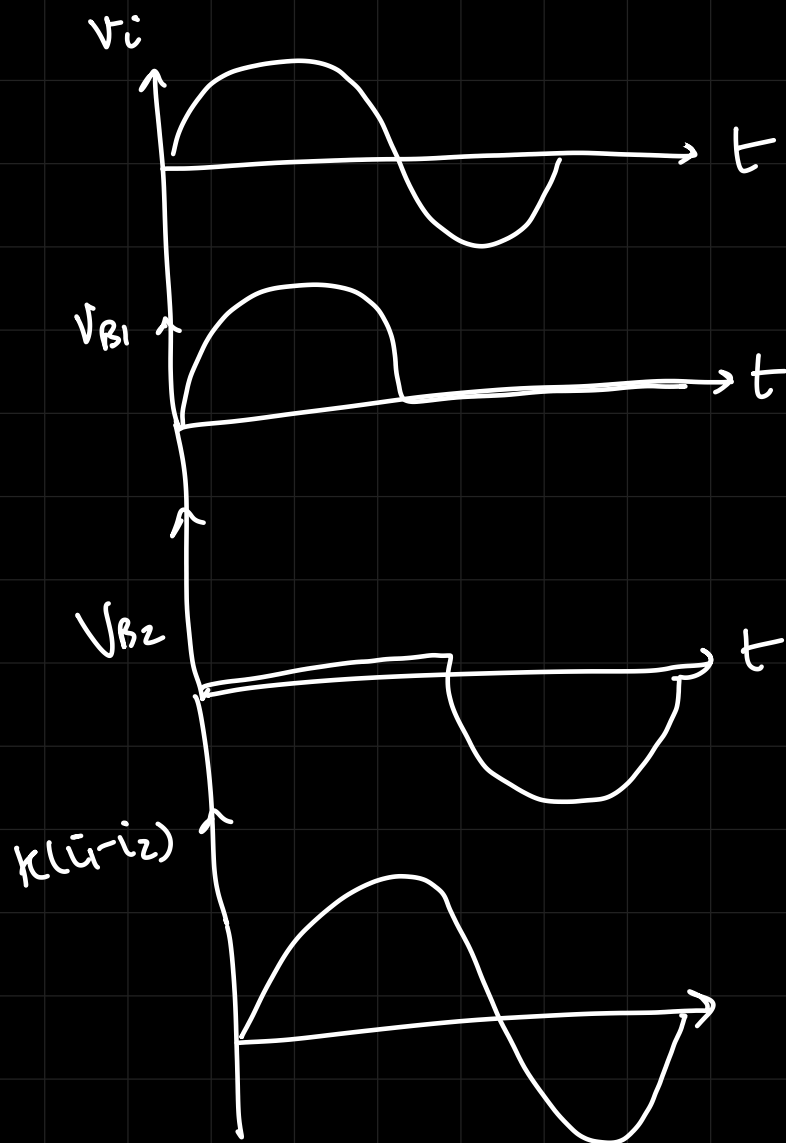when AC input is applied at the Base 1,2
 $V_{in} \Rightarrow$



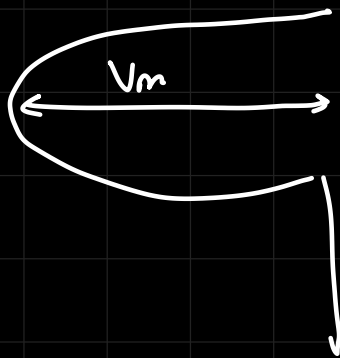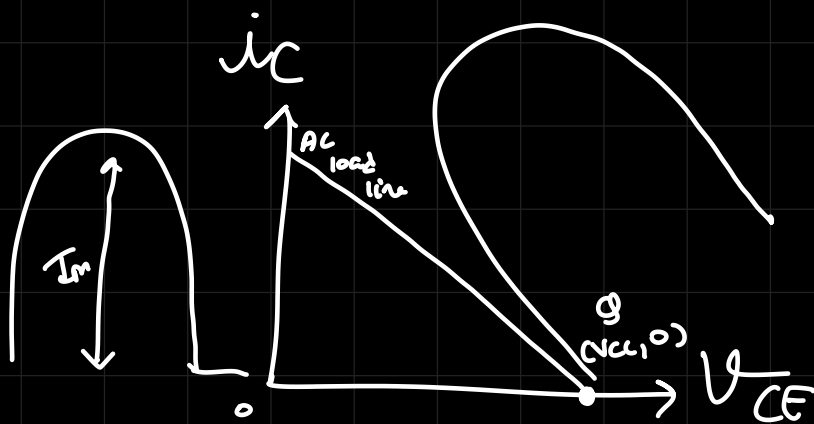Note: DC and AC load line similar as class A transformer coupled amplifier but in class B amplifier operating point will be at extreme end point of the load line.



conduction angle $\rightarrow 180^\circ$

$$\eta \% = \frac{P_{ac}}{P_{dc}} \times 100\%$$

$$P_{ac} = V_{rms} \times I_{rms}$$

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} = \frac{V_{CC} - 0}{\sqrt{2}} \times \frac{I_m - 0}{\sqrt{2}}$$

$$= \frac{V_{CC} \times I_m}{2}$$

$$P_{dc} = V_{oc} I_{pc}$$


$$I_{avg} = I_{pc} = \frac{I_m}{\pi} + \frac{I_m}{\pi} = \frac{2I_m}{\pi}$$

$$\eta \% = \frac{\frac{1}{2} \frac{V_{cc} \times I_m}{V_{cc} \times \frac{2I_m}{\pi}}}{\frac{\pi}{4}} \times 100 = \frac{78.5\%}{\text{ideal case}} \downarrow$$



DRAWBACK of class B Amplifier is

CROSS OVER DISTORTION

which is over come by class AB amplifier

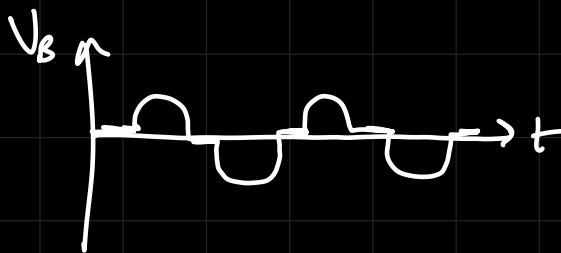

CLASS AB amplifier

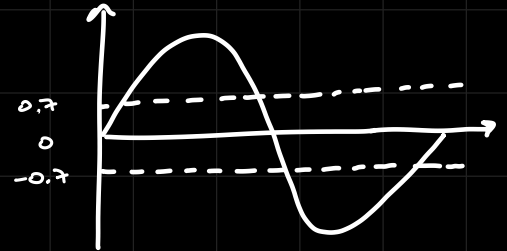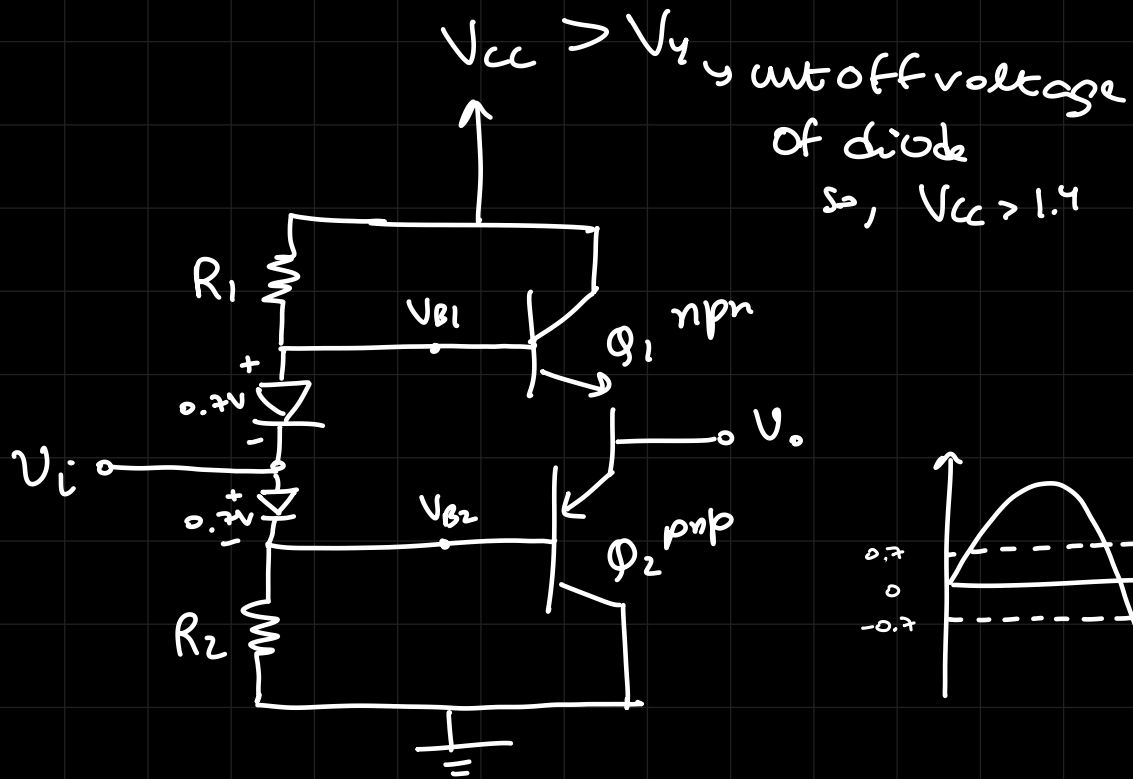


CLASS C Amplifier

will be discussed in Friday's TUTOR

CMOSFET

complementary MOSFET

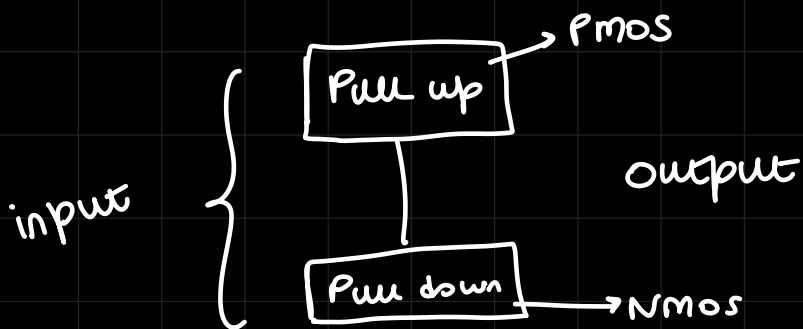


$$\lim_{x \rightarrow 8} \frac{1}{x-8} = \infty$$

$$\lim_{x \rightarrow 5} \frac{1}{x-5} = \text{L-shaped curve}$$

from fig 12.14

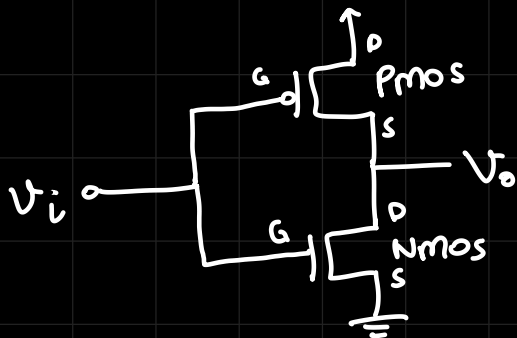with circle \rightarrow PMOS
w/o circle \rightarrow NMOS } no need for arrow



$$V_i = V_{max}$$

INVERTER


\equiv NOT Gate

Shunt operation


for p channel: PMOS $\rightarrow V_{GS}$: negative $V_{GS} < -V_{th}$
 n channel: NMOS $\rightarrow V_{GS}$: positive $V_{GS} > V_{th}$

for $V_i = \text{HIGH}$

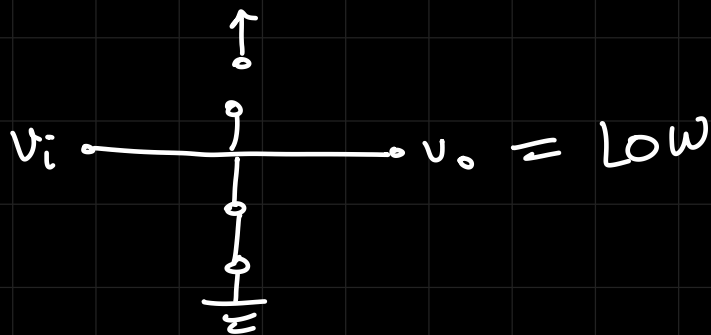$M_1 \rightarrow \text{OFF}, M_2 \rightarrow \text{ON}$




for $V_i = \text{LOW} \rightarrow$

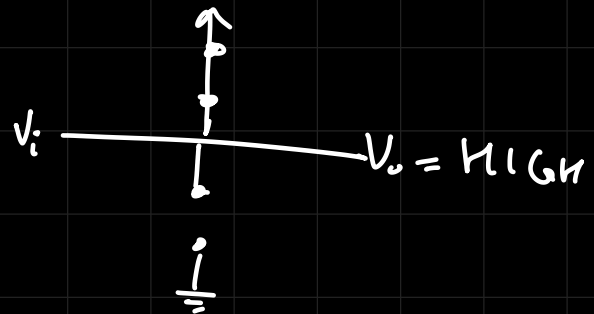

OR gate parallel

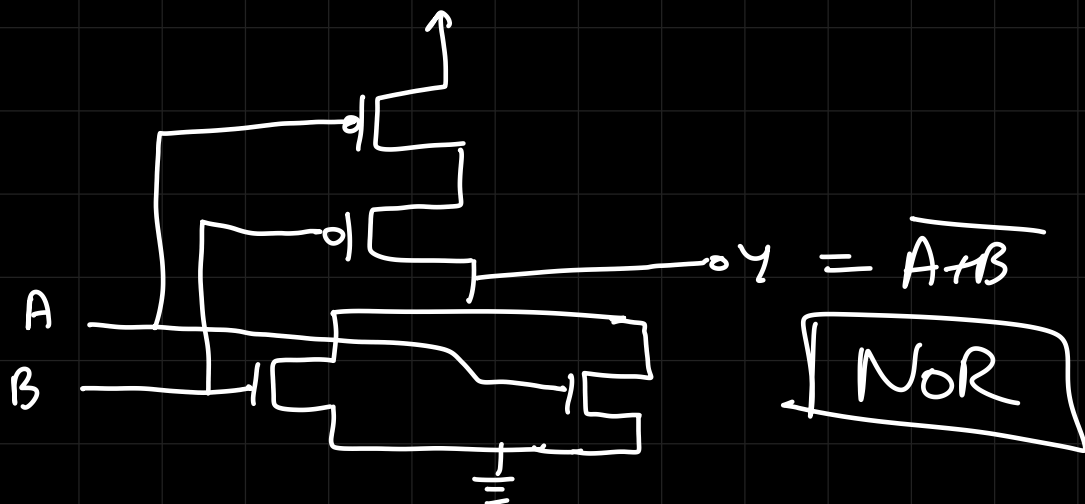if pull down: parallel
 \hookrightarrow pull up: series



AND Gate series

