

$$E_{\text{incident}} = E_0 e^{-ikz}$$

$$E_{\text{reflected}} = \Gamma_0 E_0 e^{ikz}$$

if Γ_0 is negative then \vec{E} has changed the direction

$$\Gamma_0 = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1} \quad \eta_1 = \left(\frac{\mu_1}{\epsilon_1}\right)^{1/2}, \quad \eta_2 = \left(\frac{\mu_2}{\epsilon_2}\right)^{1/2}$$

for non magnetic media

$$\eta_1 = \sqrt{\frac{\mu_0}{\epsilon_1}}, \quad \eta_2 = \sqrt{\frac{\mu_0}{\epsilon_2}}$$


$$\Gamma_0 = \frac{\sqrt{\mu_0/\epsilon_1} - \sqrt{\mu_0/\epsilon_2}}{\sqrt{\mu_0/\epsilon_1} + \sqrt{\mu_0/\epsilon_2}} = \frac{\sqrt{\epsilon_1} - \sqrt{\epsilon_2}}{\sqrt{\epsilon_1} + \sqrt{\epsilon_2}}$$

$$\frac{\sqrt{\epsilon_{r1}} - \sqrt{\epsilon_{r2}}}{\sqrt{\epsilon_{r1}} + \sqrt{\epsilon_{r2}}} \longleftarrow = \frac{\sqrt{\epsilon_0 \epsilon_{r1}} - \sqrt{\epsilon_0 \epsilon_{r2}}}{\sqrt{\epsilon_0 \epsilon_{r1}} + \sqrt{\epsilon_0 \epsilon_{r2}}}$$

$$\downarrow$$

$$\boxed{\frac{n_1 - n_2}{n_1 + n_2}}$$

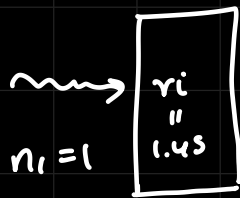↪ these n are not η (eta)
this is refractive index



for non magnetic material


$$\Gamma_o = \frac{n_1 - n_2}{n_1 + n_2} = -ve$$

and so, $\vec{E}_r = \text{opposite to } \vec{E}_i$

Initial KVL/KCL problem


Wavelength for $f_{eq} = 50 \text{ kHz} \rightarrow \frac{3 \times 10^8}{50} = 6 \times 10^8 \text{ cm}$

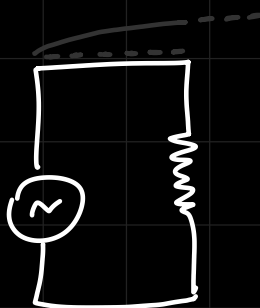Since wavelength is very big, we can assume for a very small circuit that voltage remains constant along a $R=0$ line



but for very long ckt,
we cannot assume:

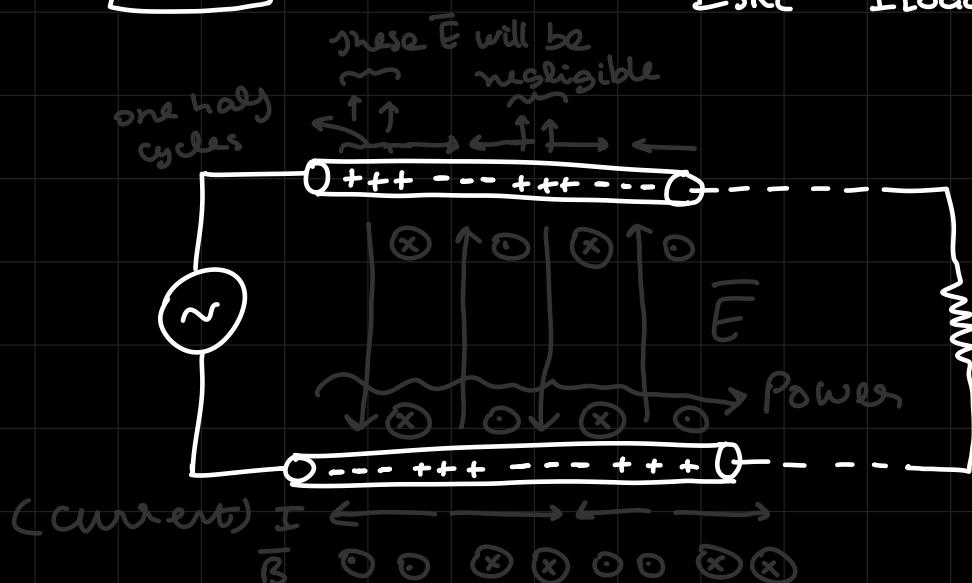
$$\left. \begin{array}{l} V_{src} = V_{load} \\ I_{src} = I_{load} \end{array} \right\} \times$$



$\vec{E} \times \vec{H}$ is almost zero outside the circuit because of \vec{E}

$(\vec{E} \times \vec{H})$ Power is held / concentrated within the 2 conductors and being guided from SRC \rightarrow Load at all points because both \vec{E} and \vec{H} switch directions together.

Guided wave propagation

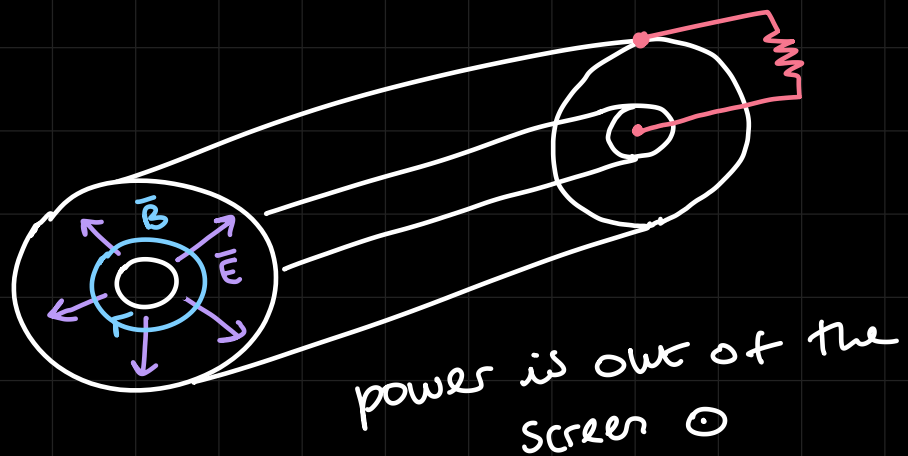


ERROR POSSIBLE: These conductors might not remain as PEC at higher frequency


Distributed Resistance
(not lump resistance x)
throughout the conductors
because not PEC

Assume that distributed resistance
per unit length as $R_s (\Omega/m)$

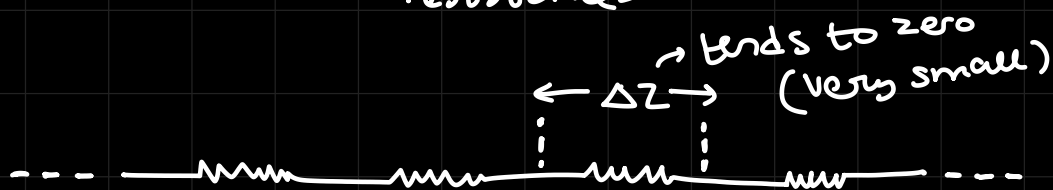
↓ ↪ not just r because distributed
series
resistances




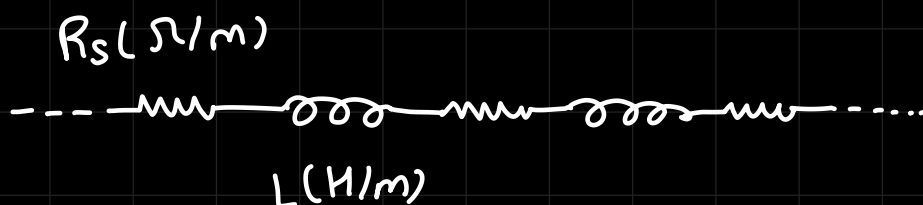
along with this we have inductance
as well because of the \vec{B}



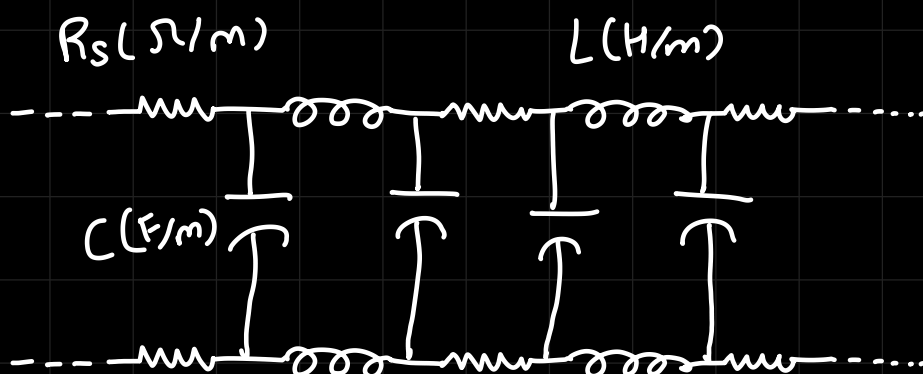additionally, we also have distributed
capacitance due to the \vec{E}



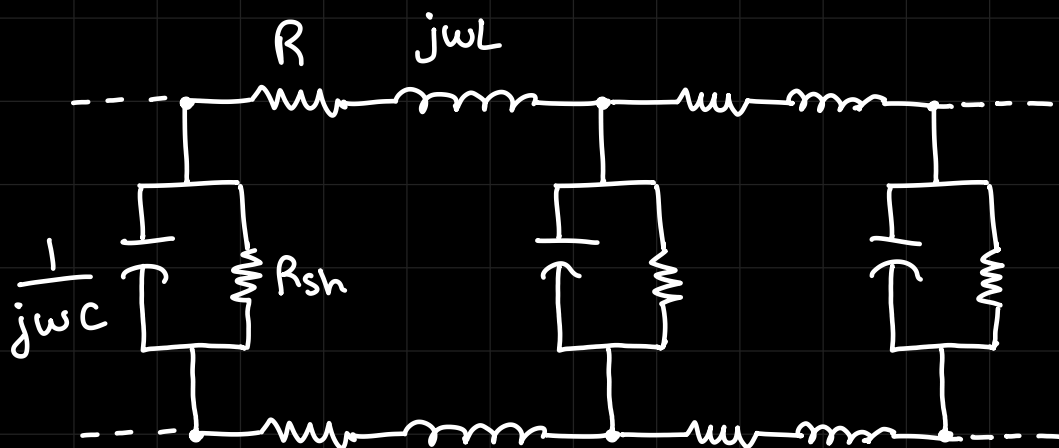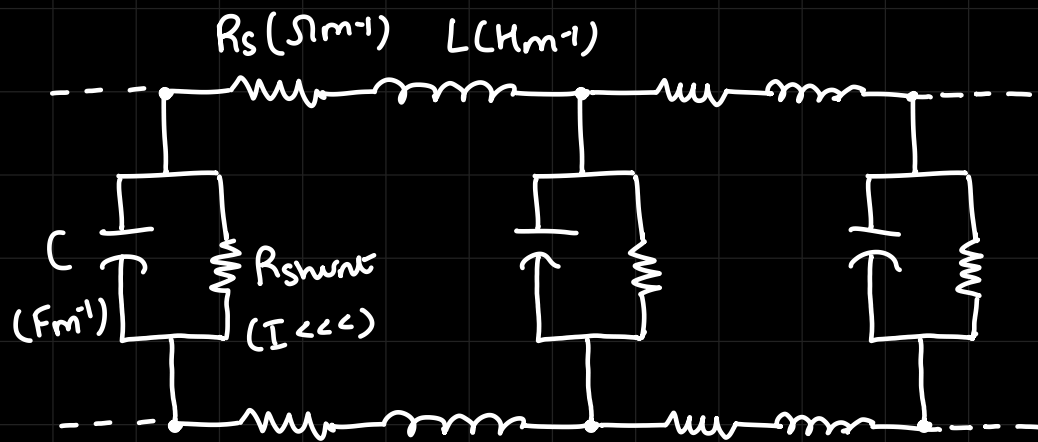lastly, we have σ very small between the two conductors so that means very high resistance between them (dielectric medium)
(leakage current)




← $\Delta Z \rightarrow 0$ →

<fig1>

let $X = R + j\omega L$
(admittance) $Y = j\omega C + \frac{1}{R_{sh}} = (G + j\omega C)$
↳ very less
because $R_{sh} \gg$

Since we have all these non-idealities, there must be some voltage drop and hence KVL/KCL would fail without considering these factors.

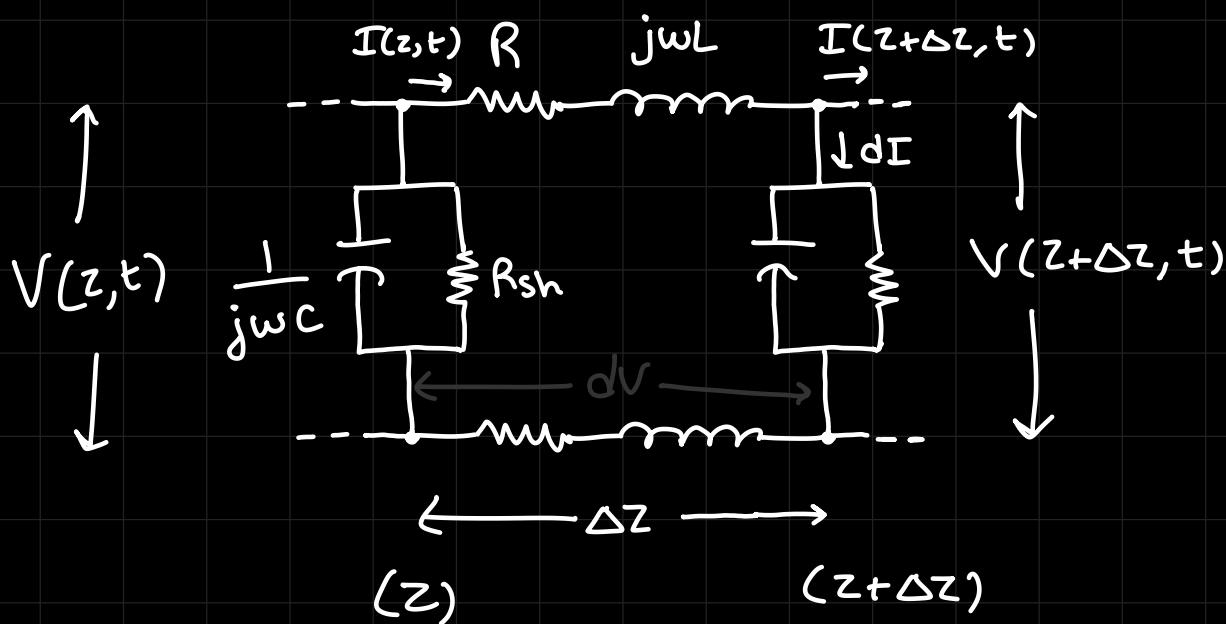KCL/KVL fails for macroscopic circuitry but still work for <fig1> because $\Delta z \rightarrow 0$ (because distance very small)



$$V(z,t) - I(z,t)[R + j\omega L]\Delta z - V(z+\Delta z,t) = 0$$

$\underbrace{\hspace{1.5cm}}$
 because R and L
 are per unit values

$$-I(z,t) \times \Delta z = V(z+\Delta z,t) - V(z,t)$$

$$\frac{V(z+\Delta z,t) - V(z,t)}{\Delta z} = -X I(z,t)$$

$$\lim_{\Delta z \rightarrow 0} \rightarrow$$

$$\frac{\partial V}{\partial z} = -XI(z,t)$$

What about the current?

$$I(z,t) = I(z+\Delta z,t) + dI$$

$$I(z+\Delta z,t) - I(z,t) = -dI$$

$$I(z+\Delta z,t) - I(z,t) = -VY\Delta z$$

$$\frac{\partial I}{\partial z} = -VY$$

now we find the wave equation
(requires 2nd derivation)

$$\frac{\partial^2 V}{\partial z^2} = -X \frac{\partial I}{\partial z} = -X(-VY) = V \cdot XY$$

note: $X = R + j\omega L$
 $Y = G + j\omega C$ } complex nums

$$\frac{\partial^2 V}{\partial z^2} - \gamma^2 V = 0$$

(helmholtz eqⁿ)

where $\gamma = \sqrt{XY}$

$$\gamma = \left((R + j\omega L)(G + j\omega C) \right)^{1/2}$$


$$\gamma = \alpha + j\beta$$

general solⁿ:

$$V = V_+ e^{-\gamma z} + V_- e^{\gamma z}$$

$$V = V_+ e^{-\alpha z} e^{-j\beta z} + V_- e^{\alpha z} e^{j\beta z}$$
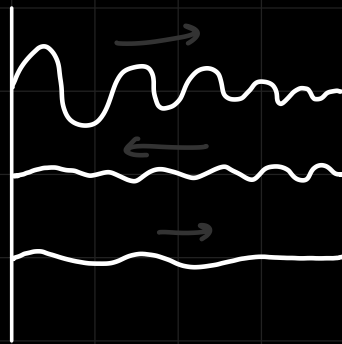
$$V(z, t) = V_+ e^{-\alpha z} e^{j(\omega t - \beta)z} + V_- e^{\alpha z} e^{j(\omega t + \beta)z}$$



continuous transmission
and reflection

Now, when will have lossless transmission
i.e. no attenuation in signal?

when $e^{-\alpha z}$ and $e^{\alpha z} = 0$

↳ $\alpha = 0$ i.e. $\gamma =$ purely complex

so, $R = 0$ and $G = 0$

↳ series resistance = 0

↳ leakage current = 0 ($R_{\text{shunt}} \uparrow \uparrow$)

so, $\gamma = j\beta = j\omega\sqrt{LC} \rightarrow \underline{\beta = \omega\sqrt{LC}}$

$$\text{wavelength} : \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{LC}} = \frac{1}{f \sqrt{LC}}$$

and velocity \rightarrow

$$v = \frac{1}{\sqrt{LC}}$$




this is of the
guided wave

quiz 3 and quiz 4 syllabus some
(open book) (closed book)

quiz 5 and quiz 6 syllabus : till today
(open book) (closed book)
30 mins 30 mins

PROJECT

{ finite difference method }

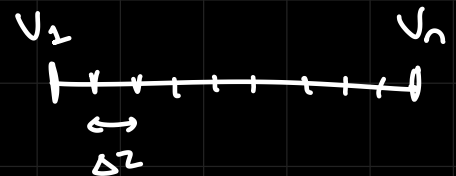

$$\frac{v_{i+1} - v_i}{\Delta z}$$

forward difference

$$\frac{v_i - v_{i-1}}{\Delta z}$$

backward difference

central difference (best)