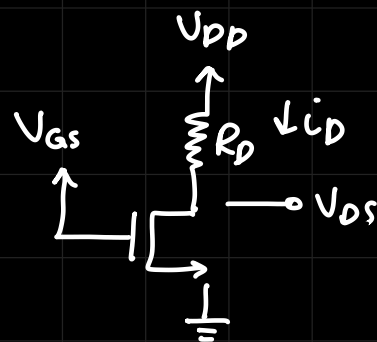


MOSFET Amplifier Biasing

→ Establish I_D through biasing

↳ DC operating point for a given V_{GS}

so that the amp provides adequate gain and undistorted output swing for input transitions



slope $\rightarrow -\frac{1}{R_D}$


$$V_{DS} = V_{DD} - I_D R_D$$

$$I_D = \frac{V_{DD} - V_{DS}}{R_D}$$


Input-output characteristics

Q point in Voltage Transfer characteristics, (V_{DS}, V_{GS})

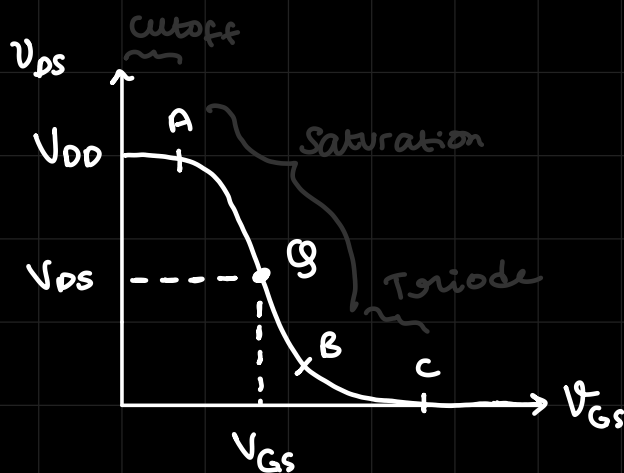Q point in $I_D - V_{GS}$ curve $\rightarrow (I_D, V_{DS})$




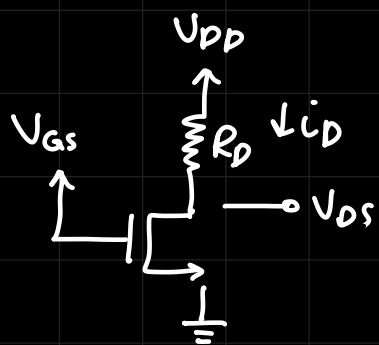if Q was further down, towards B, the output will have non linear distortions because the Amp goes into triode mode. (when input signal swing is high)



What value of R_D to choose?

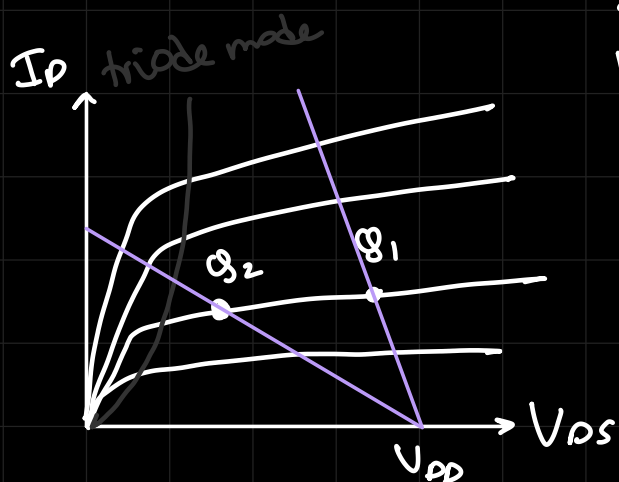① Suppose we choose $R_D = R_{D2}$ so that the we enter Q point at Q_2 for V_{GS}




but negative transients of the input signal might make the amp go into triode mode (not ideal)

for Q point = Q_1 , we are very close to V_{DD} and the amplifier might go to cutoff mode for large -ve transients of input signal (distorted output)

We need R_D to be such that Q point is between the above 2 extreme points

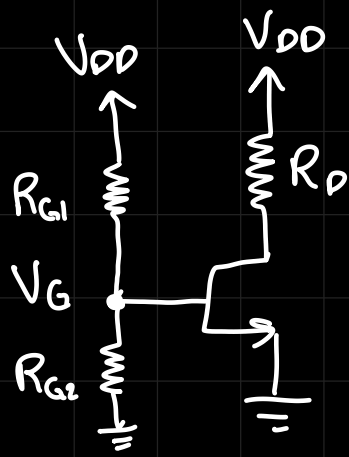R_D should be such that for a given V_{GS} the Q point is well within the saturation point



① Since $I_G = 0$ always we can keep higher values of R_{G1} and R_{G2} and hence high input impedance so it helps us capture the entire info in the input signal

②

R_{G1} and R_{G2} should be high but keep in mind $V_G > V_T$ for saturation.

also $V_D > V_G - V_T$

③ If I fix the value of V_G , my ckt is still not stable to variations in device parameters or temperature variation

→ We need a feedback mechanism and for this, an R_S resistance is placed at the source


$$\text{if } i_D \uparrow \rightarrow V_G = V_{GS} + I_D R_S$$

$$\downarrow \quad V_{GS} = V_G - I_D R_S$$

$$V_{GS} \downarrow$$

$$\rightarrow i_D \downarrow$$
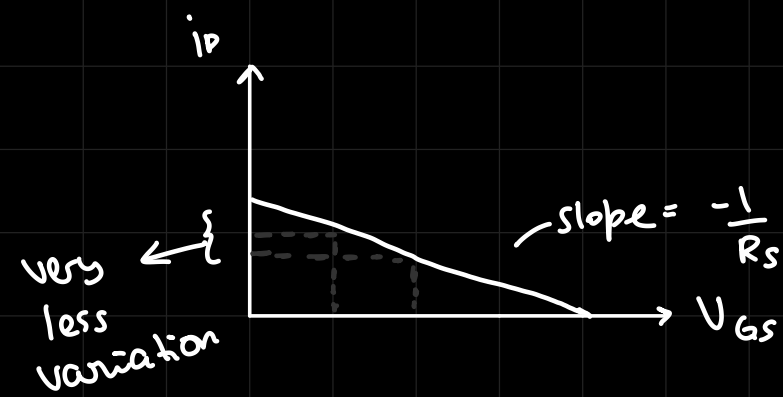
$$\text{if } i_D \downarrow \rightarrow V_{GS} \uparrow \rightarrow i_D \uparrow \quad (\text{feedback})$$




slope should be lower $\rightarrow R_S$ should be \uparrow
but not $\rightarrow \infty$

SUMMARY :

- ① R_D : should be high provided the cutoff region is avoided
- ② R_{G1}, R_{G2} : should be high such that MOSFET operates in the saturation region
- ③ R_S : should also be very high to avoid fluctuations in i_D

eg3

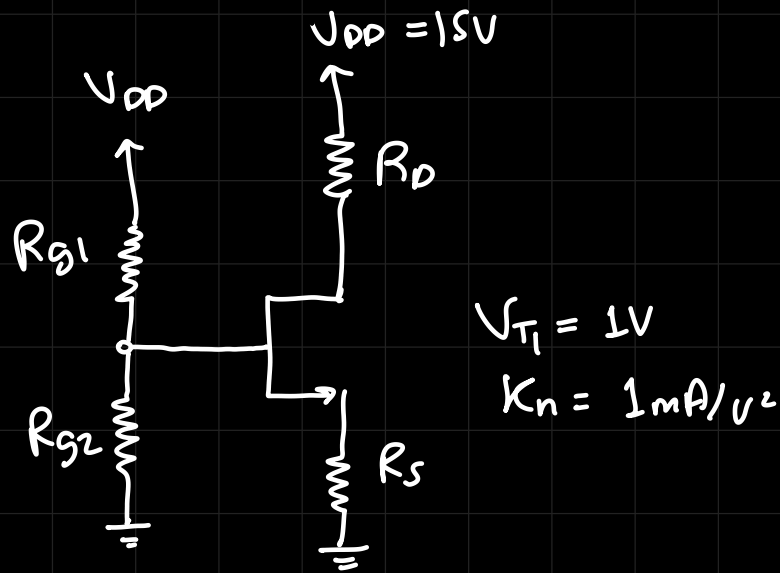

- Q) calculate the change in I_D if m_{os} is changed with device with same k_n but different $V_{T2} = 1.5V$

Rule of thumb: We choose the R_D and R_S voltage drop as $1/3^{rd}$ of the supply voltage

Ans) $V_D = V_{DD} - \frac{V_{DD}}{3} = 1.5 - 0.5 = \underline{1.0V}$

$$V_S = V_{DD} - \frac{V_{DD}}{3} - \frac{V_{DD}}{3} = 0.5V$$

Saturation $\rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$

$$1 = (V_{GS} - 1)^2$$

$$V_{GS} = 2V$$

$$V_G = V_{GS} + V_S = \underline{2.5V}$$

$$V_{DS} = 5V \quad V_{GS} - V_T = 1V$$

$$V_{DS} > V_{GS} - V_T \quad \checkmark$$

$$V_G = \frac{R_2}{R_1 + R_2} \times 15$$

$$7R_1 + 7R_2 = 15R_2$$

$$7R_1 = 8R_2$$

if i assume $R_1 = 8m\Omega \rightarrow R_2 = 7m\Omega$


$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5}{0.5m} = \underline{10k\Omega}$$

$$R_S = \frac{V_S}{I_D} = \frac{5}{0.5m} = 10k\Omega$$

all resistors found

→ at $V_T = 1.5V$

V_{GS} and I_D will change

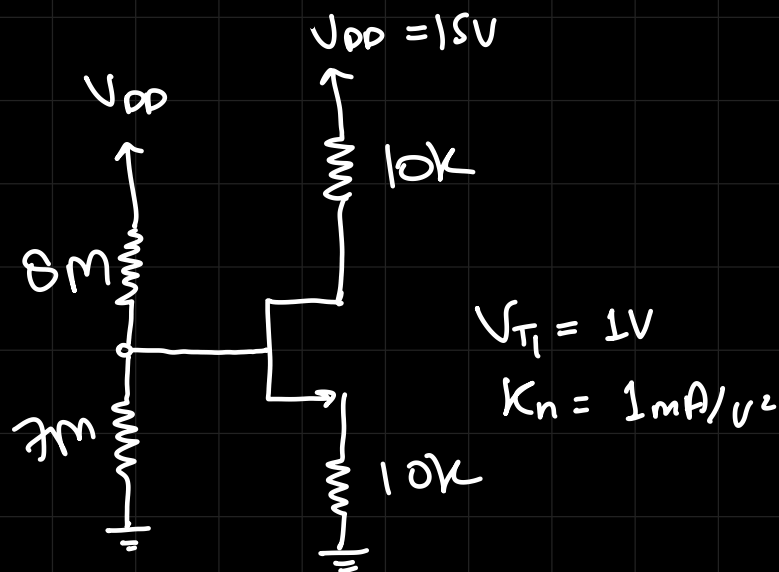

$$-15 + 10K I_D + V_{DS} + 10K I_D = 0$$

$$I_D = \frac{15 - V_{DS}}{20K}$$

$$V_G = V_{GS} + V_S = V_{GS} + I_D R_S$$

$$V_{GS} + 10K I_D = 7$$


$$I_D = \frac{1}{2} (5.5 - 10K I_D)^2$$

$$2I_D = 30.25 + 100M I_D^2 - 110K I_D$$

$$I_{D2} = 0.5mA, I_{D1} =$$

note: $K_n = \mu_n C_{ox}$


Current mirror circuit

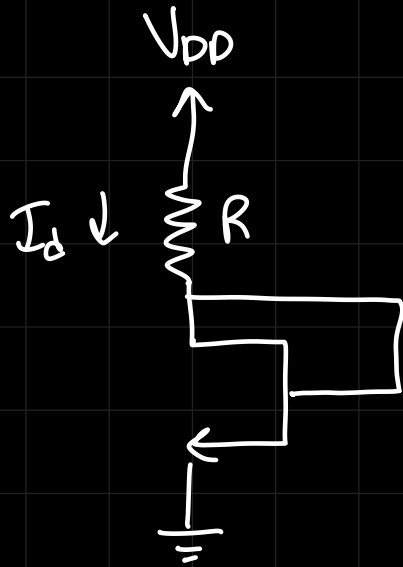

We know,
 $V_D = V_G$
 $V_G > V_T$ w/c
 $V_D > V_G - V_T$
always in
saturation mode

$$I_D = K (V_{GS} - V_T)^2$$

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_T$$

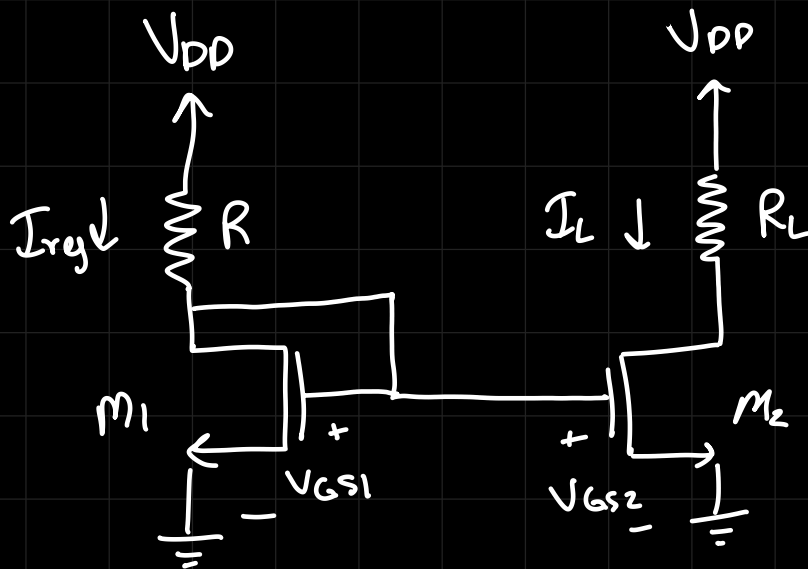

if $V_{T1} = V_{T2}$ and M_1, M_2 have
same characteristics

$$I_L = k(V_{GS2} - V_T)^2$$

$$I_{ref} = K(V_{GS1} - V_T)^2$$

Since both gate terminals are shorted
 $V_{GS1} = V_{GS2}$

So, $I_{ref} = I_L$ only if R_L is
such that M_2 remains in saturation

8th march → Tut simulation