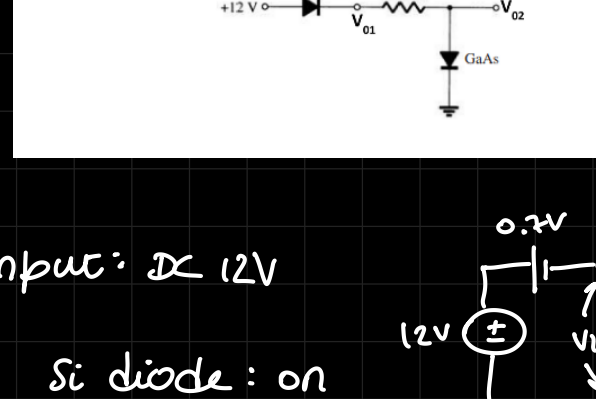


Tutorial 3

g5)




also calculate the series current of the circuit

input: DC 12V

Si diode: on

GaAs diode: on

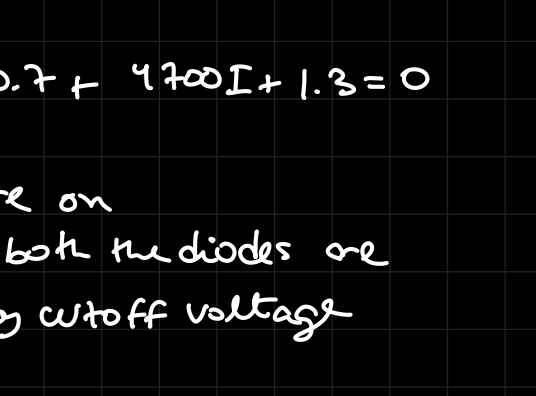

$$-12 + 0.7 + 4700I + 1.3 = 0$$

both the diodes are on
it means that both the diodes are replaced by cutoff voltage


$$I = \frac{10}{4.7} \text{ mA} = 2.12 \text{ mA}$$

$$V_2 = 1.3 \text{ V}$$

$$-12 + 0.7 + V_0 = 0$$

$$V_1 = 11.3 \text{ V}$$


g6)

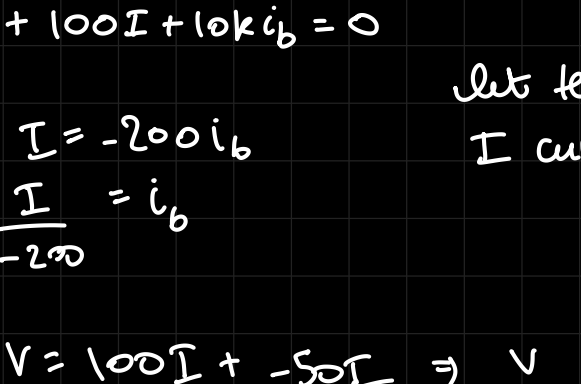

Theremin Equivalent

but dependent src

so, add a test voltage source of V

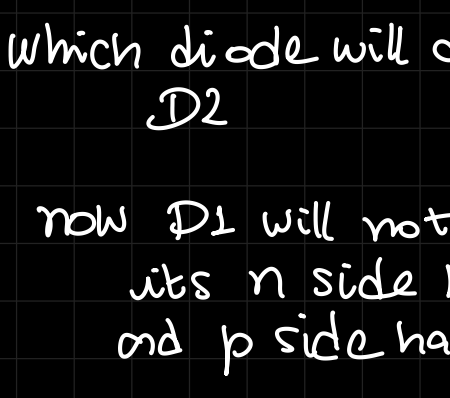

no independent source is present in the network. so, we apply a test src across terminal 1 and 2 either a current or voltage src

$$10k i_b + 100I + 100k i_b = 0$$

$$-V + 100I + 100k i_b = 0$$

$$I = -200 i_b$$


$$\frac{I}{-200} = i_b$$

$$V = 100I + -50I \Rightarrow \frac{V}{I} = Z_{th} = 50\Omega$$

test test src \rightarrow V vol

I current

g7)

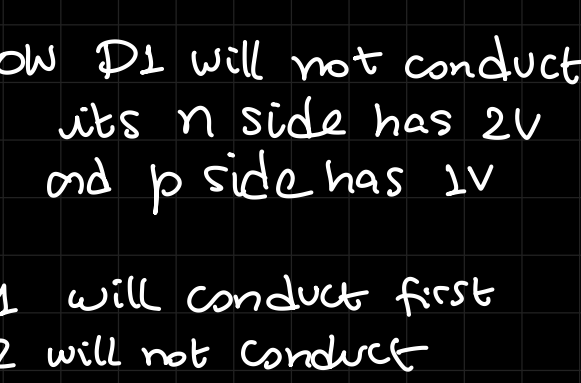

(a) Which diode will conduct first?

D2

now D1 will not conduct because its n side has 2V and p side has 1V

(b) D1 will conduct first

D2 will not conduct

in reverse bias, the lesser potential one will conduct

Rectifier: AC \rightarrow pulsating DC

AC: varies with time : bidirection \pm

DC: const with time : unidirection $+/-$

Rectifier

\hookrightarrow Half wave

\hookrightarrow Full wave


\hookrightarrow Centre Tap

\hookrightarrow Bridge

\hookrightarrow Better

Transformer doesn't work with DC
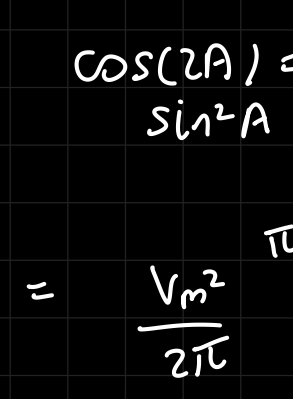
$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$




transformer

\hookrightarrow step up

\hookrightarrow step down

generally, used for power transformation

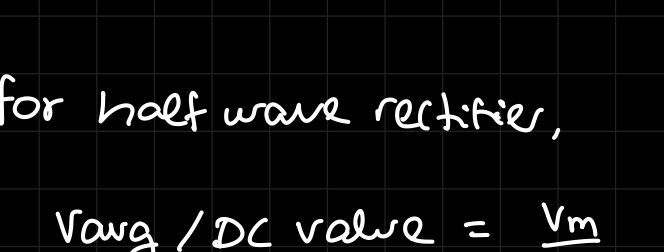

AC

$V = V_m \sin \omega t$

$V = V_m \sin \omega t$

pulse repetition time:

originally: 2π

rectified: π

pos half cycle \rightarrow D2, D4 on

neg half cycle \rightarrow D1, D3 on

$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin \omega t \, d\omega t$$

$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} \left[-\cos \omega t \, d\omega t \right]$$

$$= \frac{2V_m}{\pi}$$

$$V_{rms} = \frac{1}{T} \int_0^T V_o^2(t) \, d\omega t$$

$$= \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2(\omega t) \, d\omega t$$

$$= \frac{V_m^2}{2\pi} \int_0^{\pi} (1 - \cos(2\omega t)) \, d\omega t$$

$$\cos(2A) = 1 - 2\sin^2 A$$

$$\sin^2 A = \frac{1 - \cos(2A)}{2}$$

$$= \frac{V_m^2}{2\pi} \left[\omega t - \sin\left(\frac{2\omega t}{2}\right) \right]$$

$$= \frac{V_m^2}{2\pi} (\pi + 0 + 0 + 0)$$

$$= \frac{V_m^2}{2}$$

for half wave rectifier,


$$V_{avg} / \text{DC value} = \frac{V_m}{\pi}$$

$$\text{and RMS value: } V_{rms} = \frac{V_m}{2}$$

NOTE: for full wave bridge rectifier, two diodes conduct at a time. That's why we always consider two cutoff voltages

And for center tapped rectifier, only one diode conducts at a time

g1)

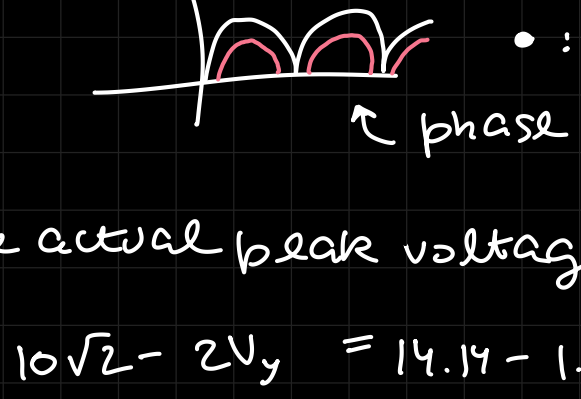

$$N_1 = 12$$


$$N_2 = 1$$

$$\frac{V_2}{V_1} = \frac{1}{12} \Rightarrow V_2 = \frac{120}{12} = 10 \text{ V}_{rms} \text{ 60Hz}$$

$$R_L = 1000\Omega \quad V_{peak} = 10\sqrt{2} = 14.14 \text{ V}$$

The given bridge rectifier is Si based

$$V_f = 0.7 \text{ V}$$

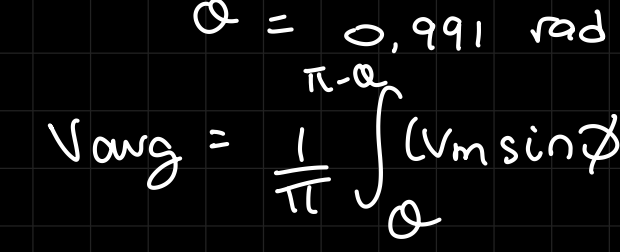

$$V_L = \frac{N_2}{N_1} \times V_1 = \frac{1}{12} \times 120 \text{ V}_{rms} = 10 \text{ V}_{rms}$$

$$= 14.14 \text{ V}$$

14.14 \rightarrow This result is for ideal analysis

ideal non-ideal

V_o

$w = \sim 0.5 \mu\text{m}$

\bullet : non ideal

\bullet : ideal

\hookrightarrow phase angle diff?

So, the actual peak voltage is

$$V_o = 10\sqrt{2} - 2V_f = 14.14 - 1.4 = 12.74 \text{ V}$$

$V_{gamma} = V_{msthold}$ of diode

this would have been correct if it was an ideal diode case

$$V_{avg} = \frac{2V_o}{\pi} = \frac{2 \times 12.74}{3.14} = 8.11 \text{ V}$$

$$V_{rms} = \frac{V_o}{\sqrt{2}} = \frac{12.74}{\sqrt{2}} \approx 9 \text{ V}$$

$$V_{avg} / \text{non-ideal} = \frac{1}{\pi} \int_0^{\pi} (V_m \sin \phi - 2V_f) \, d\phi$$

$$\phi = \sin^{-1} \left[\frac{2V_f}{V_m \sqrt{2}} \right] = \sin^{-1} \left[\frac{1.4}{10\sqrt{2}} \right]$$

$$\phi = 0.991 \text{ rad}$$

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} (V_m \sin \phi - 2V_f) \, d\phi$$

$$J_{ac} = J_f = \eta \frac{V_T}{I_L}$$

ZENER DIODE

$$\text{depletion width: } W = \sqrt{\frac{2\epsilon}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) (V_o - V)}$$

$$E = \frac{|V_o|}{W}$$

excess holes

p

trivalent impurity

n

pentavalent impurity

excess e^-

acceptor ion N_A

donor ion N_D

$$V_o = \frac{kT}{q} \ln \frac{N_A N_D}{n_i^2}$$

n_i : intrinsic ion

N_A : acceptor ion

N_D : donor ion

highly doped PN junction diode reverse biased