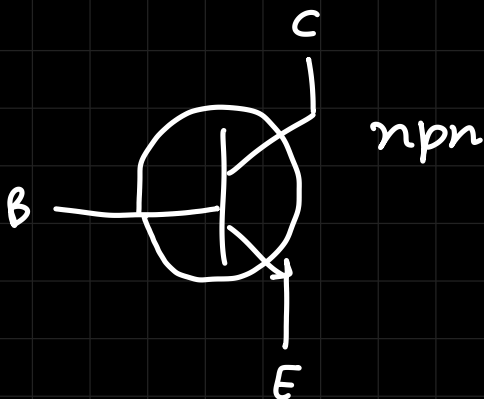


BJT (Revision)

controlling current on one terminal by varying voltage on two terminals




Application:

Amplifier → only in active mode

Switch → saturation and cutoff mode

for NPN BJT →

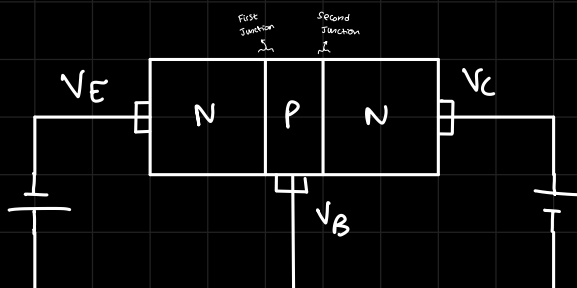

not exactly but
can be related with
 \approx

Active mode: $V_E < V_B$ and $V_B < V_C$

Cutoff mode: $V_E > V_B$ and $V_B < V_C$

Saturation mode: $V_E < V_B$ and $V_B > V_C$

$$I_C = I_S e^{V_{BE}/V_T}$$

$$\beta = \frac{I_C}{I_B}, \quad \alpha = \frac{I_C}{I_E}$$

$$I_{SE} = \frac{I_S}{\alpha} \quad \text{= saturation current of the emitter region}$$

Lecture (~Tutorials)

BJT → why bipolar?

because current is flowing through majority and minority charge carriers.


In BJT, we have 2 junctions

↳ emitter-base junction


↳ collector-base junction

EBJ	CBJ	Mode	Application
FB	RB	Active	Amplifier
RB	RB	Cutoff	off-switch
FB	FB	Saturation	On-Switch
RB	FB	Inverted	NB! used generally (comp but with very low gain)

Active mode npn →

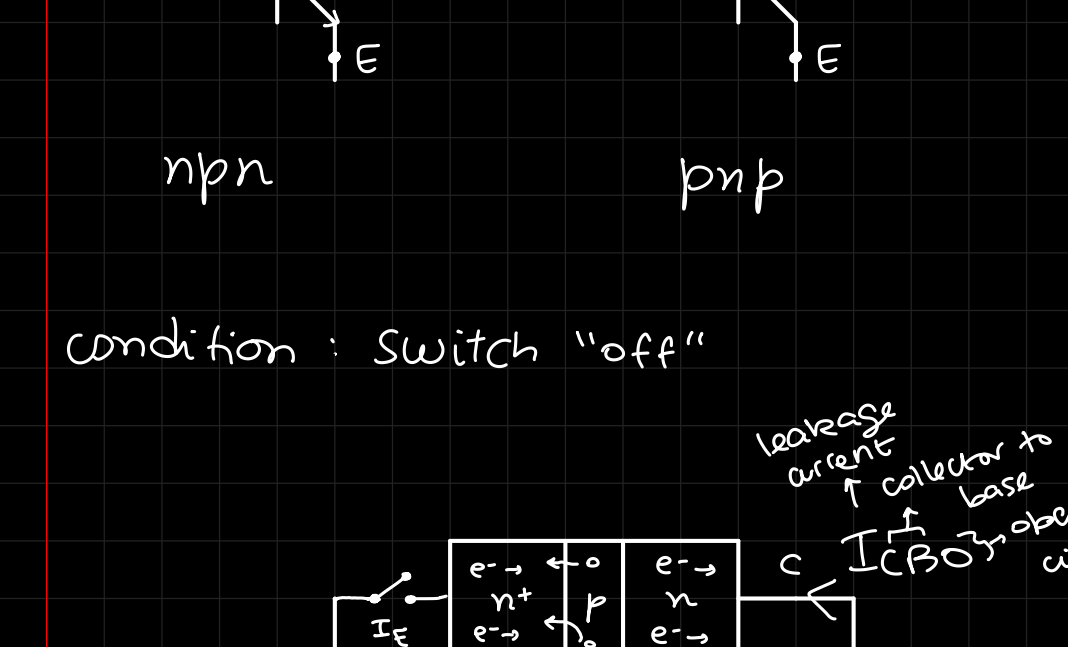

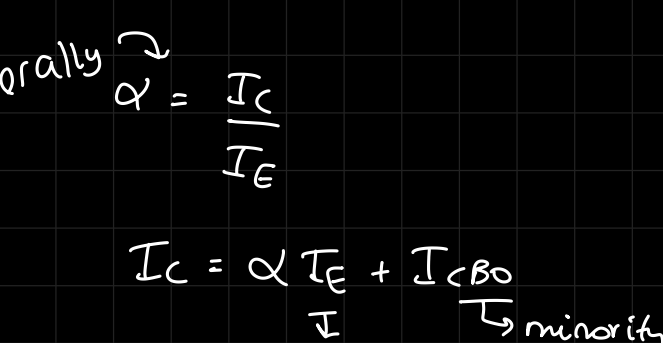
Area(C) ~ 50%
Area(B) ~ 10%
Area(E) ~ 40% } General idea (not actually precise)



npn

pnp

condition: Switch "off"

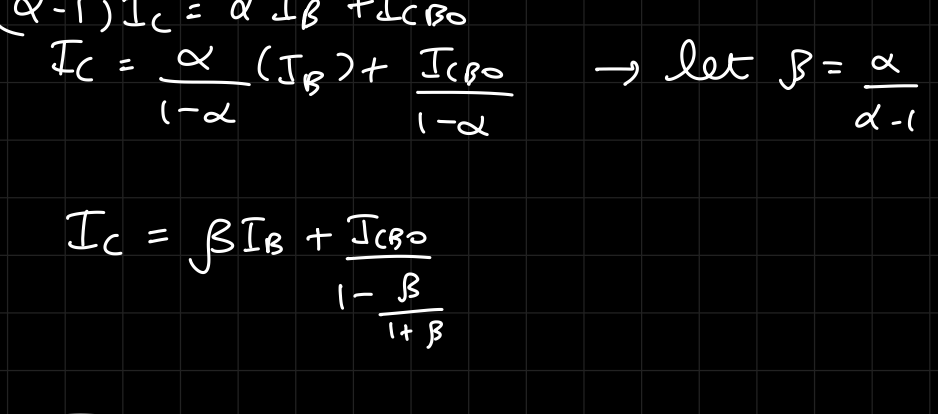

This is common base configuration

Generally $\alpha = \frac{I_C}{I_E}$

$$I_C = \alpha I_E + I_{CBO}$$

I_{CBO} minority

$$I_E = I_B + I_C$$


$$I_C = \alpha I_B + \alpha I_C + I_{CBO}$$

$$(\alpha - 1)I_C = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1-\alpha} (I_B) + \frac{I_{CBO}}{1-\alpha} \rightarrow \text{let } \beta = \frac{\alpha}{\alpha-1}$$

$$I_C = \beta I_B + \frac{I_{CBO}}{1-\frac{\beta}{1+\beta}}$$

$$I_C = \beta I_B + (1+\beta) I_{CBO}$$

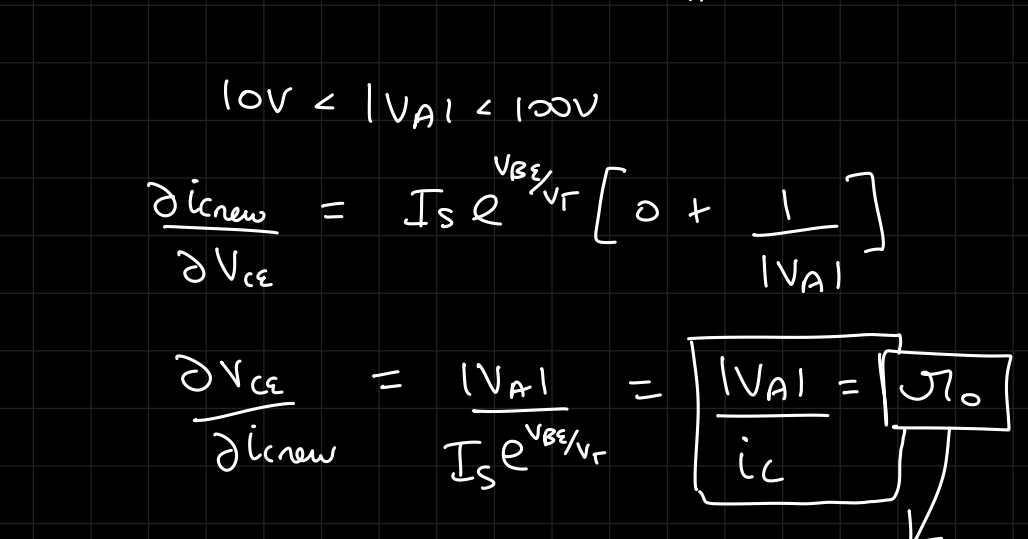

for active mode →

EBJ: FB


CBJ: RB

Depletion layer decreases in CBJ

Base width modulation ↓

V_{BE} fixed
 $V_{CE} \uparrow$ ✓
depletion layer ↑
Collector region overlaps overall base width ↓
 $I_C \uparrow$

Early effect

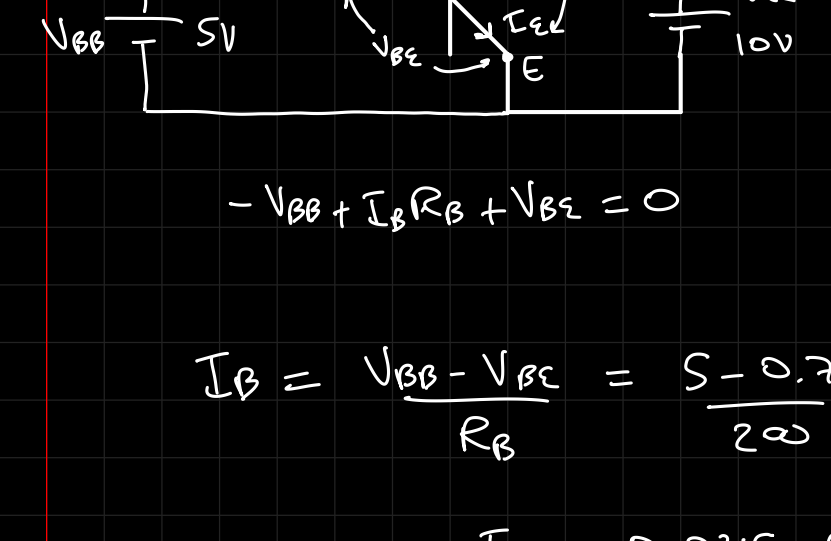

$$i_C = I_S e^{\frac{V_{BE}}{V_T}} \quad \# V_T = 25 \text{ mV for room temp}$$

$$i_{C_{new}} = I_S e^{\frac{V_{BE}}{V_T}} \left[1 + \frac{V_{CE}}{|V_A|} \right]$$

$$10V < |V_A| < 100V$$

$$\frac{\partial i_{C_{new}}}{\partial V_{CE}} = I_S e^{\frac{V_{BE}}{V_T}} \left[0 + \frac{1}{|V_A|} \right]$$

$$\frac{\partial V_{CE}}{\partial i_{C_{new}}} = \frac{|V_A|}{I_S e^{\frac{V_{BE}}{V_T}}} = \frac{|V_A|}{I_C} = r_o$$

$$\# I_C = \beta I_B$$


NUMERICAL

Q1) for a given transistor, check whether the transistor works in active or cutoff mode?

Assume that transistor is Si based

→ Active: EBJ: FB, CBJ: RB
Cutoff: EBJ: RB, CBJ: RB

Assume $\beta = 100$

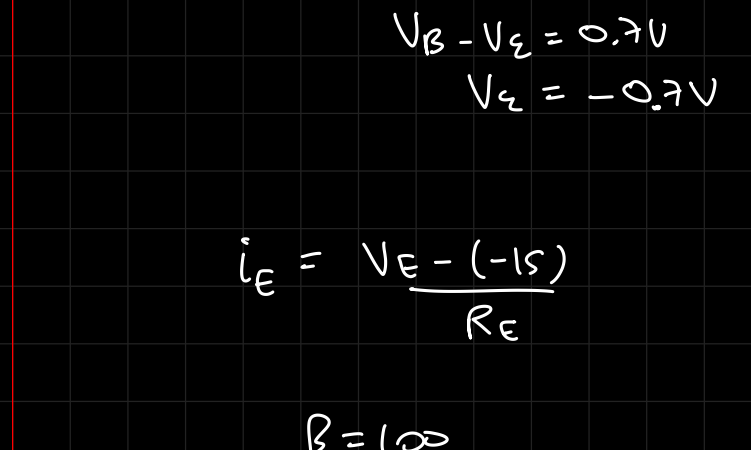

$$-V_{BE} + I_B R_B + V_{BE} = 0$$

$$I_B = \frac{V_{BE} - V_{BE}}{R_B} = \frac{5 - 0.7}{200} \text{ mA}$$

$$I_B = 0.025 \text{ mA}$$

$V_{BE} \rightarrow$ replaced by cutoff voltage here $V_{BE} = 0.7 \text{ V}$

$$\text{and } V_{CE} = 0.2 \text{ V to } 0.3 \text{ V}$$

$$I_C = \beta I_B = 2.5 \text{ mA}$$

in 2nd loop:

$$-3k I_C + 10 - V_{CE} = 0$$

$$V_{CE} = 10 - 3 \times 10^3 \times 2.5 \times 10^{-3} = 2.5 \text{ V} \gg V_{BE}$$

(Active mode)

(ii) $R_B = 50k\Omega$

$$I_B = \frac{V_{BE} - V_{BE}}{R_B} = \frac{5 - 0.7}{50} \times \text{mA}$$

$$= 0.086 \text{ mA}$$

$$I_C = \beta I_B = 8.6 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = 10 - 8.6 \times 3 = -15.8 \text{ V} \ll V_{BE} (0.7 \text{ V})$$

saturation mode

Q2) The transistor shown has $\beta = 100$ and exhibits a V_{BE} of 0.7 V and $i_C = 2 \text{ mA}$. Design the circuit so that current of 1 mA flows through the collector and a voltage of $+5 \text{ V}$ appear at the collector.

$$\rightarrow i_B = \frac{i_C}{\beta} = 10 \mu\text{A}$$

$$i_C = \frac{15 - V_C}{R_C}$$

$$R_C = \frac{15 - V_C}{i_C}$$

$V_C = 5 \text{ V}$ given

$$V_{BE} = 0.7 \text{ V} = V_B - V_E$$

$$V_B - V_E = 0.7 \text{ V}$$

$$V_E = -0.7 \text{ V}$$

$$R_C = \frac{15 - 5}{2} \text{ k}\Omega = 5 \text{ k}\Omega$$

$$i_E = \frac{V_E - (-15)}{R_E}$$

$$\beta = 100$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{101} = 0.99$$

$$\alpha = \frac{i_C}{i_E} \Rightarrow i_E = \frac{i_C}{\alpha} = \frac{2}{0.99} \text{ mA}$$

$$= 2.02 \text{ mA}$$

$$R_E = \frac{V_E + 15}{i_E}$$

$$= \frac{-0.7 + 15}{2.02} \text{ k}\Omega = 7.079 \text{ k}\Omega$$

$$i_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$i_{C2} = I_S e^{\frac{V_{BE2}}{V_T}}$$

$$\frac{i_{C1}}{i_{C2}} = e^{\frac{V_{BE1} - V_{BE2}}{V_T}}$$

$$\log_e(0.5) = \frac{V_{BE1} - V_{BE2}}{V_T}$$

$$\ln\left(\frac{1}{2}\right) = \frac{V_{BE1} - 0.7}{V_T}$$

$$V_{BE2} = -0.7 - \ln(0.5) V_T$$


$$= -0.7 - (-0.693 \times 25 \times 10^{-3})$$

$$= 0.717 \text{ V} \times 0.683 \text{ V}$$

Q3) $V_E = -0.7 \text{ V}$

$\beta = 50$

$i_E, i_B, i_C, V_C = ?$

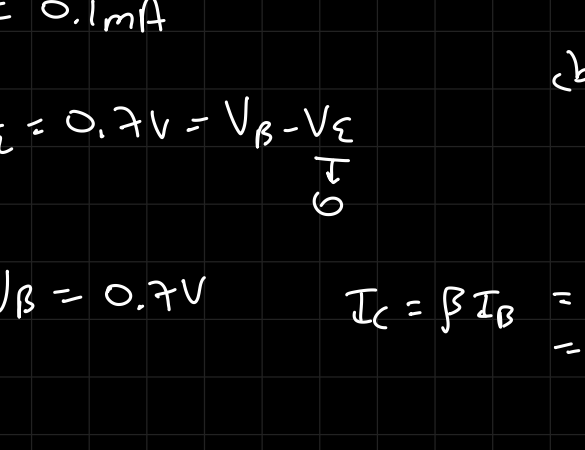

$$I_C = \frac{V_E - (-10)}{10} \text{ mA}$$

$$= \frac{10 - 0.7}{10} \text{ mA}$$

$$= 0.93 \text{ mA}$$

$$\alpha = \frac{I_C}{I_E} \Rightarrow I_C = I_E \left(\frac{\beta}{\beta+1} \right) = 0.93 \times \left(\frac{50}{51} \right) \text{ mA}$$


$$= 0.91 \text{ mA}$$

$$V_C = 10 - 5k I_C$$

$$V_C = 10 - 5 \times 0.91 = 5.45 \text{ V}$$

$$I_B = 0.082 \text{ mA}$$

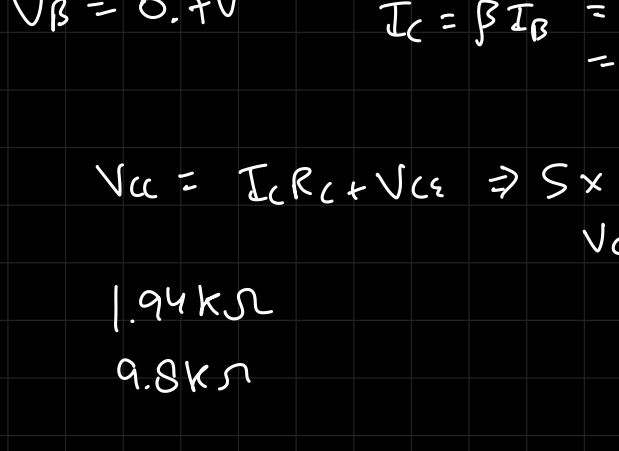Q4) for negative circuit $V_{BE} = 1.7 \text{ V}$ active mode?



While keeping V_{BE} const find that value to which R_C should be increased in order to obtain →

(a) operation at edge of saturation

(b) operation at deep saturation with $\beta_{forced} = 10$

Hint →

(a) for edge of saturation, consider $V_{CE} = 0.3 \text{ V}$

(b) for deep sat, V_{CE} is considered 0.2 V

$$V_B = 0.7 \text{ V} \quad I_C = \beta I_B = 5 \times 0.1 \text{ mA}$$

$$= 5 \text{ mA}$$

$$V_{CE} = I_C R_C + V_{CE} \Rightarrow 5 \times 1 + V_{CE} = 10$$

$$V_{CE} = 5 \text{ V} \gg V_{BE}$$

(active)

2nd) $1.94 \text{ k}\Omega$

$9.8 \text{ k}\Omega$