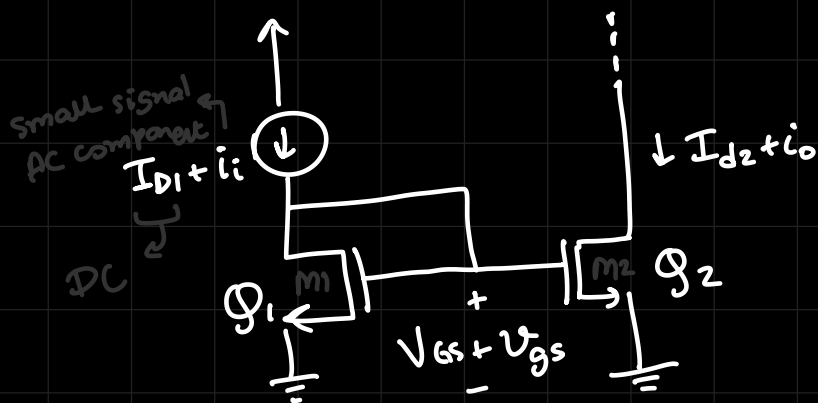


Lecture 17

⇒ Current mirror as current amplifier

low input resistance

higher output resistance wrt R_L




M_2 needs to be in saturation
for current mirror



$$V_{DS2} > V_{GS2} - V_{T2}$$

AC analysis


↳ small signal model (π)

M_1 :

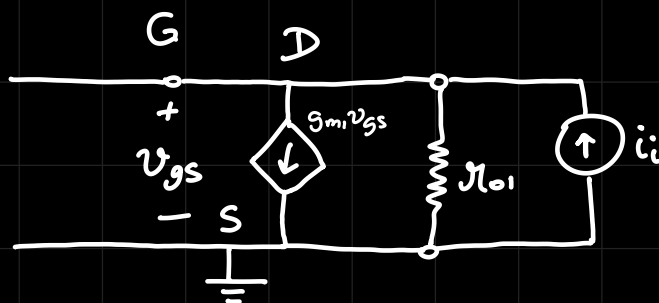


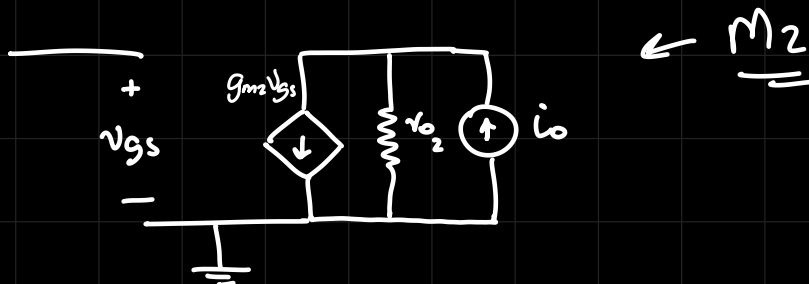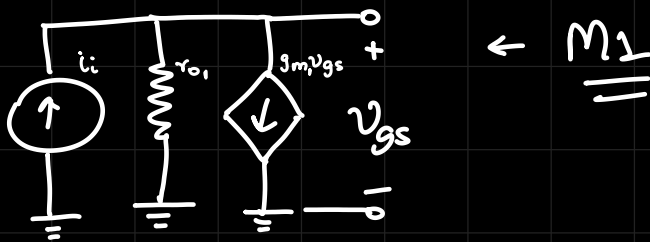

combined crt :

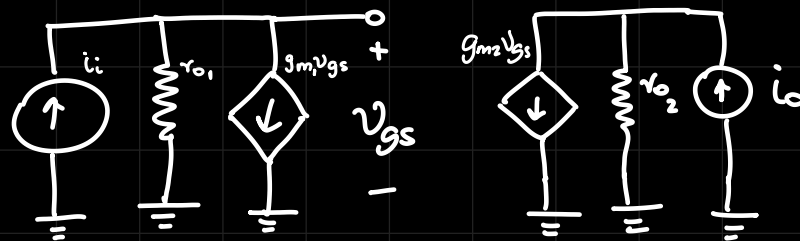

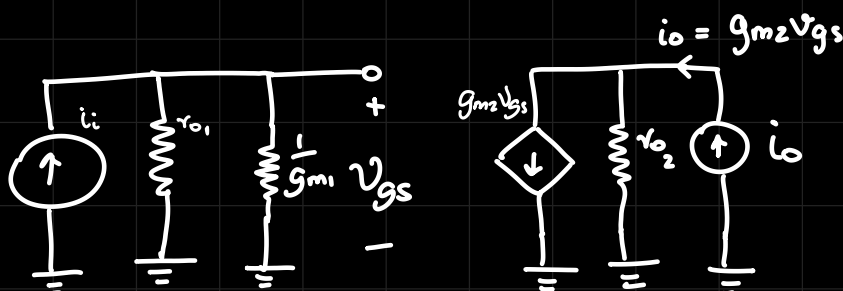dep I src \rightarrow resistor of $R = \frac{1}{g_m}$



: we dont want current to flow through r_{o2} hence r_{o2} should be very high so that I flows through Load

$$Z_{in} = r_{o1} \parallel \frac{1}{g_{m1}} \approx \frac{1}{g_{m1}}$$

$$; Z_o = r_{o2}$$

inverse of V amp

current gain: $A_i = \left. \frac{i_o}{i_i} \right|_{\text{d/p } R_{L1} \ll r_{o2}} = \frac{g_{m2} v_{gs}}{i_i}$

and $v_{gs} = i_i \cdot R_{in} \approx i_i \cdot \frac{1}{g_{m1}}$

assumption: $\frac{1}{g_{m1}} \gg r_{o1}$ \swarrow

$A_i \approx \frac{g_{m2} i_i \cdot 1/g_{m1}}{i_i} \approx \boxed{\frac{g_{m2}}{g_{m1}}} \leftarrow \text{current gain}$

note: we need gain \uparrow and
 hence we neglected $M1$'s
 early effect resistance
 in our assumption
 i.e. $r_{o1} \rightarrow \infty$


$$g_{m2} = 2K_2 (V_{GS2} - V_{T2})$$

$$g_{m1} = 2K_1 (V_{GS1} - V_{T1})$$


$$K_1 = \frac{1}{2} \mu_1 C_{ox} \left(\frac{W}{L} \right)_1, \quad K_2 = \frac{1}{2} \mu_2 C_{ox} \left(\frac{W}{L} \right)_2$$

COMMON GATE

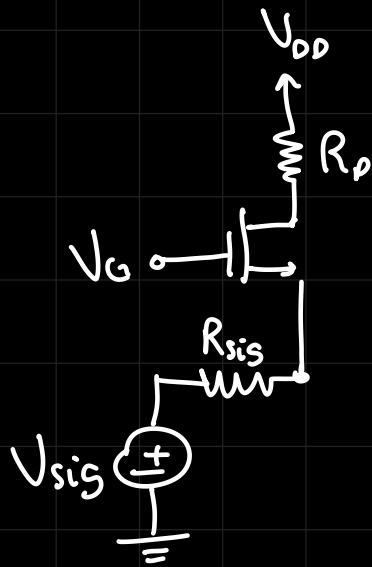We want to distribute the gain over multiple amps to prevent clipping of input.



T model

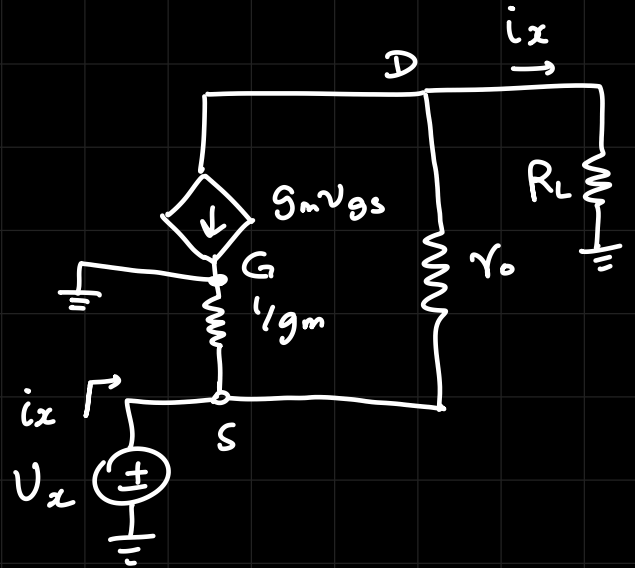

$$I_{ro} = g_m v_{gs} + i_x$$

$$I_{R_L} = i_x$$

$$-V_x + I_{ro} r_o + i_x R_L = 0$$

$$V_x = i_x (r_o + R_L) + g_m v_{gs} r_o$$

$$\text{note: } V_s = -V_{gs} = V_x$$


$$V_x (1 + g_m r_o) = i_x (R_L + r_o)$$

$$R_{in} = \frac{V_x}{i_x} = \frac{R_L + r_o}{1 + g_m r_o} \approx \frac{R_L}{g_m r_o} + \frac{1}{g_m} \quad \left\{ \text{assuming } g_m r_o \gg 1 \right\}$$

* \Rightarrow Even if $R_L \uparrow$, R_{in} scales down R_L by $g_m r_o$ and prohibits the rise of R_{in} significantly.

and hence low input resistance achieved for current amp / buffer.

Now finding out output resistance

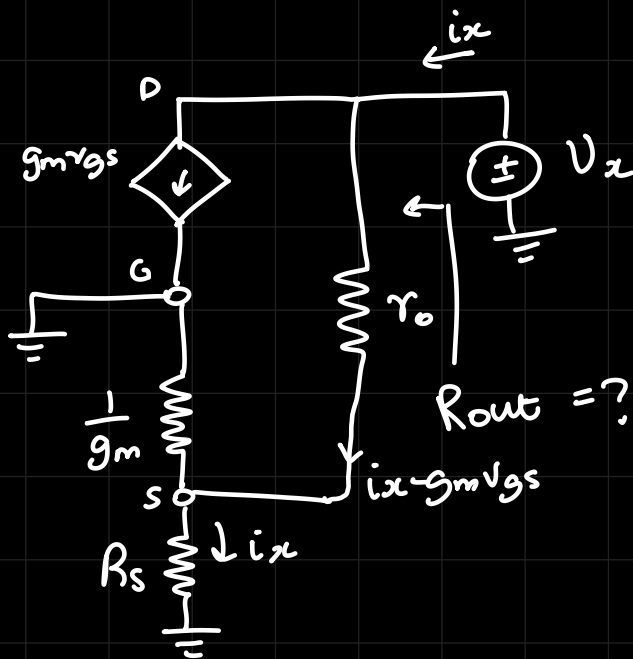


$$V_{gs} = -V_s = -i_x R_s$$

$$V_x = (i_x - g_m V_{gs}) r_o + i_x R_s = (i_x + g_m i_x R_s) r_o + i_x R_s$$

$$R_{out} = r_o + g_m R_s r_o + R_s = r_o + R_s (1 + g_m r_o)$$


The output resistance will be high : $R_{out} = R_s g_m r_o$

CASCODE AMPLIFIER

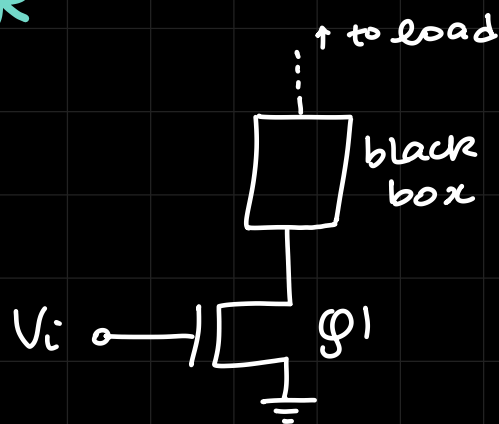

The black box can be a common gate transistor so that ...

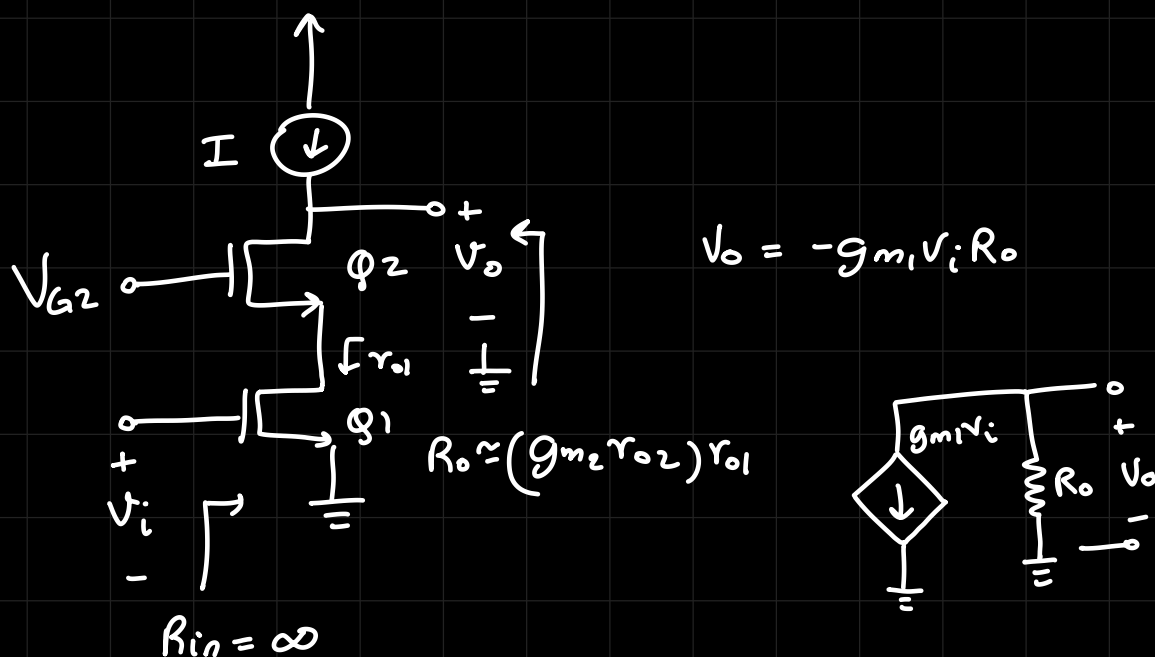- ① Input impedance is not high
and w/out R_L , R_{in} scales by $\frac{R_L}{g_{m1}r_{o1}}$
- ② Output impedance is very high.
 $R_{out} = R_S g_{m1} r_{o1}$
- ③ Current gain = 1



for the CG config,

$$R_o = g_{m2} r_{o2} R_s : \text{derived earlier}$$

$R_s = r_{o1}$ because ϕ_1 is the SRC for ϕ_2

$$\text{So, } R_o = g_{m2} r_{o2} r_{o1}$$

$$A_v = -g_{m1} R_o = -g_{m1} g_{m2} r_{o2} r_{o1}$$

$$= -g_{m1} r_{o1} g_{m2} r_{o2}$$

Let $g_{m1} = g_{m2} = g_m$ and $r_{o1} = r_{o2} = r_o$

$$A_v = -(g_m r_o)^2 = -A_{v_o}^2$$

where A_{v_o} = volt gain of regular CS transistor

TRADEOFFS:


for M_1 : saturation,

$$V_{x1} > V_{in} - V_{t1}$$

$$V_{GS2} = V_{G2} - V_{S2}$$

$$V_{S2} = V_{G2} - V_{GS2}$$
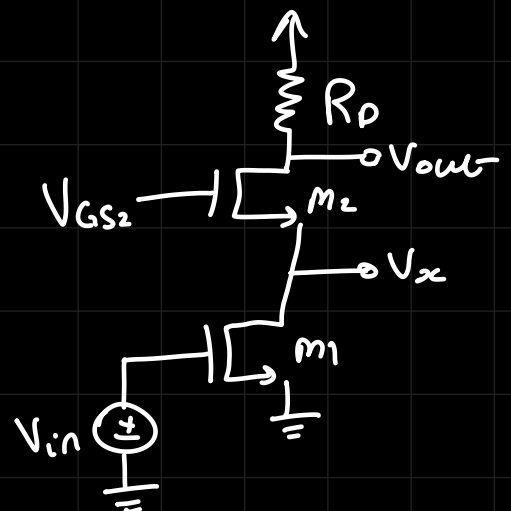
$$V_{x1} = V_{S2} = \underline{V_{G2} - V_{GS2} > V_{in} - V_{t1}}$$



for M_2 : saturation \rightarrow

$$V_{D2} > V_{GS2} - V_{T2}$$

$$V_{D2} - V_{S2} > V_{GS2} - V_{T2}$$

$$V_{out} - V_x > V_{GS2} - V_{T2}$$

$$V_{out} > V_{GS2} - V_{T2} + V_x$$

$$\text{and } V_x > V_{in} - V_{T1}$$

$$\text{but } V_x = V_{in} - V_{T1}$$

$$V_{out} \geq \underbrace{V_{GS2} - V_{T2}}_{V_{ov2}} + \underbrace{V_{in} - V_{T1}}_{V_{ov1}}$$

overdrive voltages

increasing more op_{rs} in cascode, will

keep on increasing V_{out} depending on V_{ovs}

which might distort the output signal

when $V_{out} < V_{ov1} + V_{ov2} + \dots$

HORIZONTALLY INCREASING: gain \uparrow , g stable \checkmark

VERTICALLY INCREASING : gain \uparrow , distortion \uparrow