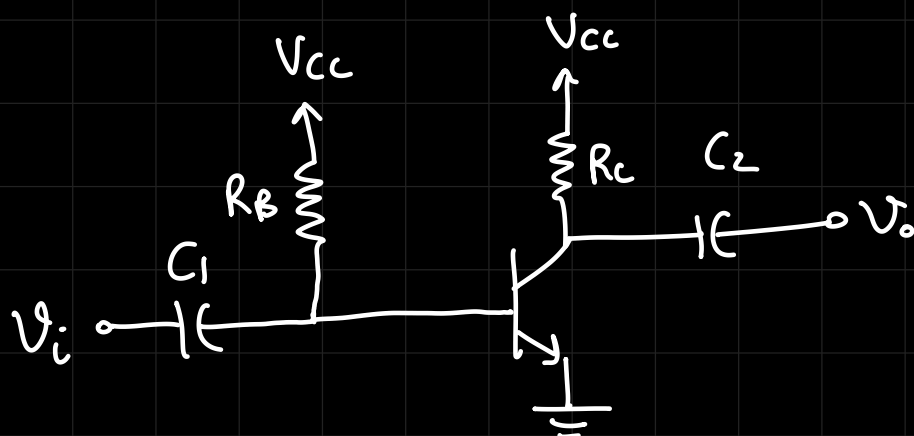


POWER Amplifier

1. CLASS A Power Amplifier / Direct coupled Power Amp
2. CLASS A Power Amplifier - Transformer coupled
3. CLASS B Amplifier - Push Pull Amplifier
4. CLASS C Amplifier

CLASS A Amp / Direct coupled amplifier

it is called direct coupled amplifier because the input and output AC voltage is directly coupled to the Transistor (BJT/MOS)



C_1 and C_2 are coupling capacitors
for DC analysis, all the caps $\rightarrow \infty$

$$V_{CC} = V_{CE} + I_C R_C$$

DC load line



$$I_C = -\frac{1}{R_C} V_{CE} + \frac{1}{R_C} V_{CC}$$

$$Q(V_{CE}, I_C)$$

$$I_C = 0 \rightarrow V_{CE} = V_{CC}$$

$$V_{CE} = 0 \rightarrow I_C = \frac{1}{R_C} V_{CC}$$

AC analysis:

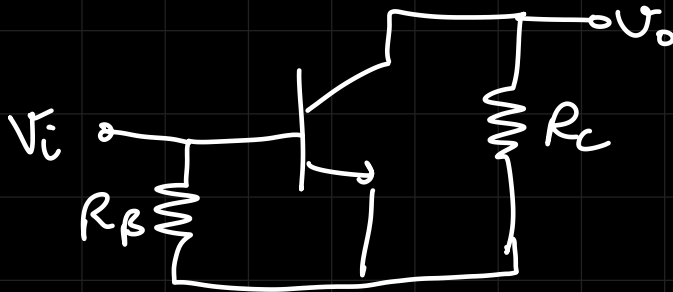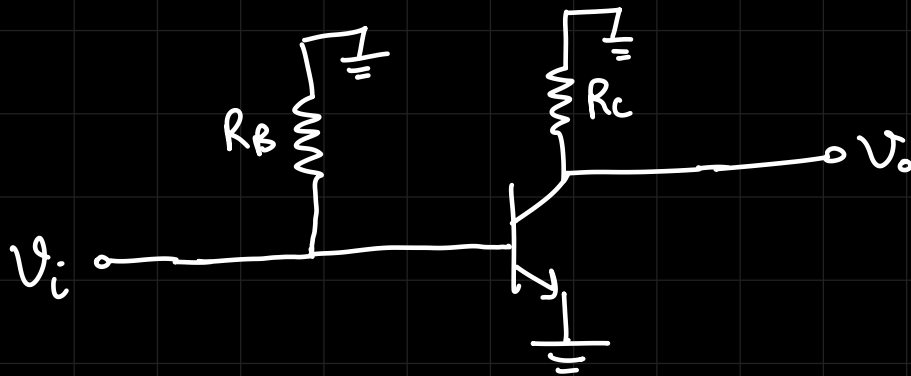

→ pure AC

$$-V_{CE} - i_C R_C = 0$$

$$i_C = -\frac{1}{R_C} \cdot V_{CE}$$

↳ slope

Note: we get the same slope for
 i_C vs V_{CE} and I_{CQ} vs V_{CE}
 (pure AC) (pure DC)

$$i_C = i_{CQ} - I_{CQ}$$

$$v_{CE} = v_{ce} - V_{CE}$$

$$i_c = \frac{-1}{R_c} V_{ce}$$

$$i_c - I_{cQ} = \frac{-1}{R_c} (V_{ce} - V_{ce,Q}) \quad - \textcircled{3}$$

$$(y - y_1) = m(x - x_1)$$

We observe that the Q point remains same for both, the AC case & the DC case

2 x BJT/mosFET
 Cascode/cascode
 CMOS
 Power Amp
 Current mirror
 Differential Amplifier

Eqn 3 is a general straight line of slope $\frac{-1}{R_c}$ and is passing through the

Q point (V_{ce}, I_c)

Since the DC and AC load line same slope and both pass through the same point

$$\text{efficiency: } \eta = \frac{P_{dc}}{P_{ac}} \times 100$$

$$P_{dc} = V_{cc} \times I_{CQ}$$

$$P_{ac} = V_{rms} \times I_{rms}$$

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$


$$= \frac{V_m I_m}{2}$$

$$V_m = \frac{V_{max} - V_{min}}{2} = \frac{V_{cc} - 0}{2} = \frac{V_{cc}}{2}$$

$$I_m = \frac{I_{max} - I_{min}}{2} = \frac{2I_{CQ} - 0}{2} = I_{CQ}$$

$$\eta = \frac{\frac{1}{2} \times V_{cc}/2 \times I_{CQ}}{V_{cc} I_{CQ}} = \frac{1}{4} = \boxed{25\%}$$

for class
A amplifier

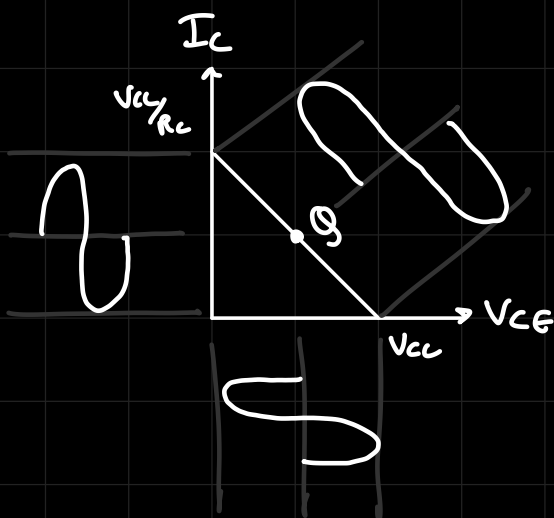


conduction
angle: 360°

full swing

CLASS-A / TRANSFORMER COUPLED AMP

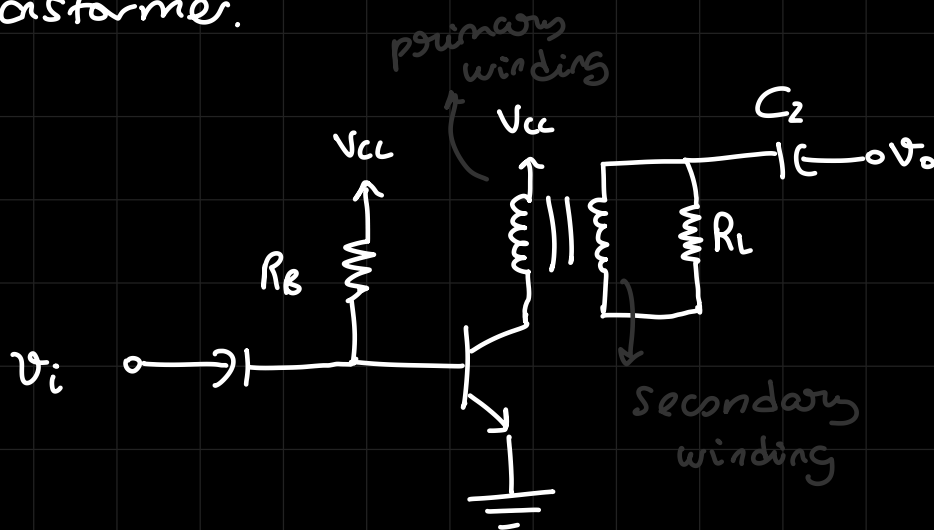In this power amplifier the load is connected to the output node of the amplifier through a transformer.



for DC analysis, all caps \rightarrow OC

$$X_L = \omega L \Omega$$
$$= 2\pi f L \Omega$$

for DC $\rightarrow X_L = 0 \Omega$

KVL: $V_{CC} = I_C X_L + V_{CE}$

$$= I_C(0) + V_{CE}$$

$$\underline{V_{CC} = V_{CE}}$$

equation of line
parallel to y axis
 ∞ slope

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2} = n$$

$$\hookrightarrow \frac{V_1}{V_2} \times \frac{I_2}{I_1} = n^2$$

$$\frac{V_1/I_1}{V_2/I_2} = n^2$$

$$\frac{V_2}{I_2} = R_L \rightarrow \frac{V_1/I_1}{R_L} = n^2$$

$$\text{let } V_1/I_1 = R_L'$$


$$\text{so, } \frac{R_L'}{1} = n^2 \cdot R_L$$

reflected load
resistance


i.e. R_L' is the reflection of R_L in primary winding ; we also replace secondary winding resistance with R_L' in the primary winding.

for AC analysis \rightarrow caps act as short ckt and deactivate DC src

AC :

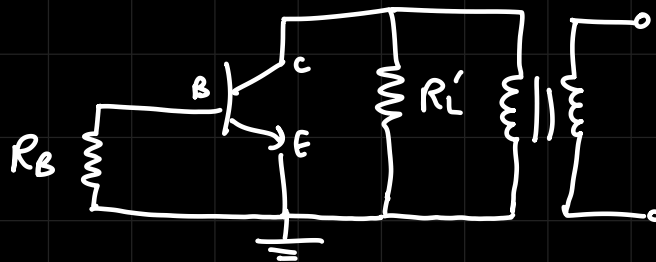

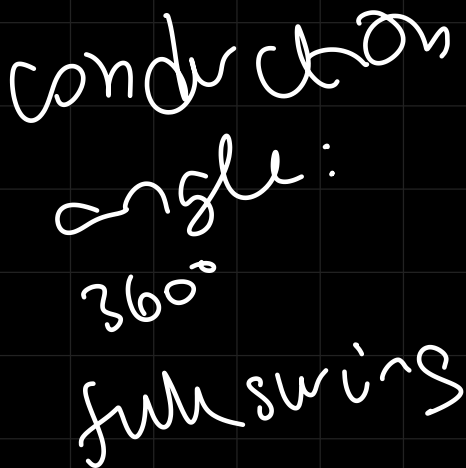At medium frequencies, the inductive reactance of the primary and secondary winding will be large enough therefore, the resistance can be treated as open ckt



→ A class A / transformer coupled amplifier delivers max AC power of 5Watt at 4Ω Load resistance. If the op pnt is located for max symmetrical swing and the DC supply voltage is 20V (V_{CC}).

- (1) transformer turn ratio
- (2) peak output current
- (3) op pnt
- (4) conversion efficiency

Ans) $P_{ac} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$

$$V_m = I_m R_L'$$

$$I_m = \frac{V_m}{R_L'}$$

$$P_{ac} = \frac{V_m^2}{2R_L'} \rightarrow$$

$$R_L' = n^2 R_L$$

$$n^2 = \frac{R_L'}{4}$$

Symmetrical $\rightarrow V_m = V_{CC} \rightarrow R_L' = \frac{20 \times 20}{2 \times 5} = \underline{40\Omega}$

$$n^2 = 10 \Rightarrow n = \sqrt{10} = 3.14 = \frac{N_1}{N_2}$$

(b) $I_m = \frac{V_m}{R_L'} = \frac{20}{40} = 0.5A$ / $V_{CEQ} = V_{CC} = 20V$
 $Q(20V, 0.5A)$

$$P_{dc} = V_{cc} \times I_{cq} = 20 \times 0.5 = 10$$

$$\eta = \frac{P_{ac}}{P_{dc}} \times 100\% = \frac{5}{10} \times 100\% = \underline{50\%}$$