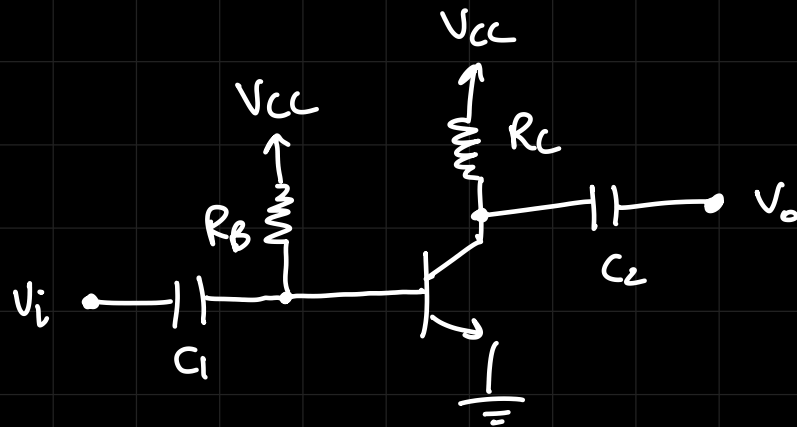


Fixed Bias




DC analysis for Q point

- ↳ open ckt all capacitors
- ↳ BE & CE loop
- ↳ common emitter config

Any variation in β will impact in I_C and hence will shift the Q point. Therefore this amplifier bias is not ideal

* For multiple devices where fixed bias ckt may be a subsystem (i.e. we may have multiple values of β), we may get different Q point which will result in the transistor being in indeterminate mode. We need standardized values.

Voltage Divider Bias

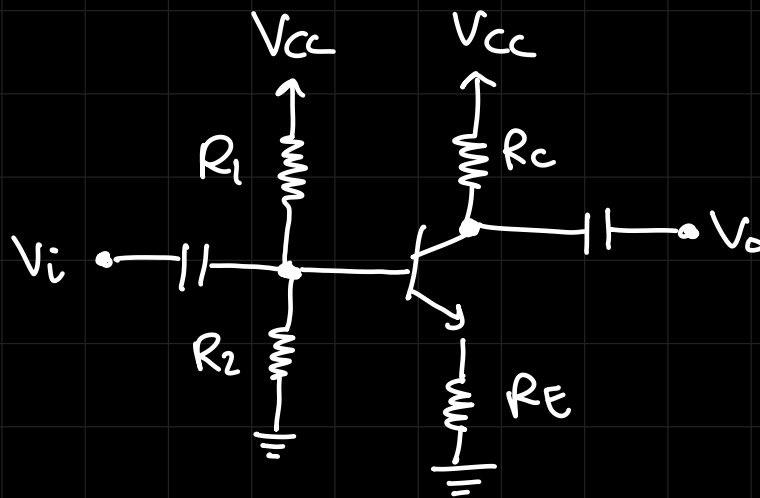

A DC bias voltage
can be created using R_1, R_2
 I_B can also be adjusted

simplified using Thevenin's Equivalent

$$-V_{Th} + I_B R_{Th} + V_{BE} + I_E R_E = 0$$

$$I_E = (\beta + 1) I_B$$

$$I_B (R_{Th} + R_E (\beta + 1)) = V_{Th} - V_{BE}$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + R_E (\beta + 1)}$$

$$I_C = \beta I_B = \frac{\beta (V_{Th} - V_{BE})}{R_{Th} + R_E (\beta + 1)}$$

due to variation in β , we have variation in I_C in the numerator but also a feedback pulling the value down in the denominator.

$$I_E = (\beta + 1) I_B = \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{\beta + 1}} \quad \left. \begin{array}{l} \text{we want} \\ \text{① } V_{TH} \gg V_{BE} \text{ to} \\ \text{not have any} \\ \text{small signal variation} \end{array} \right\}$$

CE loop: $-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$


assuming $I_C \approx I_E$

Since I_C is stabilized, V_{CE} will be stabilized as well.

we also want \rightarrow ② $R_C \gg \frac{R_{TH}}{\beta}$ to make

I_E and I_C , β invariant
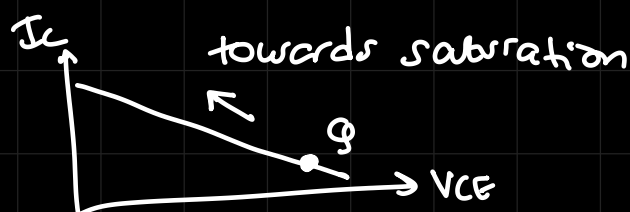
$$V_{TH} \uparrow \rightarrow I_E \uparrow \rightarrow I_C \uparrow \rightarrow V_{CE} \downarrow$$



but if $V_{Th} \downarrow$, $I_E \downarrow$, $I_C \downarrow$, $V_{CE} \uparrow$



So, we need to maintain V_{Th} such that transistor remains in active mode

Rule of thumb \rightarrow

$$V_{Th} = \frac{1}{3} V_{CC}$$

$$V_{CB} = \frac{1}{3} V_{CC}$$

(or V_{BE})

$$I_C R_C = \frac{1}{3} V_{CC}$$


$$I_1 / I_2 = (0.1 - 1) \times I_f$$

Q)

$$I_E = 1 \text{ mA}$$

$$V_{CC} = 12 \text{ V}$$

$$\beta = 120$$

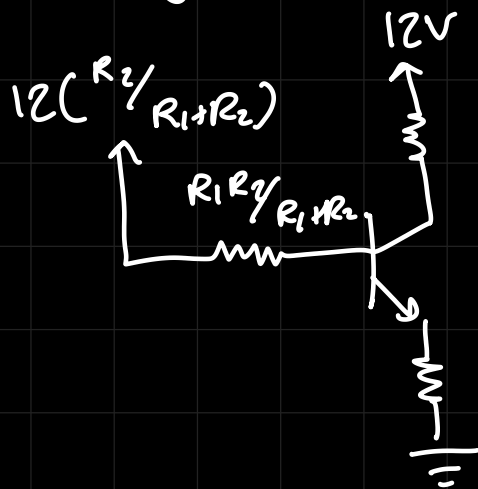

$\frac{1}{3} V_{CC}$ for R_C ; $\frac{1}{3} V_{CC}$ for R_E ; rest $\frac{1}{3}$ for possible negative signal swing

As per rule of thumb \rightarrow

$$V_B = \frac{1}{3} V_{CC} = \underline{4 \text{ V}}$$


$$V_C = \frac{2}{3} V_{CC} = \underline{8 \text{ V}}$$

$$V_E = V_B - V_{BE} = \underline{3.3 \text{ V}}$$

$$R_E = \frac{V_E}{I_E} = 3.3 \text{ k}\Omega$$

Assume, $I_B \approx 0 \rightarrow I = \frac{V_{CC}}{R_1 + R_2} \rightarrow I$ can be $[I_E, 0.1 I_E]$

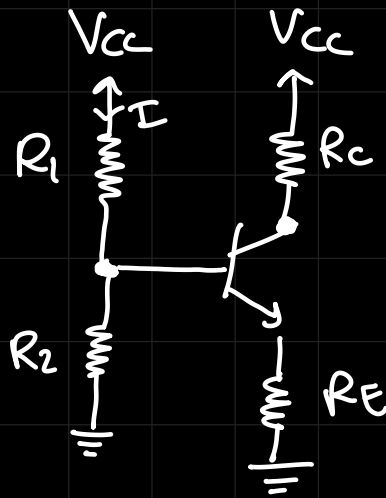Case 1: $I = 0.1 I_E = 0.1 \text{ mA} = \frac{12}{R_1 + R_2} \rightarrow R_1 + R_2 = 12 \times 10^4$ (1)



$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

$$V_B = \frac{12 R_2}{12 \times 10^4}$$

$$4 \times 10^4 = R_2 \rightarrow R_2 = 40 \text{ k}\Omega$$

$$R_1 = 80 \text{ k}\Omega$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}}, \quad R_B = \frac{320 \text{ k}\Omega}{120} \Rightarrow \frac{80}{3} \Omega$$

$$I_E = \frac{\frac{1 \times 40 \text{ k}\Omega}{10 \text{ k}\Omega} - 0.7}{R_E + \frac{320 \text{ k}\Omega}{120}} = \frac{3.3}{R_E + \frac{80}{303}}$$

$$I_E = 0.925 \text{ mA} \approx 0.93 \text{ mA}$$

now reduce R_E by $\frac{R_B}{101}$

$$R_E' = R_E - \frac{R_B}{101} = 3.3k - 0.267k = 3.03k\Omega$$

$$I_E' = \frac{4 - 0.7}{3.03k + \frac{80}{203}} \approx 1.0018 \text{ mA}$$

Case 2 : $I = I_E = 1 \text{ mA}$


$$\frac{V_{CC}}{R_1 + R_2} = 1 \text{ mA}$$

$$R_1 + R_2 = 12k\Omega$$


$$\left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = 4V \Rightarrow R_2 = 4k\Omega$$
$$R_1 = 8k\Omega$$

$$I_E = \frac{3.3}{3.3 + \left(\frac{8}{3} \right) / 101} = 0.992 \text{ mA} \approx 1 \text{ mA}$$

emitter stabilized circuit

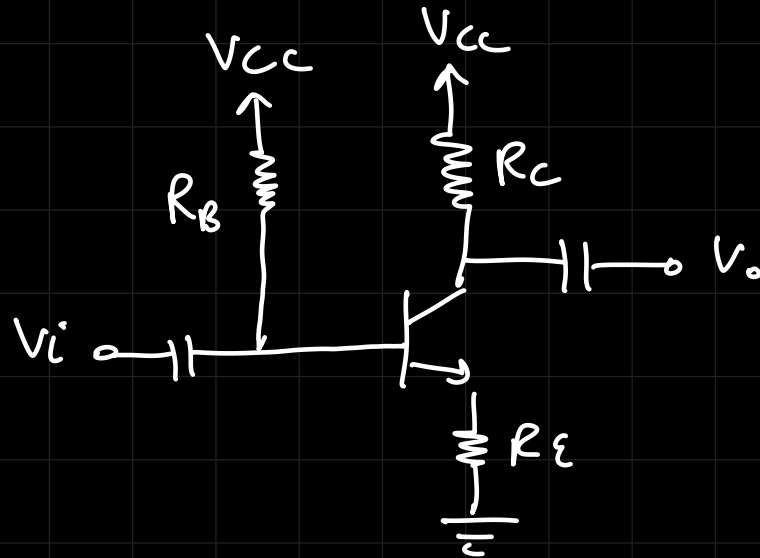

DC analysis

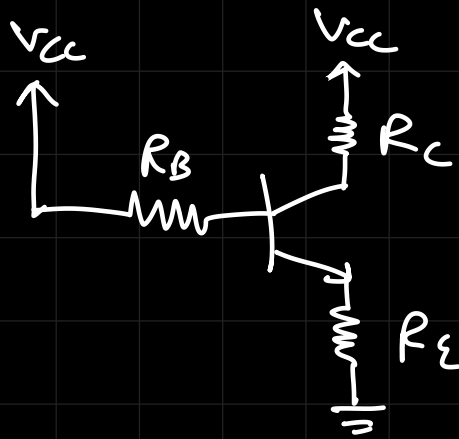

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$I_B = \frac{I_E}{(\beta + 1)}$$


$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1) R_E}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

Note: we have control/feedback unlike fixed bias

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

DC bias with voltage Feedback

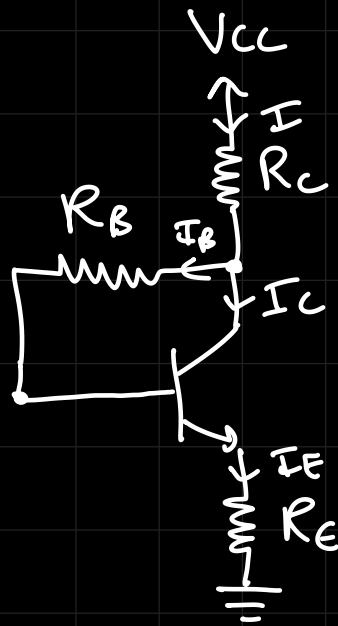

$$-V_{CC} + I_C R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

assuming $I_B \ll I_C$

$$-V_{CC} + I_C R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

$$-V_{CC} + I_B (\beta R_C + R_B + (\beta + 1) R_E) + V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{\beta R_C + R_B + (\beta + 1) R_E}$$

assuming $I_C \approx I_E$

$$\text{So, } I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta (R_C + R_E)}$$

$$I_C = \beta I_B = \frac{V_{CC} - V_{BE}}{\frac{R_B}{\beta} + R_C + R_E}$$

much better &

robust as compared to emitter stabilized bias
| What is the tradeoff? |

amplifier design \rightarrow adequate gain
prevents distortion in output \leftarrow stabilize Q point
infinite input resistance
low output impedance
linear amplification

CE: V amp \rightarrow out of phase by 180°

CB: V amp \rightarrow in phase

CC: buffer amp