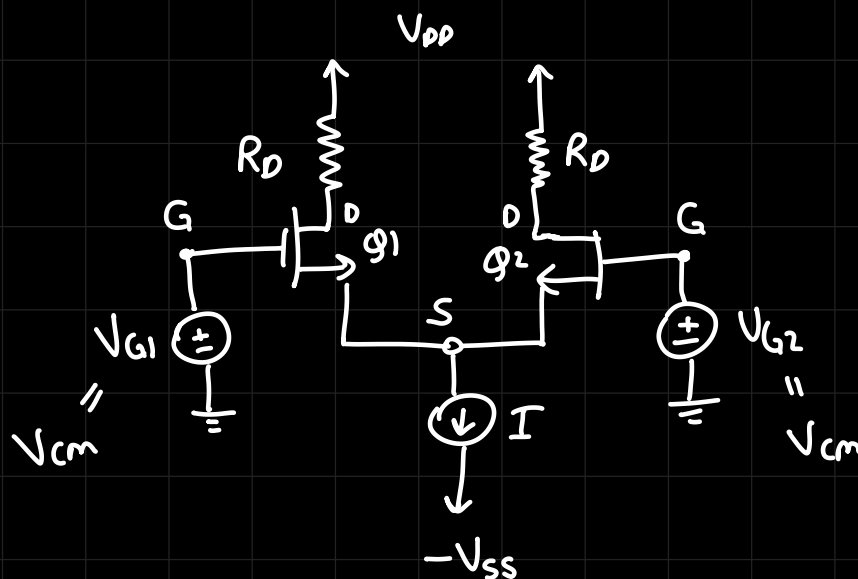


→ **Differential Amplifier**

SNR: signal to noise ratio  
(maximize it)



obj: to find the  
differential o/p  
given that some  
value of  $V_{G1}, V_{G2}$   
 $= V_{cm}$

$Q_1$  and  $Q_2$  are  
in saturation

Common mode  
voltage

↙  $V_{cm}$  is the voltage  
applied at the 2 gate  
terminals  $V_{G1}, V_{G2}$

Since  $Q_1, Q_2$  are matched, they both will conduct  
a current  $I'$  i.e.  $I_{D1} = I_{D2} = I'$  and since  $I_{D1} + I_{D2} = I$   
so →  $I' = I/2$

Biased by the current source  $I$

$$V_s = ?$$

$$V_{GS} = V_G - V_S = V_{cm} - V_S$$

$$\underline{V_S = V_{cm} - V_{GS}}$$

$$\text{but } K = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$$

$$\text{for } g_1 \rightarrow \frac{I}{2} = \frac{1}{2} \overset{\mu_n C_{ox}}{K_n} \left( \frac{W}{L} \right) (V_{GS} - V_T)^2$$

$$\text{we know } V_{GS} - V_T = V_{ov}$$

$$I = K_n \left( \frac{W}{L} \right) V_{ov}^2$$

$$V_{ov} = \sqrt{\frac{I}{K_n (W/L)}} \quad \text{--- ①}$$

to find the output voltage i.e. differential in nature  $\rightarrow V_o = V_{D2} - V_{D1}$

$$V_{D1} = V_{DD} - \frac{I}{2} R_D = V_{D2}$$

$$\boxed{V_o = 0}$$

Range over which  $V_{cm}$  will give a valid outcome for  $V_o = 0$  ?

note:  $g_1$  and  $g_2$  must remain in saturation



$$V_{DS} > V_{GS} - V_T \quad \downarrow$$

$$V_D > V_G - V_T$$

$$V_{DD} - \frac{I}{2} R_D > V_{cm} - V_T$$

$$V_{cm} < V_T + V_{DD} - \frac{I}{2} R_D$$

$$\boxed{V_{cm}^{max} = V_T + V_{DD} - \frac{I}{2} R_D}$$

② for the current SRC to give current bias, we need some potential  $\approx V_{CS}$

$$V_S - (-V_{SS}) > V_{CS}$$

$$V_S = V_{cm} - V_{GS}$$

$$V_{cm} - V_{GS} + V_{SS} > V_{CS}$$


$$V_{cm} > V_{CS} + V_{GS} - V_{SS}$$

we know,  $V_{GS} = \underbrace{V_{GS} - V_T}_{V_{OV}} + V_T$

$$V_{cm} > V_{CS} + V_{OV} + V_T - V_{SS}$$

So, range of  $V_{cm}$ :
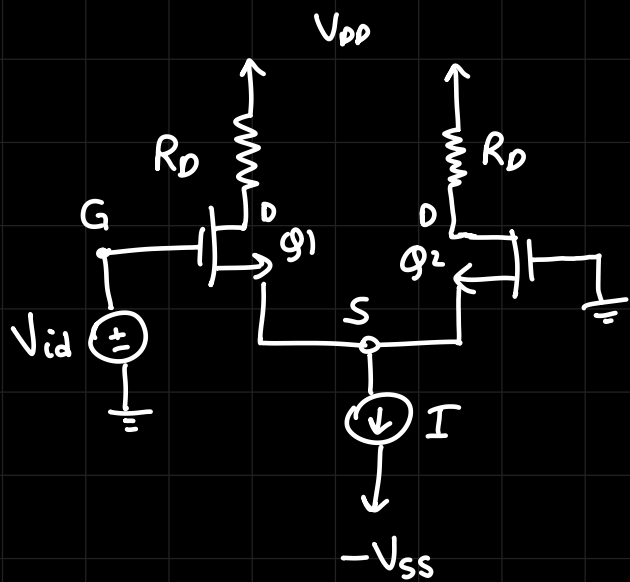
$$V_{CS} + V_{OV} + V_T - V_{SS} < V_{cm} < V_T + V_{DD} - \frac{I}{2} R_D$$



for  $V_{id}^{max}$ , current will flow through  $Q_1$  only and through  $Q_2$  for  $V_{id}^{min}$

So, now find range for  $V_{id}$  such that:  $V_{id}^{min} \leq V_{id} \leq V_{id}^{max}$

$V_{id} \Rightarrow$  potential at which the bias current ( $I$ ) will flow through  $Q_1$  and no current will flow through  $Q_2$ .

for  $Q_1$ : 
$$I = \frac{1}{2} K_n \left( \frac{W}{L} \right)_{Q_1} (V_{GS1} - V_T)^2$$

$$V_{GS1} = V_T + \sqrt{\frac{2I}{K_n(W/L)_{Q_1}}} =$$

from ①: 
$$V_{ov} = \sqrt{\frac{I}{K_n(W/L)_{Q_1}}}$$

$$V_{GS1} = V_T + \sqrt{2} V_{ov}$$

②

for  $Q_2$ :  $I = 0$

$$0 = k(V_{GS2} - V_T)^2$$

$$\rightarrow V_{GS2} = V_T$$

$$\cancel{V_{G2}}^0 - V_{S2} = V_T$$

$$-V_{S2} = -V_S = V_T$$

$$\boxed{V_S = -V_T} \text{ --- (3)}$$

from (2), (3)

$$V_{GS1} = V_T + \sqrt{2}V_{OV}$$

$$V_{G1} + V_T = V_T + \sqrt{2}V_{OV}$$

$$V_{G1} = \sqrt{2}V_{OV}$$

so,  $\boxed{V_{id}^{max} = \sqrt{2}V_{OV}}$

for  $V_{id}^{min}$ : for  $Q_1 \rightarrow I = 0$

$$V_{GS1} = V_T \rightarrow V_{G1} - V_T = V_S \text{ (4)}$$

for  $Q_2 \rightarrow I = \frac{1}{2}K_n \frac{W}{L} (V_{GS2} - V_T)^2$

$$V_{GS2} = V_T + \sqrt{\frac{2I}{k_n(W/L)_{Q_2}}} =$$

$$-V_S = V_T + \sqrt{\frac{2I}{k_n(W/L)\phi_2}}$$

$$-V_S = V_T + \sqrt{2}V_{ov}$$

$$V_S = -\sqrt{2}V_{ov} - V_T$$

$$V_{G1} - \cancel{V_T} = -\sqrt{2}V_{ov} - \cancel{V_T} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{from ①}$$


$$V_{G1} = -\sqrt{2}V_{ov}$$

$$V_{id}^{min} = -\sqrt{2}V_{ov}$$



So, range for  $V_{id}$  :

$$-\sqrt{2}V_{ov} < V_{id} < \sqrt{2}V_{ov}$$

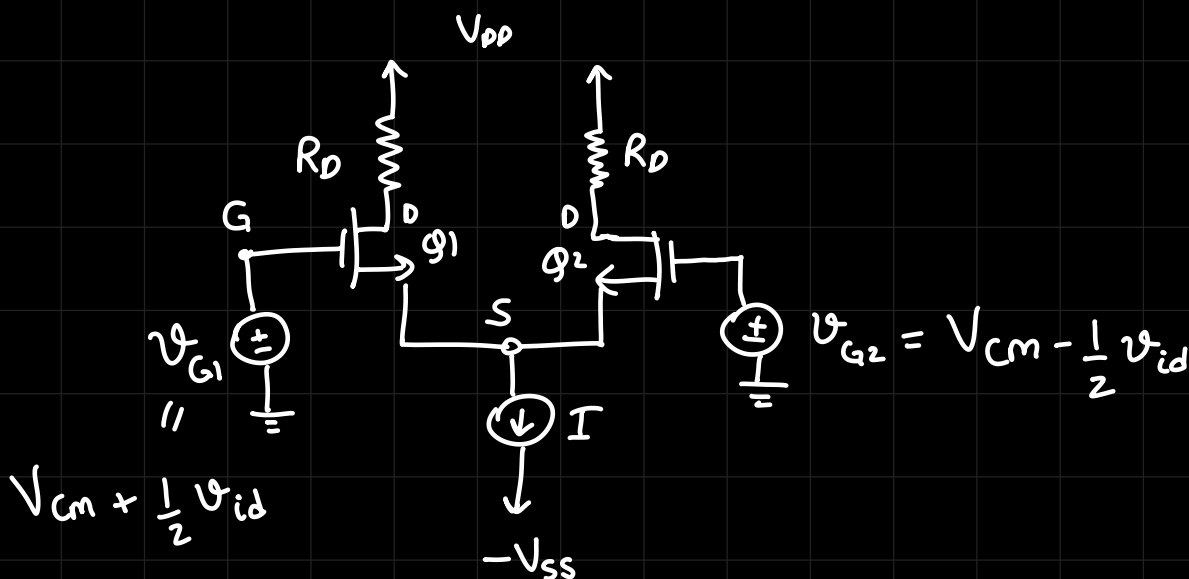assuming  $Q_1$  and  $Q_2$  are in saturation



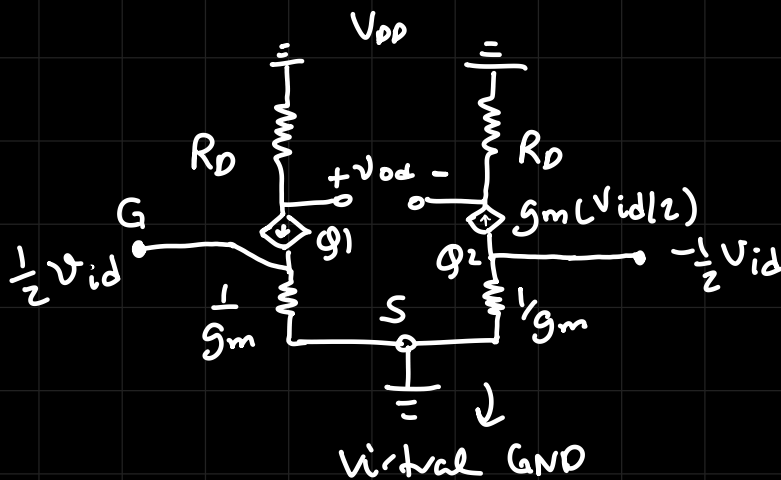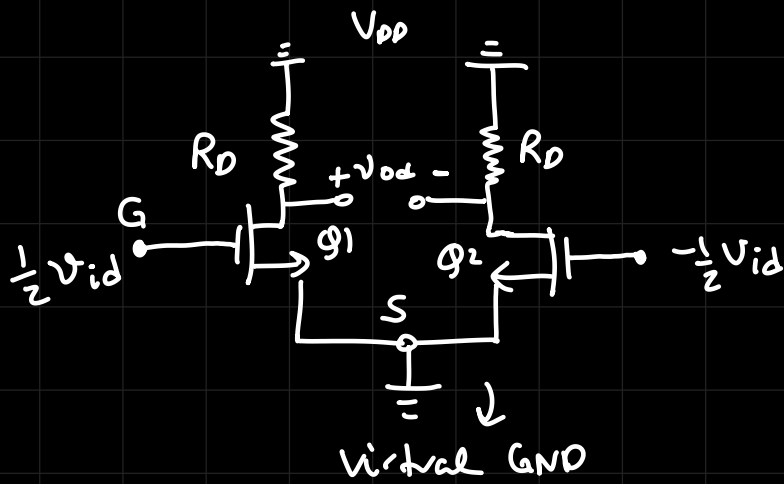AC analysis  $\rightarrow$  Remove DC SRC



$$I_D = g_m \frac{V_{id}}{2}$$

$$V_{o1} = -g_m \frac{V_{id}}{2} R_d$$

$$V_{o2} = g_m \frac{V_{id}}{2} R_d$$

$$A_{v1} = \frac{V_{o1}}{V_{id}} = -\frac{1}{2} g_m R_d \quad \left. \vphantom{A_{v1}} \right\} \text{1st branch}$$

$$A_{v2} = \frac{V_{o2}}{V_{id}} = \frac{1}{2} g_m R_d \quad \left. \vphantom{A_{v2}} \right\} \text{2nd branch}$$

$$A_D = \frac{V_o}{V_{id}} = \frac{V_{o2} - V_{o1}}{V_{id}} = \underline{g_m R_d} \quad \left. \vphantom{A_D} \right\} \text{Differential gain}$$

↳ double of that of individual branch gain

70% project

Filter

V amp

P amp

aux out