

Lecture : 1

COURSE: Analog Electronics

⇒ Signals

- contains info about stuff in physical environment
eg: Temp, Pressure, Heat, Audio etc.
- Devices are used to extract info from the environment
- Signals can be processed to achieve the desired results; eg: amplification / compression / ...
- Processed using electronic circuits.
- Physical signals must be identically converted into an electronic signal using **TRANSDUCERS**
eg: microphones have pressure transducers
seismic transducers used for animal movement by NFR in remote areas

Voltage SRC → Thevenin

Current SRC → Norton

waves

↳ Amplitude

↳ Frequency

↳ Phase

• FREQUENCY SPECTRUM OF SIGNALS

no. of frequencies in...

~ sinusoidal signal → 1 at origin

~ rectangular signal → very high

~ sawtooth signal → very high


Sampling → convert from analog to discrete

digital vs discrete

limited on the amplitude scale

no limit on the set of amplitude it can achieve

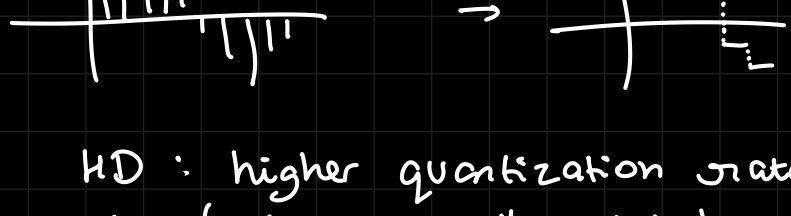Two level quantizer → snaps the value to either 0/1 depending if value is low/high



4 level quantizer → better resolution / precision



HD : higher quantization rate

(not necessarily related to sampling rate)


more info per "packet"

expensive

↳ ckt design

↳ transportation from source to destination

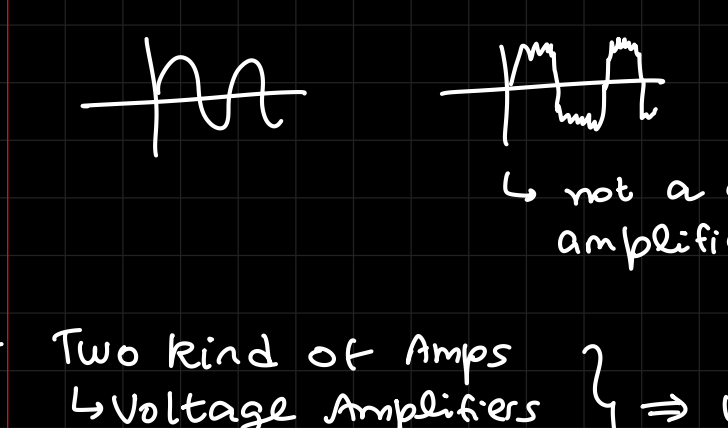Conversion happens using **A/D converter**




⇒ Amplification

Transducers operate at very low power ~ low

Here, the signal produced has a very low amplitude. That's why amplifiers are needed.

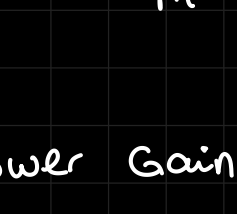LINEARITY : after amplification, no distortion should be introduced



↳ not a good amplifier (non-linear)

* Two kind of Amps


↳ Voltage Amplifiers

↳ Current Amplifiers

⇒ we also have power amplifiers

↳ substantial current gain

↳ moderate voltage gain

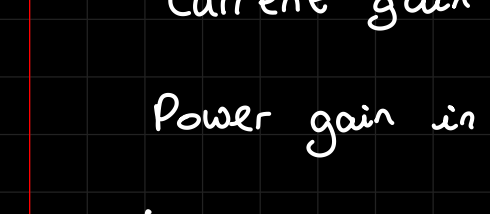

• Voltage Gain (A_v)

$$A_v = \frac{V_o}{V_i}$$



• Current Gain (A_i)

$$A_i = \frac{i_o}{i_i}$$

• Power Gain (A_p)

$$A_p = \frac{V_o i_o}{V_i i_i} = A_v A_i$$

→ Gain in dB (logarithmic scale)

only two operations : add/subtract
easier to operate on larger values

$$\text{VOLT gain in dB} = 20 \log_{10} |A_v|$$

$$\text{Current gain in dB} = 20 \log_{10} |A_i|$$

$$\text{Power gain in dB} = 10 \log_{10} |A_p|$$

if you combine two phase shifted waves, it is destructive


⇒ Amplifier Power Supply

where are the extra signals coming from?

↳ DC Power Source


↳ decides the gain of the amplifier

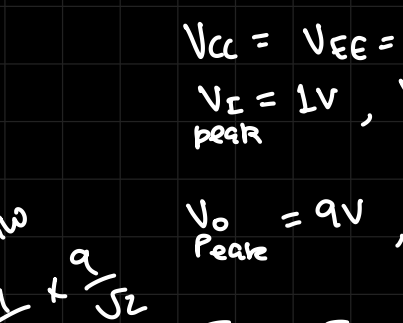Actual amplifiers do not provide an amplification. There is some threshold which is allocated by the DC SRC (**BIAS**)



$$P = V_{cc} I_{cc} + V_e I_e$$

$$P_{dc} + P_i = P_L + P_{dissipated}$$

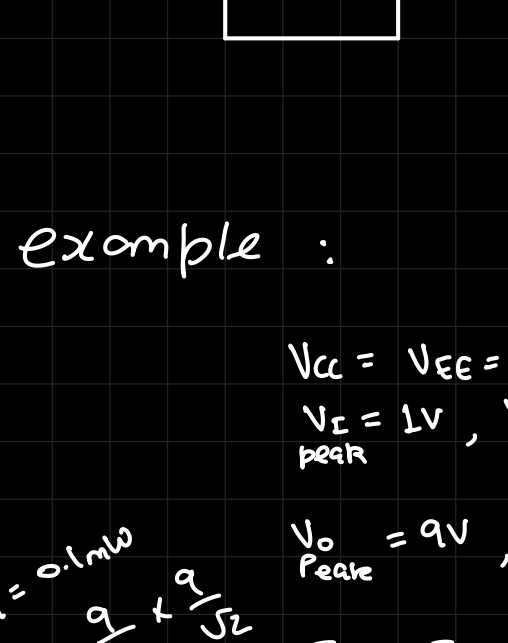

example :

$$V_{cc} = V_{EE} = 10V$$

$$V_E = 1V, \quad V_{RMS I} = \frac{1}{\sqrt{2}} V$$

$$V_o = 9V, \quad V_{RMS o} = \frac{9}{\sqrt{2}} V$$

$$I_{cc} = I_{EE} = 9.5 mA$$

$$R_L = 1 k\Omega$$

$$i_E = 0.1 mA, \quad i_{RMS I} = \frac{0.1}{\sqrt{2}} mA$$

$$P_i = 0.1 mW$$
$$P_L = \frac{9}{\sqrt{2}} \times \frac{9}{\sqrt{2}}$$
$$\downarrow$$
$$V_o \times I_o = \frac{81}{4}$$
$$= 40.5 mW$$

$$\text{Voltage gain : } A_v = \frac{9/\sqrt{2}}{1/\sqrt{2}} = 9 = 19.1 dB$$

$$\text{Current gain : } A_i = \frac{V_o/R_L}{0.1} = \frac{9/1000}{0.1 \times 10^{-3}} = 90 = 39.08 dB$$

$$\text{Power gain : } A_p = A_i \times A_v = 810 = 29.1 dB$$

$$\text{Power drawn from dc src : } P_{dc} = 190 mW$$
$$\downarrow V_{cc} I_{cc} + V_{EE} I_{EE}$$

$$\text{Power dissipated in amp : } P_{diss} = P_L - P_i - P_{dc}$$
$$= 149.5 mW$$

$$\text{efficiency} = \frac{P_L}{P_{dc}} \times 100 = 23.1\%$$

→ Amplifier Saturation

Signal clipping : if amp not designed properly

↳ Amp error