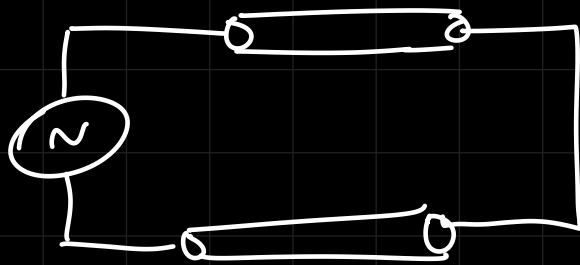


# # Lecture

transmission line ended with short circuit



for low freq det, KVL and KCL apply and  $Z_{in} = 0$


for high freq  $\rightarrow Z_{in} = Z_0 \left[ \frac{Z_L + Z_0 \tan(\beta L)}{Z_0 + Z_L \tan(\beta L)} \right]$   
but  $Z_L = 0$

$$Z_{in} = Z_0 \tan(\beta L)$$

for no transmission loss:

$$Z_{in} = jZ_0 \tan(\beta L)$$

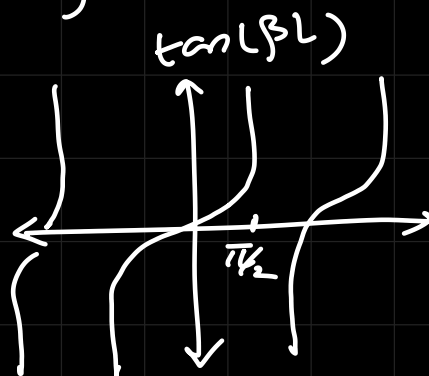inductive  
or  
capacitive?  
depends on  $L$



reflection coefficient?

we know  $\Gamma_L(z) = \frac{Z_L - Z_0}{Z_L + Z_0}$

and  $Z_L = 0$

so  $\Gamma_V(z) = -1$

and  $\Gamma_I(z) = -\Gamma_V(z) = 1$

if  $\beta L = \frac{\pi}{2}$

$\beta = \frac{2\pi}{\lambda} \rightarrow \frac{2\pi}{\lambda} L = \frac{\pi}{2}$

$L = \frac{\lambda}{4}$

and  $Z_{in} = \infty$   
because  
 $\tan(\pi) = \infty$

for  $L = \frac{\lambda}{2} \rightarrow \beta L = \pi \rightarrow Z_{in} = 0$

What if transmission line ended by open circuit?


$$Z_{in} = Z_0 \left[ \frac{Z_L + Z_0 \tan(\beta L)}{Z_0 + Z_L \tan(\beta L)} \right]$$

but  $Z_L = \infty$

$$\begin{aligned} Z_{in} &= Z_0 \left[ \frac{1 + Z_0/Z_L \tan(\beta L)}{Z_0/Z_L + \tan(\beta L)} \right] \\ &= Z_0 \left[ \frac{1}{j \tan(\beta L)} \right] = \underline{-j Z_0 \cot(\beta L)} \end{aligned}$$

$$Z_{in} = -j Z_0 \cot(\beta L)$$

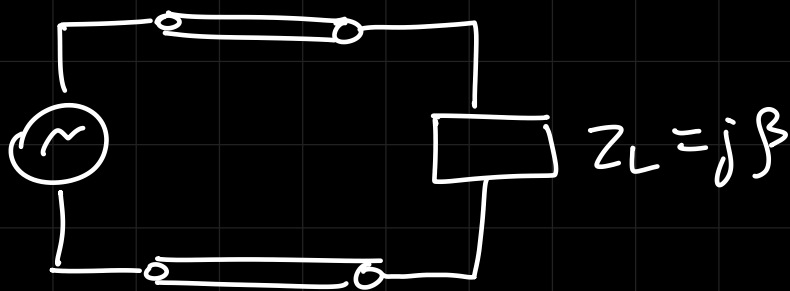So if we really want  $\infty$  input impedance we don't just do oc we short output and put  $L = \frac{\lambda}{2}$



$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= \frac{j\beta - Z_0}{j\beta + Z_0}$$

$$|\Gamma_L| = \text{reflection coefficient} = 1$$

perfect / pure reflection  
no absorption of energy  
goes back to SRC

Now prove,

A Perfect Electric Conductor is a perfect reflector

$$\Gamma = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1}$$

$$\eta_1 = \sqrt{\frac{\mu_0}{\epsilon_1}}$$

①

$$\eta_2 = \sqrt{\frac{\mu_0}{\epsilon_2}}$$

②

PEC

plasma frequency:  $\omega_p \sim \text{UV Range}$

$$\text{metal} \rightarrow \epsilon(\omega) = \epsilon_0 \left( 1 - \frac{\omega_p^2}{\omega^2} \right)$$

for  $\omega < \omega_p$  and lossless transmission,

$$\epsilon(\omega) = -ve$$

$$\text{So, } \eta_2 = \sqrt{\frac{\mu_0}{\epsilon_2}} = \sqrt{\frac{\mu_0}{-a}}$$

$$= jm$$

$$\Gamma = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1} = \frac{jm - \eta_1}{jm + \eta_1}$$

$$|\Gamma| = \frac{m^2 + n^2}{m^2 + n^2} = \underline{\underline{1}}$$

hence for  $\omega < \omega_p$  and lossless transmission, a metal acts as a perfect reflector

