
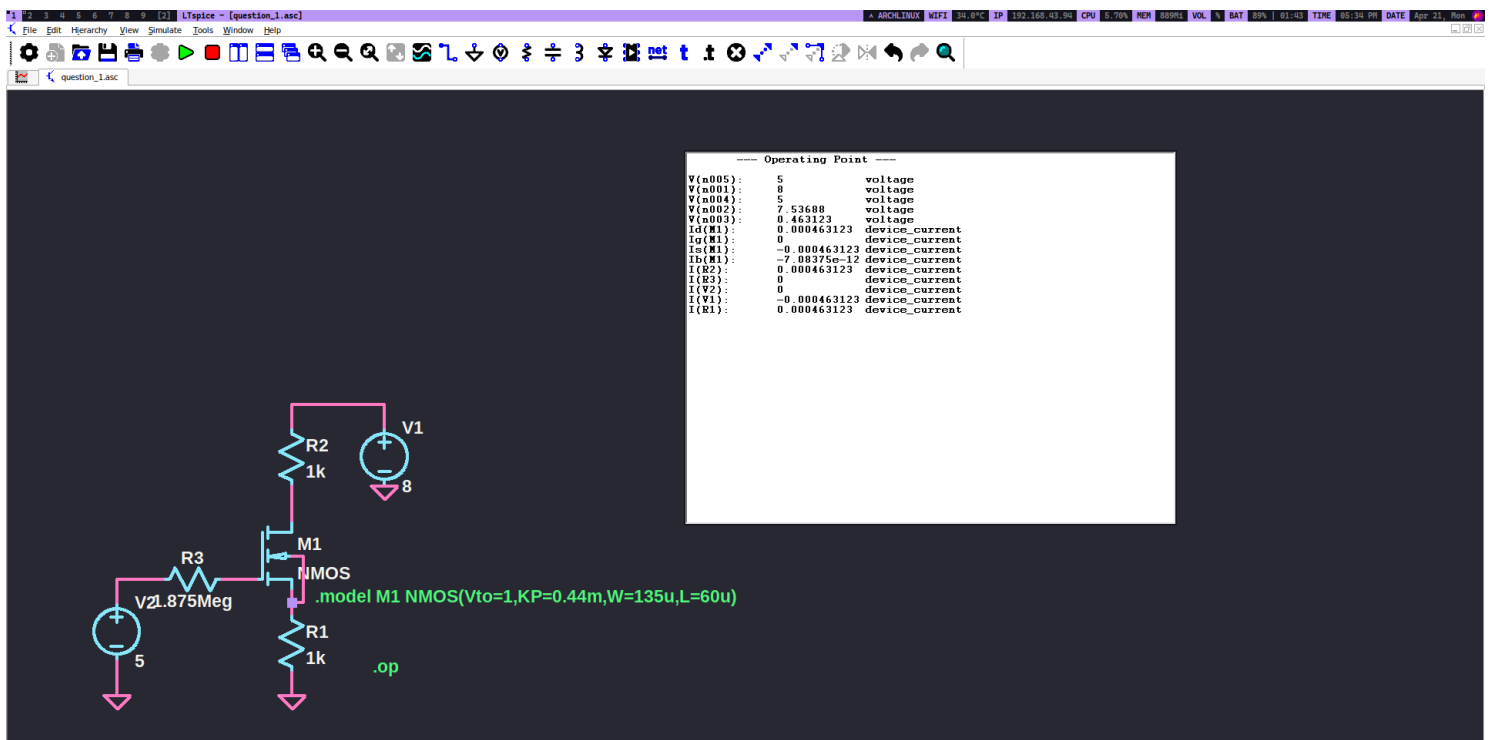



IE Tutorial Simulation 3 & 4

Aditya Gautam

2023043


Ans 1.

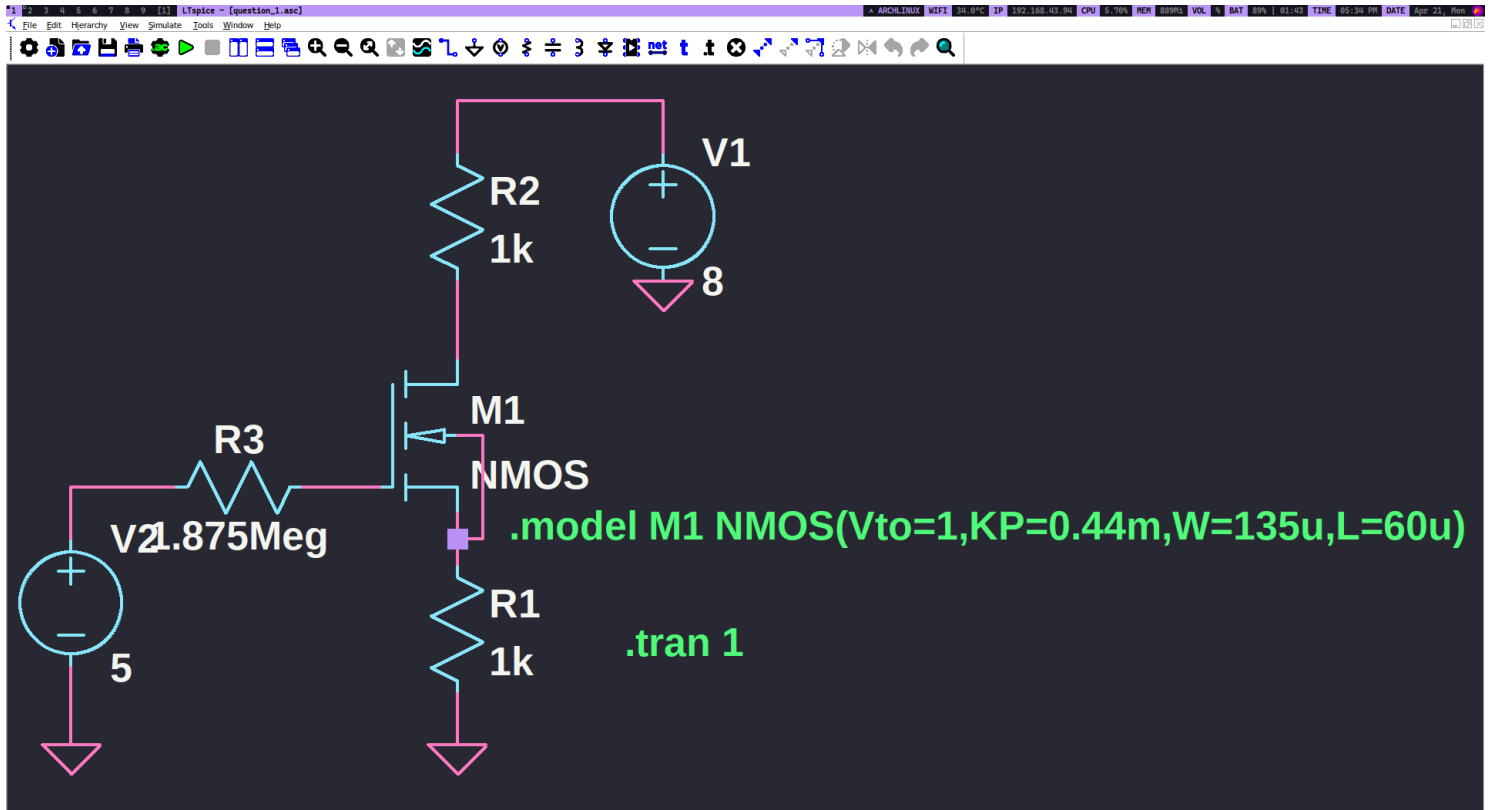

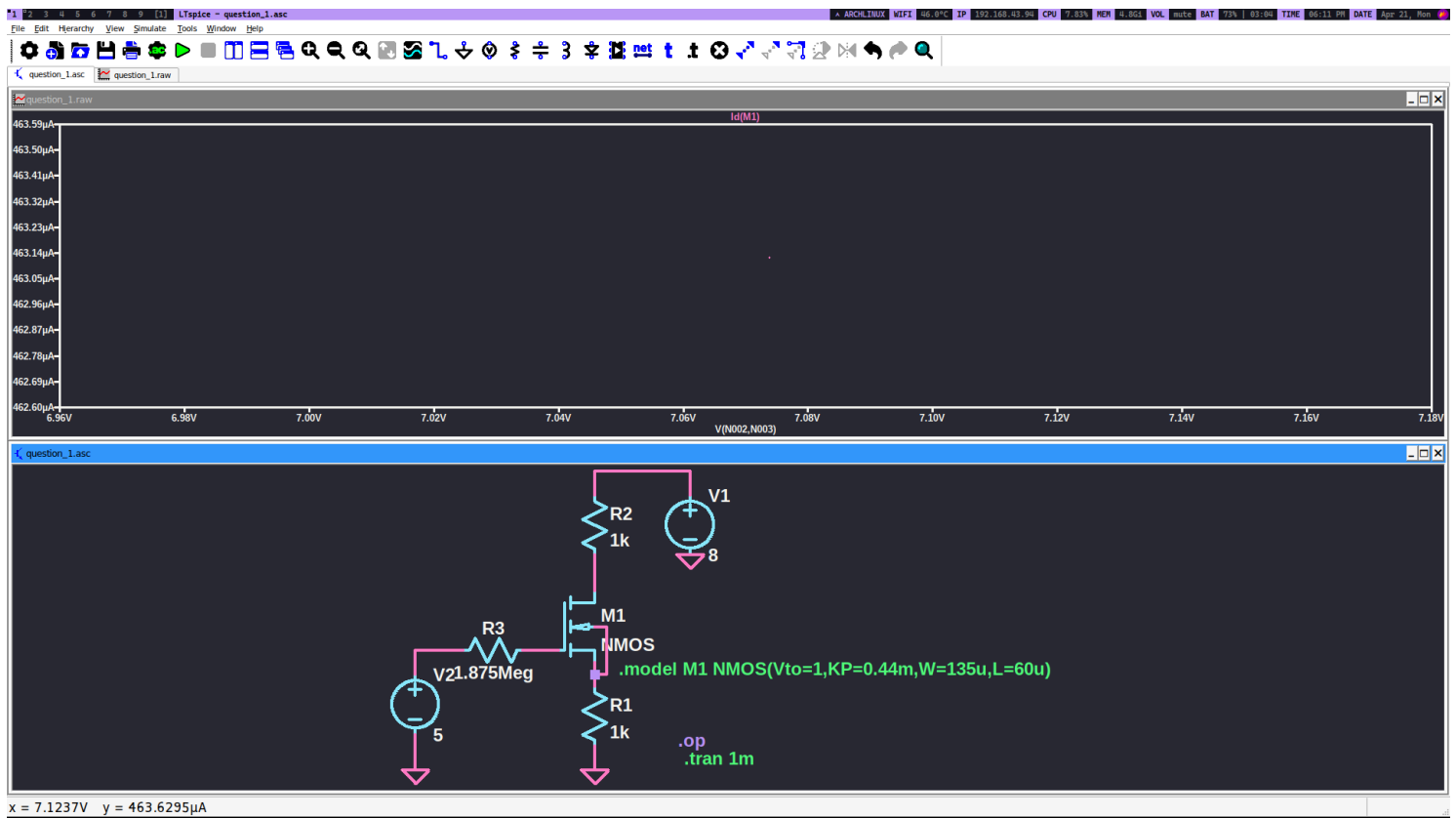

Note: I am getting a single point in the plot because in this circuit, I am getting constant I_D and V_{DS}

Ans 2.

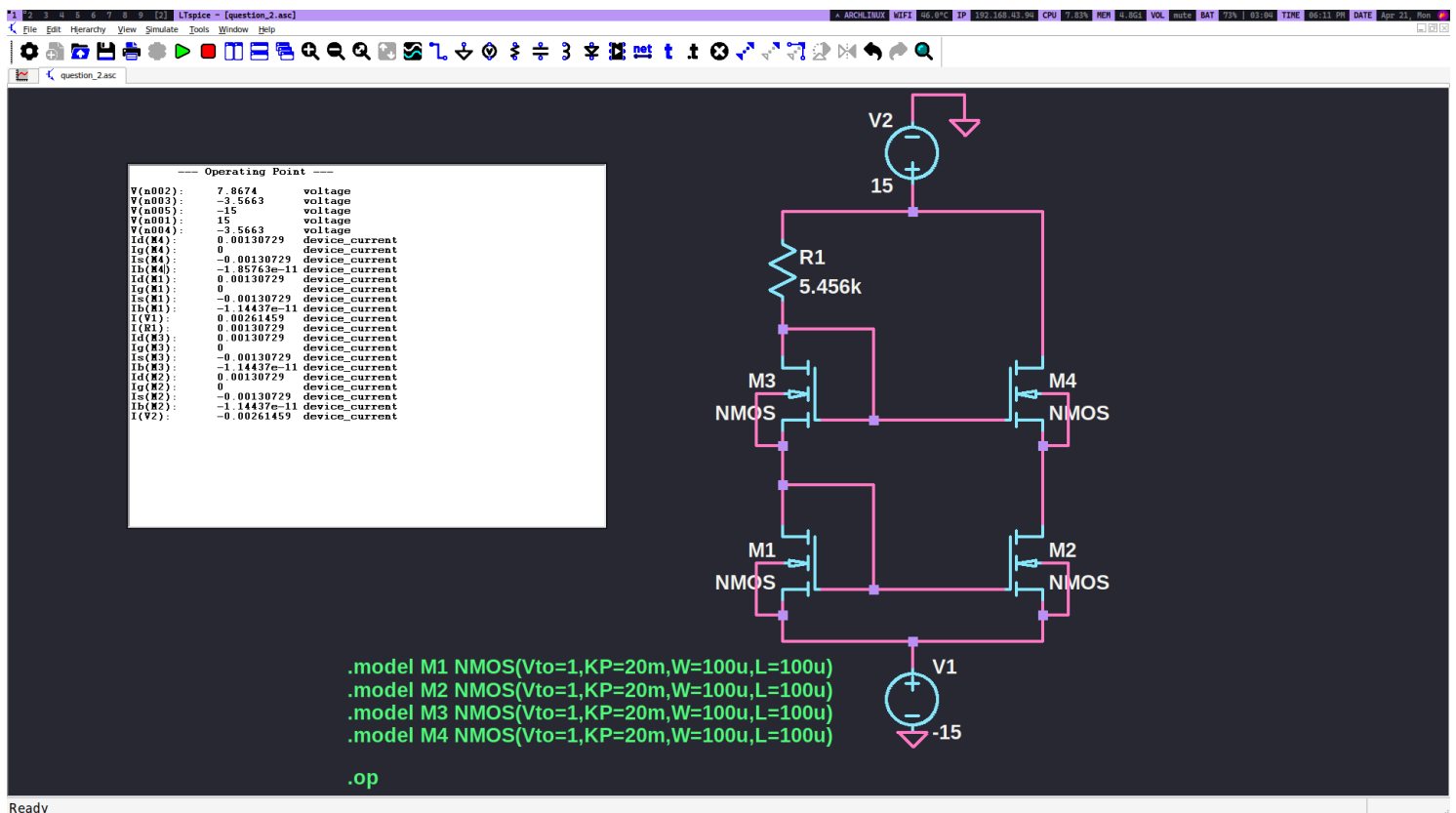

NOTE: I have made the same circuit and provided the MOSFET parameters as given in the question for both the questions but still I am getting wrong values in the analysis.

My theoretical answers ->

Q1. $I_D = 2\text{mA}$

Q2. $R = 5.456\text{k ohm}$