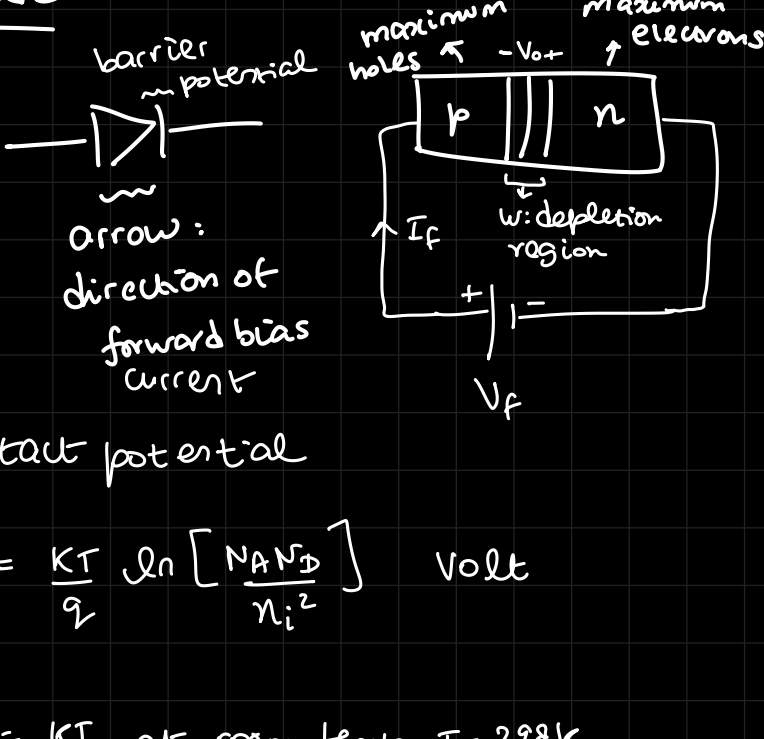


→ TF taking the lecture

Zener Diode



V_0 : contact potential

$$V_0 = \frac{kT}{q} \ln \left[\frac{N_A N_D}{n_i^2} \right] \text{ Volt}$$

$$V_T = \frac{kT}{q} \text{ at room temp, } T = 298K$$

$$k = 1.38 \times 10^{-23} \text{ J/K}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$V_T = \frac{T}{11,600} \text{ Volt} \approx 25mV$$

$$W = \sqrt{\frac{2\epsilon}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) V_0 - V}$$

width of depletion region

ϵ = electric permittivity

$$\epsilon = \epsilon_0 \epsilon_r$$

$$\downarrow$$

$$8.854 \times 10^{-12} \text{ F/m}$$

V = applied voltage

V_0 = contact potential

in reverse bias \rightarrow applied voltage = $-V_e = V$

$$V_0 - V = +ve$$

$$W = +ve \uparrow$$

Width of depletion region increases in reverse bias

In forward bias, depletion layer decreases

In reverse bias, depletion layer increases

w/o no bias

Diode general current equation

$$I = I_s \left[e^{\frac{V}{\eta V_T}} - 1 \right]$$

$$\eta = 1 \text{ for Ge and } 2 \text{ for Si}$$

$$2.7 \text{ for GaAs}$$

I_s = leakage current

V_F = forward bias voltage

$$\frac{V_F}{V_T} \rightarrow \frac{V_F}{25 \times 10^{-3}} = \frac{V_F \times 10^3}{25} > 1 \checkmark \text{ for forward bias}$$

$$e^{V_F/V_T} \gg 1$$

neglect the -1 wrt e^{V_F/V_T} in above eqn

$$I_F \approx I_s \left(e^{V_F/V_T} \right)$$

for reverse bias,

$$V = -V_e = -V_R$$

$$e^{-V_R/V_T} \ll 1$$

$$I_R \approx -I_s$$

$$Si \rightarrow 14 \rightarrow 2, 8, 4$$

$$Ge \rightarrow 32 \rightarrow 2, 8, 18, 4$$

valence e- easier to leave for Ge

but we still use Si why?

$$I_{s_{Si}} = nA$$

$$I_{s_{Ge}} = \mu A$$


because leakage current is way higher in case of germanium

ZENER DIODE

① Always works under reverse bias

② In forward bias, it acts as normal pn junction diode

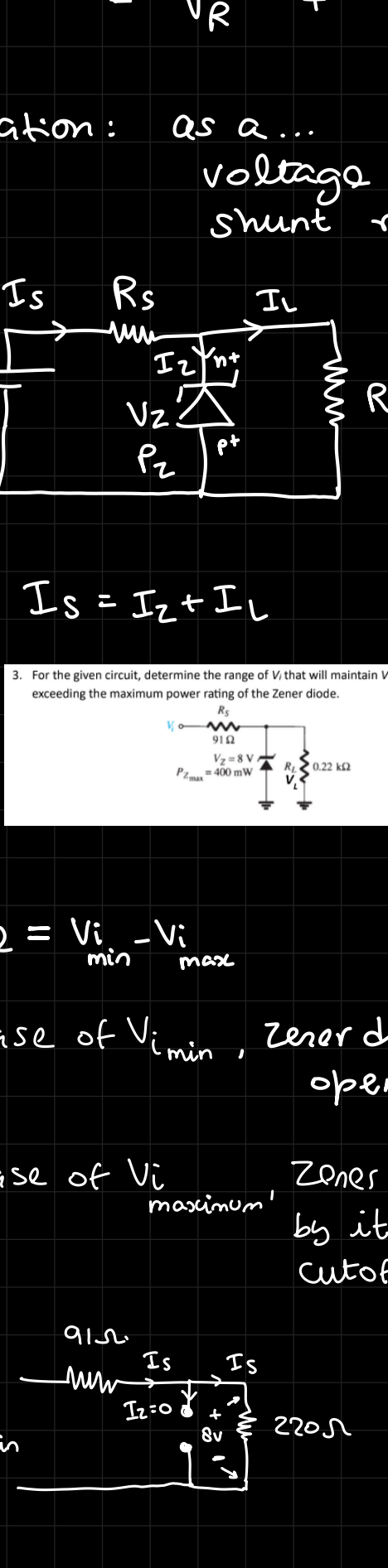③ Zener diode works always under high electric field



③ As we increase the reverse voltage, depletion layer also increases

$$W = \sqrt{\frac{2\epsilon}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) V_0}$$

$$W \propto \frac{1}{\sqrt{\text{doping concentration}}}$$

$$\text{and since } E \propto \frac{1}{W}$$


works in very high electric field

\equiv Very high current

④ Zener diode is a very highly doped pn junction

1 impurity in every 10^3 atom (Si/Ge)

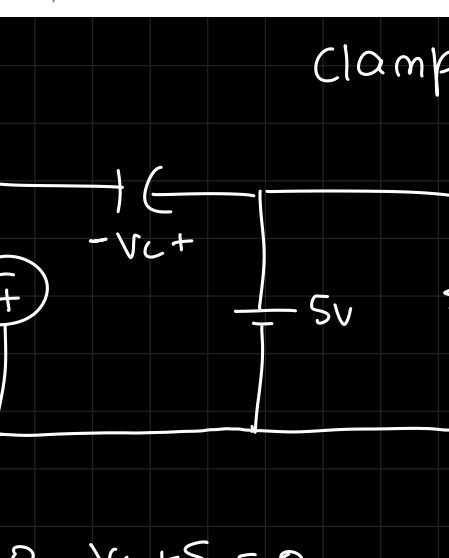normal pn junction diode $\rightarrow 1:10^6$




p^+, n^+ : highly doped

Application: as a ...


voltage regulator

shunt regulator

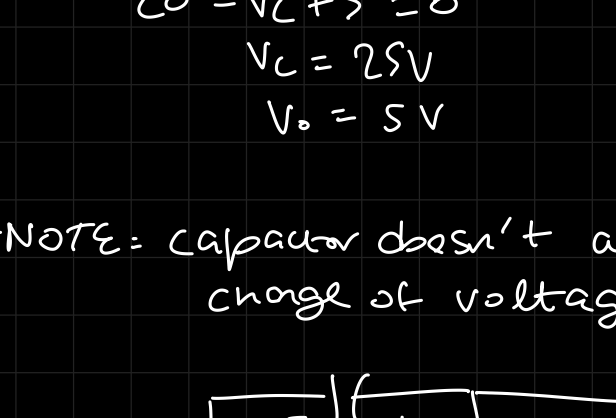

$$I_s = I_Z + I_L$$


g3)

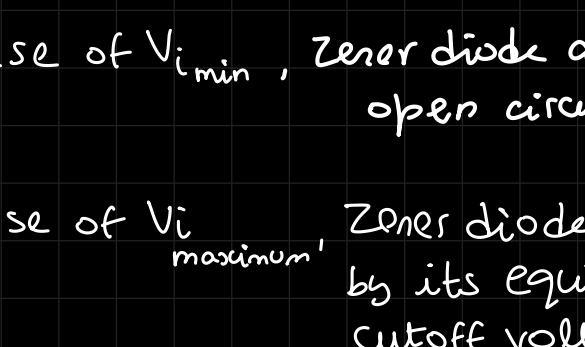

$$\text{Range} = V_{i_{\min}} - V_{i_{\max}}$$

in case of $V_{i_{\min}}$, Zener diode acts as open circuit

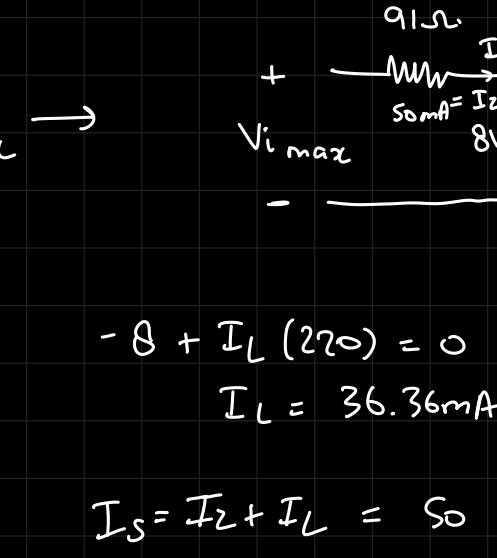in case of $V_{i_{\max}}$, Zener diode replaced by its equivalent cutoff voltage V_Z



$$P_Z = 400mW$$


$$V_Z = 8V$$

$$P_Z = V_Z I_Z$$

$I_Z = 50mA$ when Zener diode works properly

$$\frac{V_{i_{\min}} \times 220}{220 + 91} = 8$$

$$V_{i_{\min}} = 11.3V$$

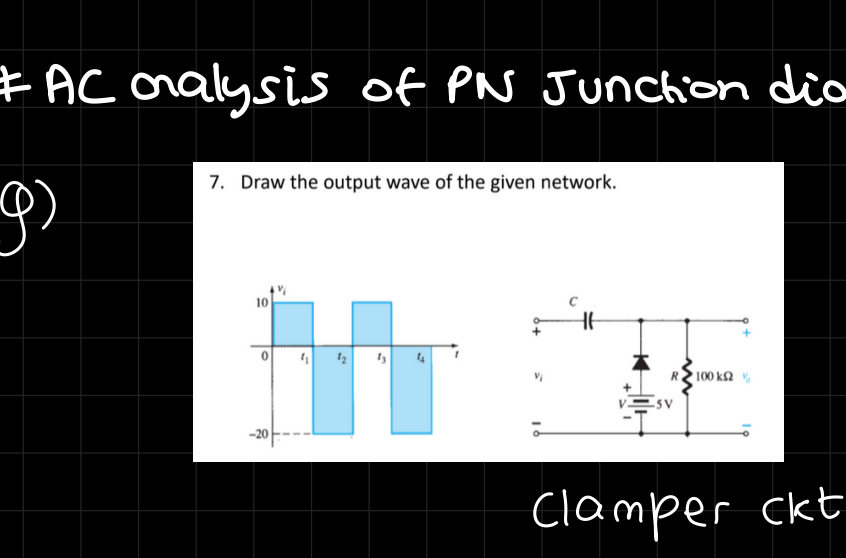

$$-8 + I_L(220) = 0$$

$$I_L = 36.36mA$$

$$I_s = I_Z + I_L = 50 + 36.36 = 86.36mA$$


$$8 - V_{i_{\max}} + 91(86.36 \times 10^{-3}) = 0$$

$$V_{i_{\max}} = 15.858V$$


$$\text{Range: } 11.3V < V_i < 15.85V$$

AC analysis of PN Junction diode

g)

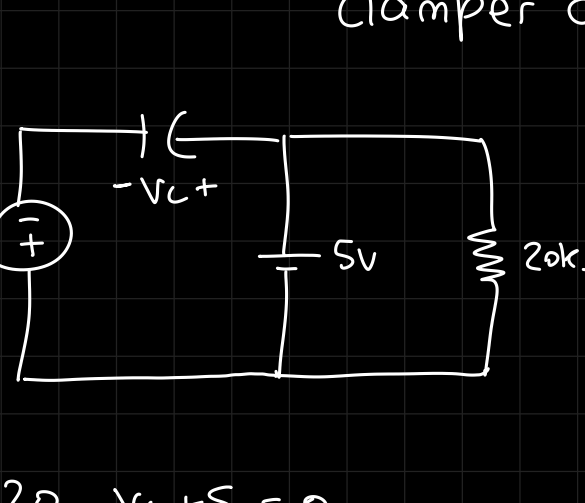

clamper ckt

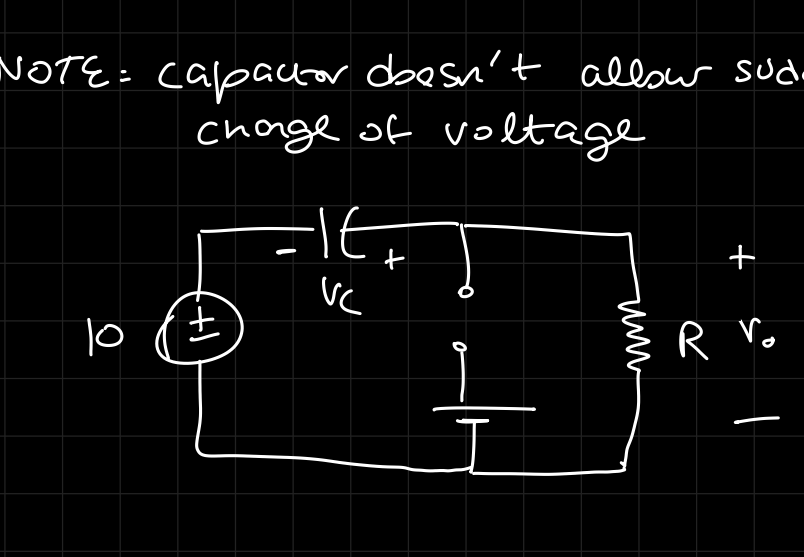


$$20 - V_C + 5 = 0$$

$$V_C = 25V$$

$$V_o = 5V$$
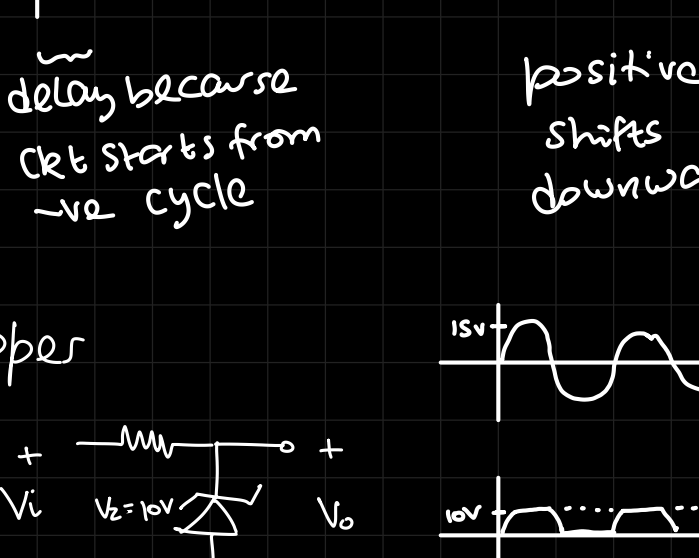
#NOTE = capacitor doesn't allow sudden change of voltage



$$-10 - V_C + V_o = 0$$

$$V_o = 10 + V_C = 10 + 25 = 35V$$


#NOTE: we take case where diode is on first



negative clamper because diode was $n \rightarrow p$


positive clamper shifts waveform downwards

Clipper

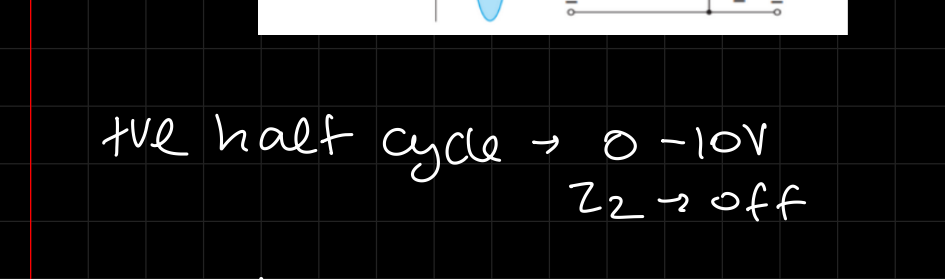

for

g)

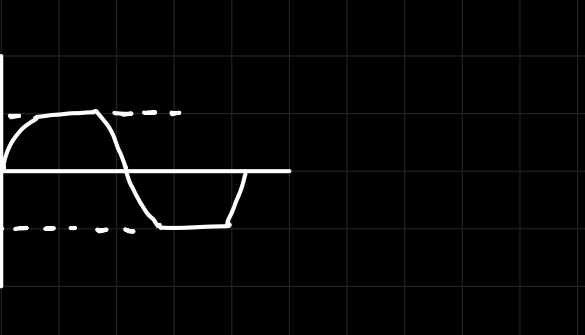

1st half cycle $\rightarrow 0 - 10V$

$Z_2 \rightarrow$ off

