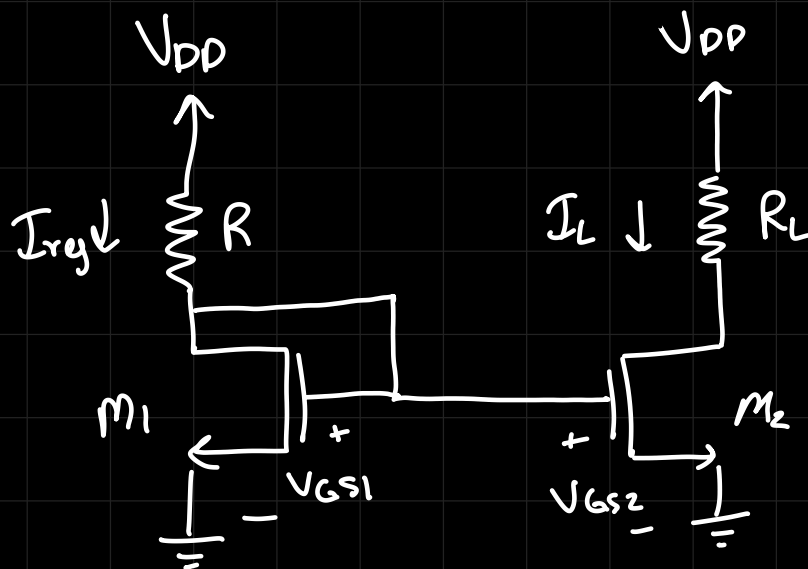


21st (Monday) → Tut sim x2 5-7pm

↳ MOSFET Biasing

↳ Current mirror/ cas code

lecture: current mirror



if M_1 and $M_2 \rightarrow k_n$ and V_T characteristics are same and they are in saturation,

$$I_L = I_{ref}$$

but is this true $\forall R_L$?

NO

we require M_2 to be in saturation.

$$V_{G2} > V_{T2}$$

$$V_{D2} > V_{G2} - V_{T2}$$

for M_1 ,

$$I_{ref} = \frac{V_{DD} - V_{D1}}{R}$$

now since $V_{D1} = V_{G1}$

$$I_{ref} = \frac{V_{DD} - V_{G1}}{R}$$

$$V_{G1} = V_{DD} - I_{ref} R$$

for $M_2 \rightarrow$

$$\left. \begin{array}{l} V_{D2} > V_{G2} - V_{T2} \\ V_{D2} > V_{G1} - V_{T1} \end{array} \right\} \therefore M_1 \approx M_2$$

$$V_{DD} - I_{RL} > V_{G1} - V_{T1}$$

$$V_{DD} - I_{ref} R_L > V_{G1} - V_{T1} \quad \left. \vphantom{V_{DD} - I_{ref} R_L} \right\} I_{ref} = I_L$$

(we want this)


$$V_{G1} = V_{DD} - I_{ref} R$$

$$V_{DD} - I_{ref} R_L > V_{DD} - I_{ref} R - V_{T1}$$

$$I_{ref} R + V_{T1} > I_{ref} R_L$$


$$R_L < \frac{V_{T1}}{I_{ref}} + R$$

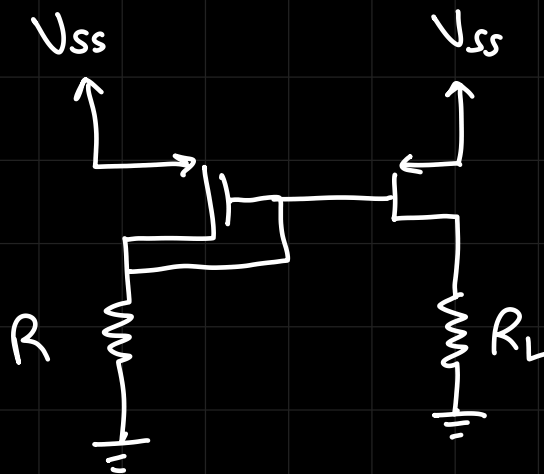if $R_L < R + \frac{V_T}{I_{ref}}$ then M_2 would be in saturation and $I_L = I_{ref}$



PMOS
current mirror

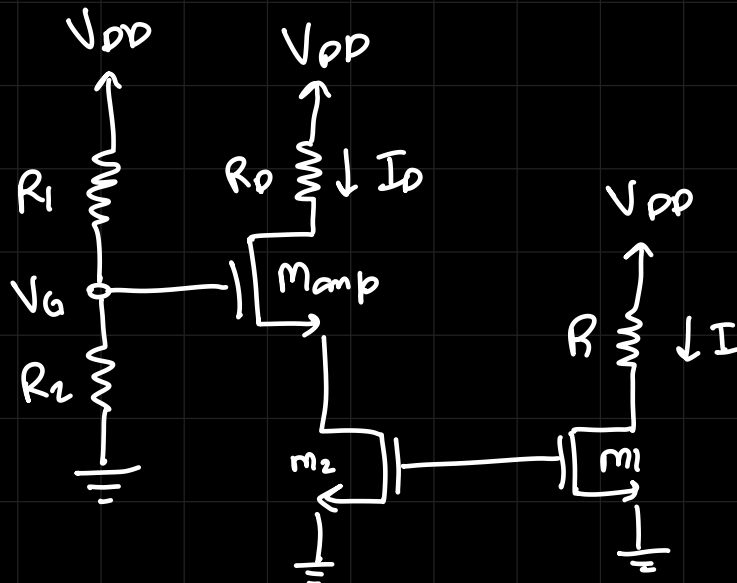We can use a current source to bias a MOSFET and for that we use the current mirror circuit



if $M_{amp} \equiv \text{saturation}$
 $I_d = k(V_{GS} - V_T)^2$

Since $I_d = I \rightarrow V_{GS} = \sqrt{\frac{I}{k}} + V_T$

$$V_G = V_{DD} \times \frac{R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - V_S$$

$$V_S = V_G - V_{GS}$$

$$= V_{DD} \left(\frac{R_2}{R_1 + R_2} \right) - \left(\sqrt{\frac{I}{k}} + V_T \right)$$

for saturation of M_{amp} : $V_{DS} > V_{GS} - V_T$

and to satisfy this, $V_{DS} \uparrow \uparrow \rightarrow V_S \downarrow \downarrow$



bias s.t. V_S is small
by tweaking R_2, R_1 ,

but V_S shouldn't be that small
because $V_S = V_{D2}$

{ Optimization problem }

Q// What is the limit to which we can reduce V_S ?

for $m_2 \equiv \text{saturation} \rightarrow$

$$V_{DS2} > V_{GS2} - V_{T2}$$

since $V_{S2} = V_{S1} = 0 \rightarrow$

$$V_{D2} > V_{G2} - V_{T2}$$

and since $V_S = V_{D2}$,

$$V_S^{\min} = V_{G2} - V_{T2} = V_{G1} - V_{T1}$$

put V_S^{\min} in $V_G = V_{GS} + V_S$

$$V_G = V_{GS} + V_{G1} - V_{T1}$$

for $M_{\text{omp}}: V_{GS} = \sqrt{\frac{I}{k}} + V_T$

$$V_{GS1} = V_{G1} = V_{DD} - IR$$

$$V_G = \sqrt{\frac{I}{k}} + V_{T_{\text{omp}}} + V_{DD} - IR - V_{T1}$$

\hookrightarrow and $V_G = V_{DD} \times \frac{R_2}{R_1 + R_2}$

This is the min value of V_G
we need to maintain

R_1 and R_2 are input impedance
and hence for the op, R_1 and $R_2 \gg$
to prevent signal loss

R_1, R_2 : as high as possible

now what about R_D = ?

$M_{amp} \equiv$ should be in SATURATION

$$V_{DS} > V_{GS} - V_T$$

i.e. V_D should \uparrow

$$\text{and } V_D = V_{DD} - I_D R_D$$

So, R_D should be less

$$V_S^{\min} > V_{G1} - V_{T1}$$

$$V_D - V_S > \underbrace{V_{GS} - V_T}_{M_{amp}}$$


$$V_{DD} - I_D R_D - V_{S1} > V_{GS} - V_T$$

$$R_D < \frac{V_{DD} - V_S - V_{GS} + V_T}{I_D}$$

for $I_D = I$ (Current mirror)

$$R_D < \frac{V_{DD} - V_G + V_T}{I}$$

φ}

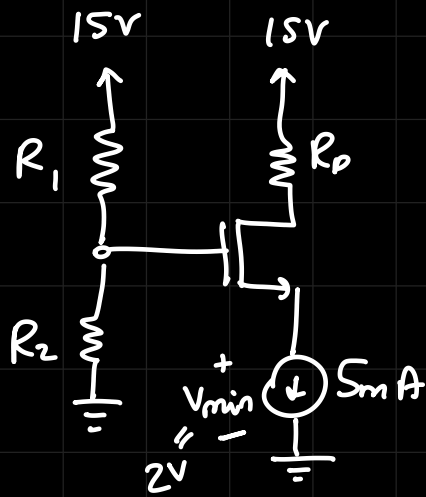

$$K = 0.2 \times 10^{-3}$$

$$V_T = 1V$$

$$V_{GS} = \sqrt{\frac{I}{K}} + V_T$$

$$I_d = K(V_{GS} - V_T)^2$$

$$V_{GS} = \sqrt{\frac{5}{0.2}} + 1 = \underline{\underline{6V}}$$

$$V_S^{min} = 2V$$

$$V_G = \underline{\underline{8V}}$$

$$V_G = 15 \times \frac{R_2}{R_1 + R_2}$$

$$\frac{R_2}{R_1 + R_2} = \frac{8}{15}$$

$$8R_1 + 8R_2 = 15R_2$$

$$8R_1 = 7R_2$$

lets choose $R_1 = 7M\Omega \rightarrow R_2 = 8M\Omega$

$$R_D \leq \frac{V_{DD} - V_G - V_T}{I_D} = \frac{15 - 8 + 1}{5} k\Omega$$

$$= \frac{8}{5} k\Omega = \underline{1.6 k\Omega}$$

$$\boxed{R_D \leq 1.6 k\Omega}$$

check if Amp \rightarrow saturation mode

$$V_{DS} > V_{GS} - V_T$$

$$-15 + 8 + V_{DS} + 2 = 0$$

$$V_{DS} = 5V$$

$$V_D = 7V$$

$5 > 6 - 1 \checkmark$ but just at the
edge of saturation
for $R_D = 1.6 k\Omega$

Choosing $R_D = 1 k\Omega$ would be more suited.


$\Rightarrow R_D$ will change the slope of the load line



slope: $\frac{1}{R_D}$

Current Steering Circuit

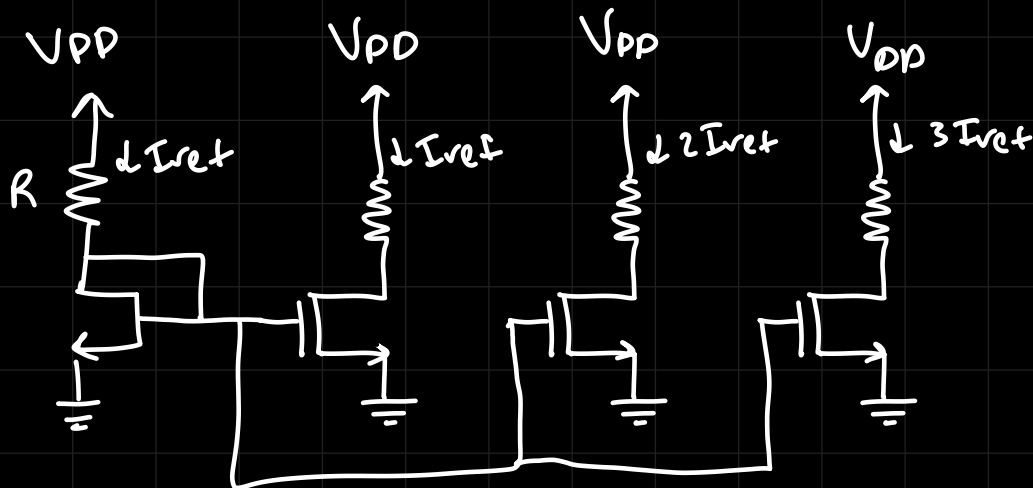Create multiple I sources from a single reference current.



The current mirror ckt ensures V_{GS} to be same as reference branch so that same ref current flows through each identical branch (MOSFETs)

$$V_{GS}^{ref} = V_{GS1} = V_{GS2} = \dots$$

if mos are identical,

$$K_{ref} = K_1 = K_2 = \dots$$

$$\text{and } V_T^{ref} = V_{T1} = V_{T2} = \dots$$

now if i want scaled ref current for diff branches,

$$\text{eg: for } n^{\text{th}} \text{ branch} \rightarrow I_{Dn} = K_n (V_{GSn} - V_{Tn})^2$$

We know $I_D = k_{ref} (V_{GS}^{ref} - V_T)^2$

if $k_{ref} \neq k_n$, $\frac{I_{Dn}}{I_D} = \frac{k_n}{k_{ref}} \frac{(V_{GSn} - V_{Tn})^2}{(V_{GS}^{ref} - V_T)^2}$

scaling
factor

$$I_{Dn} = \frac{k_n}{k_{ref}} I_D$$

current steering

$$I_{D1} = 25 \mu A$$

$$I_{D2} = 50 \mu A$$

$$I_{D3} = 125 \mu A$$

$$I_{D4} = 25 \mu A = I_{D5}$$

$$V_{GS1} = \sqrt{\frac{I}{k}} + V_T = \sqrt{\frac{25 \mu}{5 \times 50 \mu}} + 1$$

$$R = \frac{V_{G4} - V_{G1}}{I_{ref}}$$

PMOS: m_n

$$V_{SD} = V_S - V_D$$

$$V_A = V_D = S - V_{Sp} = S - V_{SG} = S + V_{GS}^p$$

$$\text{for } M_1 : V_{DS} = V_D - V_S$$

$$V_{DS} = V_D + S$$

$$V_{GS} = V_D + S$$

$$V_B = V_D = V_{GS} - S$$

$$R = \frac{V_A - V_B}{I_{ref}} = \frac{V_{GS} + S + S - V_{GS}}{2S\mu A}$$

$$\text{for } M_4 \rightarrow I_{d4} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) (V_T - V_{GS})^2$$

$$\text{for } M_1 \rightarrow I_{d1} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

$$(V_{GS} + 1)^2 = \frac{2S\mu \times 2}{20\mu \times 5}$$