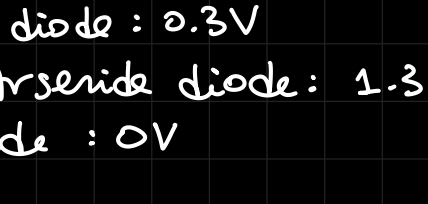


Tue: 2

PN Junction diode



* diode equivalent circuit



Silicon diode : 0.7V

Germanium diode : 0.3V

Gallium Arsenide diode: 1.3V

Ideal diode : 0V

r_f : forward resistance

V_f : cutoff voltage

$$r_{ac} = r_f = \eta \frac{V_T}{I_L}$$

η : utility factor

$V_T = 25\text{mV}$: thermally generated voltage


Bohrsmann \rightarrow temp (Kelvin) : room temp $\rightarrow 298\text{K}$

const $V_T = \frac{kT}{q}$

$= 1.38 \times 10^{-23} \text{ J/K}$ q : magnitude of charge $= 1.6 \times 10^{-19} \text{ C}$

$\approx 25\text{mV}$ at room temperature

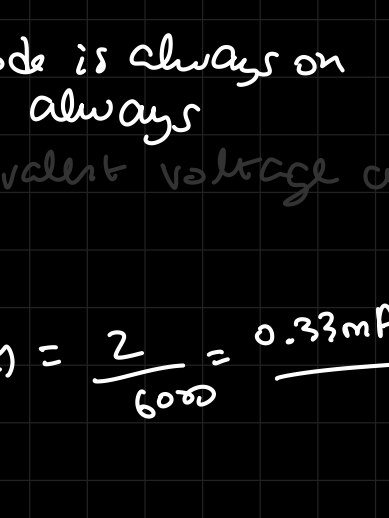
Q1) $V_{on} = 0.7\text{V}$
diode "on" voltage
current i_z (mA)



a) if $V' > 0.7\text{V}$, diode is on
diode replaced by equivalent cutoff voltage
forward bias


$$V_{AB} = 2 \times \frac{2000}{2000+6000} = 0.5\text{V}$$

diode is always off $\rightarrow \infty$

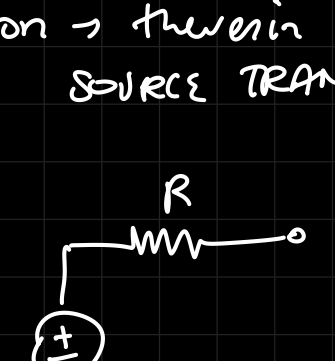

$$i(t) = \frac{2}{8000} = 0.25\text{mA}$$

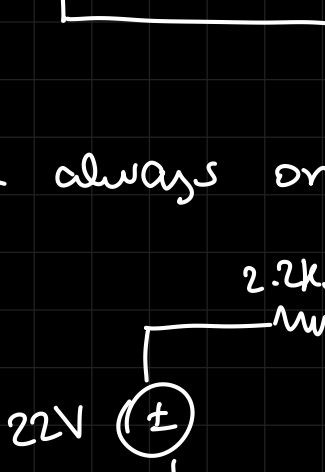b) for ideal case \rightarrow diode is always on
because $0.5\text{V} > 0\text{V}$ always
replaced by equivalent voltage cutoff




$$i(t) = \frac{2}{6000} = 0.33\text{mA}$$

we apply voltage at $2\text{k}\Omega$ is 0.5V
and since $0.5 > 0$, diode is always on



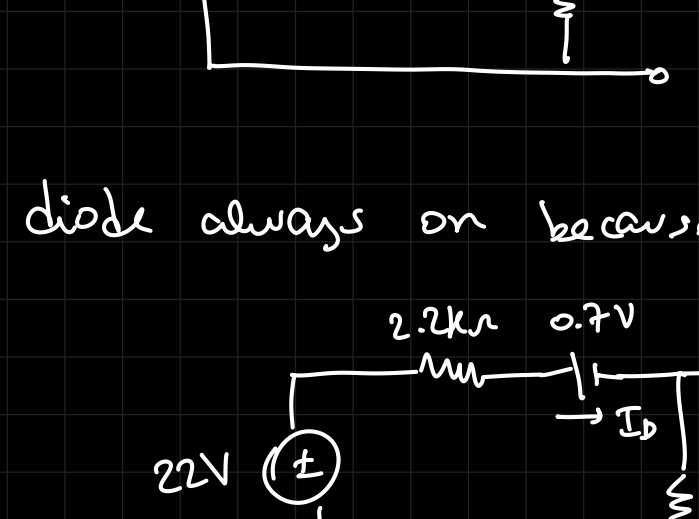
Q2) output voltage V_o } ?
diode current I_D }

note: diode senses only voltage src $V_m = 0.7\text{V}$




norton \rightarrow thevenin

SOURCE TRANSFORMATION

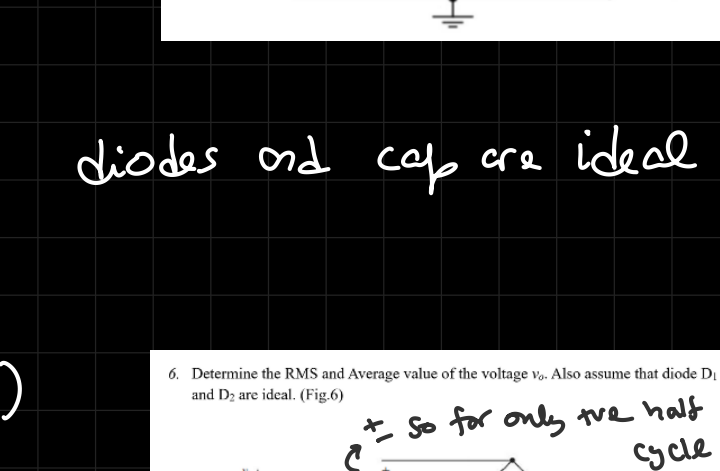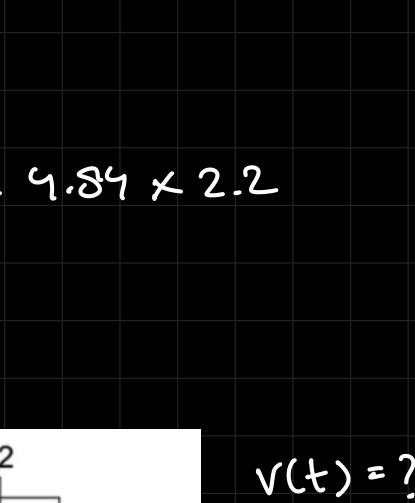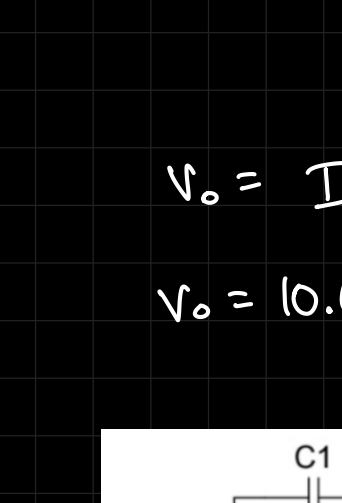

diode always on because $22 > 0.7$

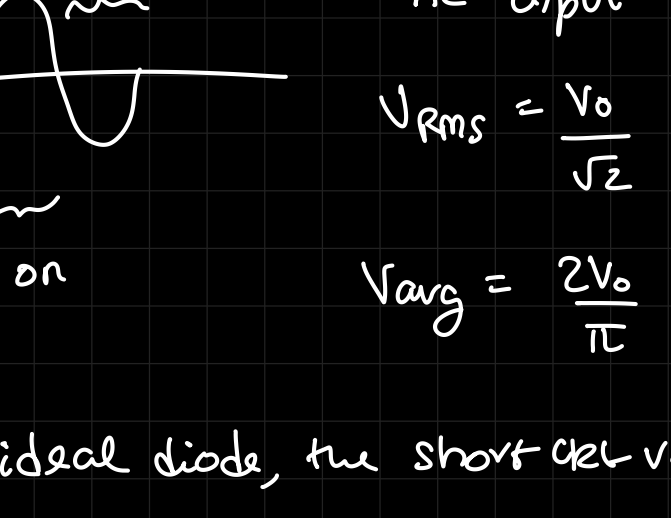


$$-22 + 2.2 I_D + 0.7 + 2.2 I_D = 0$$

$$I_D = \frac{21.3}{4.4} \text{ mA} = 4.84 \text{ mA}$$

$$V_o = I_D R = 4.84 \times 2.2$$

$$V_o = 10.648 \text{ V}$$



Q3)

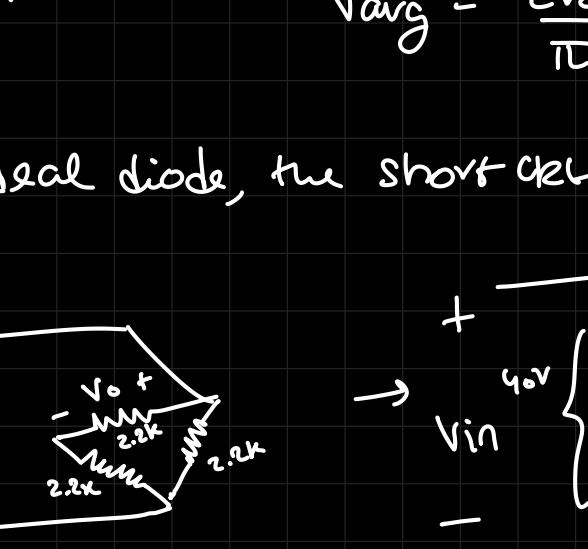

$V(t) = ?$

diodes and cap are ideal in this ckt

Q6)

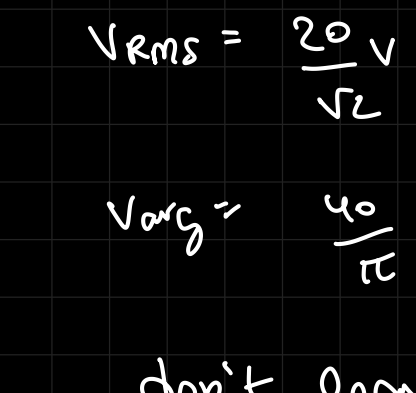
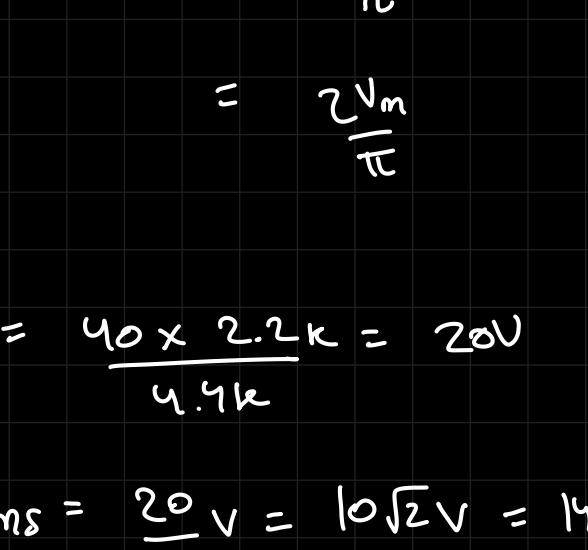


AC input

$$V_{RMS} = \frac{V_o}{\sqrt{2}}$$

$$V_{avg} = \frac{2V_o}{\pi}$$

for ideal diode, the short ckt volt = 0V

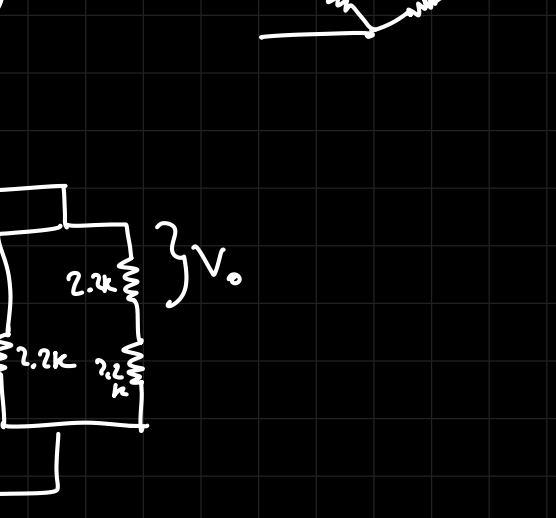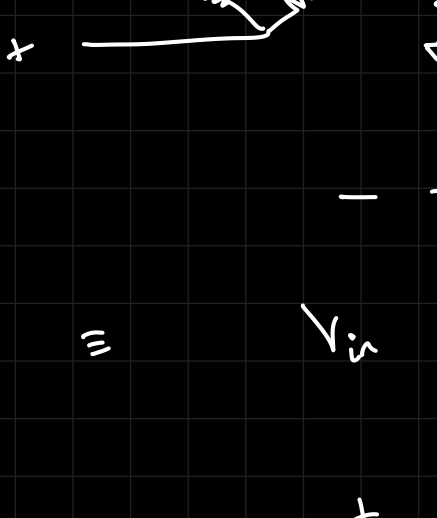

$$V_{avg} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$

$$= \frac{V_m}{\pi} [-\cos(\omega t)]$$

$$= \frac{V_m}{\pi} [-\cos(\pi) + \cos(0)]$$

$$= \frac{2V_m}{\pi}$$


$$V_o = \frac{40 \times 2.2\text{k}}{4.4\text{k}} = 20\text{V}$$

$$V_{RMS} = \frac{20}{\sqrt{2}} \text{ V} = 10\sqrt{2} \text{ V} = 14.14 \text{ V}$$

$$V_{avg} = \frac{40}{\pi} = 12.7\text{V}$$

don't leave in $\sqrt{2}$ form
solve it

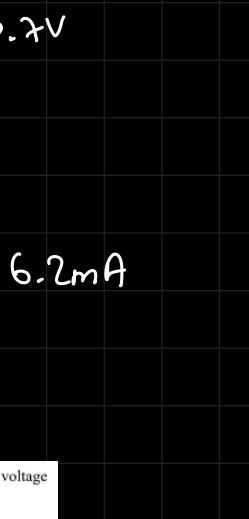for the negative half cycle (not needed according to ques)




$$V_o = \frac{-40 \times 2.2\text{k}}{4.4\text{k}} = -20\text{V}$$

$$V_{RMS} = \frac{-20}{\sqrt{2}} = -14.14\text{V}$$

$$V_{avg} = \frac{-20 \times 2}{\pi} = \frac{-40}{\pi} = \frac{40}{3.14} \approx -12.7\text{V}$$

Q5)

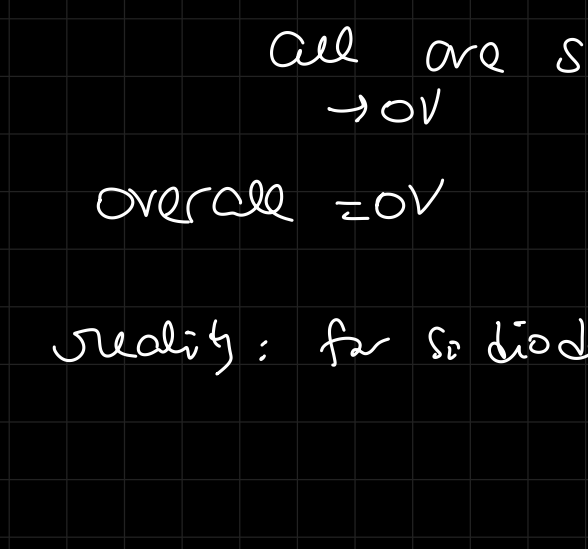

not a silicon diode

general diode

exponential
V-I characteristic

but in the ques V-I characteristic is linear
so not a silicon diode

ques diode

which will have greater slope

$$\text{for } V > 0.7\text{V} \Rightarrow i = \frac{V - 0.7}{500}$$

$$500i + 0.7 = V$$

$$500di + 0 = dV$$

$$\frac{dV}{di} = 500\Omega \text{ (Resistance offered by the PN junction diode)}$$


circuit:



$$-10 + 0.7 + 1500i = 0$$

$$i = \frac{9.3}{1.5} \text{ mA} = 6.2\text{mA}$$

Q4)

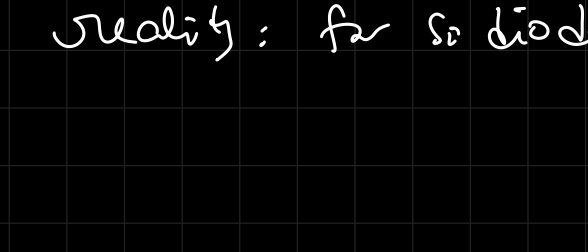

for the half cycle,
all diodes are off
all ∞
 $\rightarrow 0\text{V}$

for the half cycle

all are short ckt
 $\rightarrow 0\text{V}$

overall $= 0\text{V}$

Reality: for Si diode $\rightarrow 4 \times 0.7 \Rightarrow 2.8\text{V}$